

# LSP考试结果与解析 — 2026年1月13日

CVUT FEL (CVUT) – České vysoké učení technické v Praze | Czech Technical University in Prague

中文版 | English | Čeština

Course: B0B35LSP – Logické systémy a procesory | BE5B35LSP – Logic Systems and Processors

Keywords: Zkouska, Exam, Test, Solutions, Výsledky, Answers, K-Map, RS Latch, Pipeline

---

## 官方结果（原始）+ 详细解析

Source PDF (official sheet): 2026-01-13\_Exam\_Results\_Official.pdf

说明: The PDF contains diagrams (circuits/K-maps). Text extraction preserves most of-ficial answers, but some purely-graphical parts (notably Q6/Q7 drawings) may not appear as plain text. When a diagram answer is not fully extractable, this document links back to the PDF and provides a robust solving method.

---

## 第1题 — Moore/Mealy FSM ordered tuple

官方答案 (from PDF)

- $X$  is finite set of all input vectors
- $S$  is finite set of all output vectors
- $Z$  is finite set of all internal states
- $\delta$  is a mapping
  - Moore:  $\delta : X \times S \rightarrow S$
  - Mealy:  $\delta : X \times S \rightarrow S$
- $\omega$  is a mapping
  - Moore:  $\omega : S \rightarrow Z$
  - Mealy:  $\omega : X \times S \rightarrow Z$
- $s_0$  is initial state  $s_0 \in S$

解析 (how to write it fast)

- **Moore:** output depends only on state  $S$ .
  - **Mealy:** output depends on input+state  $X \times S$ .
- 

## 第2题 — Simulate circuit outputs $X$ and $Y$ at $t_0..t_4$

官方答案 (from PDF)

Inputs (as shown): –  $A$ : 0 | 1 | 1 | 0 | 0 –  $B$ : 1 | 1 | 0 | 0 | 1

Outputs: –  $X$ : 0 | 1 | 1 | 1 | 0 –  $Y$ : 1 | 0 | 0 | 0 | 1

### 解析 (why these values)

From the official Q3 formula for the same circuit (see next question), we can interpret  $X$  as a **level-sensitive latch** controlled by  $B$ : – If  $B = 1$  then  $X$  follows  $A$  (transparent) – If  $B = 0$  then  $X$  holds its previous value (memory)

So: –  $t_0$ :  $B = 1 \Rightarrow X = A = 0$ ; and the given result shows  $Y = \neg X = 1$  –  $t_1$ :  $B = 1 \Rightarrow X = A = 1$ ;  $Y = 0$  –  $t_2$ :  $B = 0 \Rightarrow X$  holds 1;  $Y = 0$  –  $t_3$ :  $B = 0 \Rightarrow X$  still holds 1;  $Y = 0$  –  $t_4$ :  $B = 1 \Rightarrow X = A = 0$ ;  $Y = 1$

---

### 第3题 — Shannon expansion + Karnaugh maps ( $f_0, f_1$ )

#### 官方答案 (from PDF)

The official expression shown:

•

$$X = (A \wedge B) \vee (X \wedge (\neg B \vee (A \wedge B)))$$

And: –  $f_0 = A \wedge B$  –  $f_1 = (A \wedge B) \vee (\neg B \vee (A \wedge B)) = (A \wedge B) \vee \neg B = A \vee \neg B$

#### 解析 (copy-paste method)

Given  $X = f(A, B, X)$ , Shannon on variable  $X$ :

$$X = (\neg X \wedge f_0(A, B)) \vee (X \wedge f_1(A, B))$$

Compute by substitution: –  $f_0(A, B) = f(A, B, 0)$  –  $f_1(A, B) = f(A, B, 1)$

Then simplify: –  $f_1 = (A \wedge B) \vee \neg B = A \vee \neg B$  (absorption)

Interpretation shortcut: – When  $B = 1$ :  $f_1 = A \vee 0 = A$  so  $X$  becomes  $A$  (transparent) – When  $B = 0$ :  $f_1 = A \vee 1 = 1$  so  $X$  becomes  $X$  (hold)

---

### 第4题 — 12-bit number as unsigned and signed (two's complement)

Number: 1000 0001 1111

#### 官方答案 (from PDF)

- Unsigned: **2079**
- Signed (two's complement): **-2017**

#### 解析

Let  $N = 12$ , unsigned value: –  $1000\ 0001\ 1111_2 = 2^{11} + 2^4 + 2^3 + 2^2 + 2^1 + 2^0 = 2048 + 31 = 2079$

Two's complement signed: – MSB is 1 so it is negative –

$$\text{signed} = \text{unsigned} - 2^{12} = 2079 - 4096 = -2017$$

---

## 第5题 — Equivalent logic functions

The PDF text extraction shows the four candidate functions ( $y_1..y_4$ ), but does not explicitly print the “marked” selection.

已验证等价性 (by exhaustive truth-table check)

- $y_1 \equiv y_2 \equiv y_4$
- $y_3$  is not equivalent to them

真值表 (ordered by  $A, B, C$  from 000 to 111): –  $y_1$ : 11011000 –  $y_2$ : 11011000 –  $y_4$ : 11011000 –  $y_3$ : 01011100

So the correct “mark” set is:  $y_1, y_2, y_4$ .

---

## 第6题 — One-bit full adder (complete the schema)

The PDF page shows a schematic to be completed; the exact gate drawing may not appear in plain text extraction.

Standard correct completion (equations)

Let inputs be  $A, B, C_{in}$  and outputs be Sum  $S$  and Carry-out  $C_{out}$ :

- $$S = A \oplus B \oplus C_{in}$$
- $$C_{out} = (A \wedge B) \vee (C_{in} \wedge (A \oplus B))$$

Wiring hint

- First XOR:  $X_1 = A \oplus B$
  - Second XOR:  $S = X_1 \oplus C_{in}$
  - ANDs:  $G_1 = A \wedge B, G_2 = C_{in} \wedge X_1$
  - OR:  $C_{out} = G_1 \vee G_2$
- 

## 第7题 — Gate-only implementation (AND/NAND/OR/NOR/NOT)

The official result for Q7 is primarily diagrammatic in the PDF. If you need an exact “final wiring”, refer to the diagram in: – 2026-01-13\_Exam\_Results\_Official.pdf

Reliable solving method

- Rewrite everything into only **NAND** (or only **NOR**) using De Morgan
  - Replace XOR/XNOR using standard NAND/NOR constructions
  - Keep track of inversions (bubble-pushing)
-

## 第8题 — 5 pipeline instruction phases + operations

官方答案 (from PDF)

- **FETCH** — fetches an instruction from memory.
- **DECODE** — the instruction is decoded and operand values are read from registers.
- **EXECUTE** — ALU performs an operation on decoded operands.
- **MEMORY** — possible work with memory; read/write using ALU address; if branch then write new address to PC.
- **WRITE-BACK** — results are saved in registers.

Exam-friendly wording

- IF / ID / EX / MEM / WB (the classic 5-stage pipeline naming)
- 

## 附录 — How Q5 equivalence was checked

A brute-force truth table over all  $A, B, C \in \{0, 1\}$  shows  $y_1 = y_2 = y_4$  for all 8 combinations.