



Exam 15 January 15.1.18, questions and answers

Logic Systems And Processors (České Vysoké Učení Technické v Praze)




Scan to open on Studocu

Surname and first name:.....

Exam 15.1.2018- write here only your answers

 
1. Rewrite the logical expression F so that not operators were only before variables - check your solution in K-map!

$F = \text{not} ((A \text{ or } \text{not } B \text{ or } \text{not } C) \text{ or } ((A \text{ or } B) \text{ and } \text{not} (A \text{ or } \text{not } C)))$





F =

 2. Inputs A, B, C have values shown in the figure in times t_0, t_1, t_2, t_3 . Write values of X and Y outputs. Assume that the intervals between changes in the inputs are so long so we can neglect delays of gates.



  3. Function $Q=f(A,B,C, Q)$ from question 2, decompose into $X= (\text{not } X \text{ and } f_0(A, B,C)) \text{ or } (X \text{ and } f_1(A,B,C))$ with the aid of Shannon's expansion. Write f_0 and f_1 functions as Karnaugh maps:



4. What decimal value is 10-bit number 10 0000 1111 if we interpret it as an integer

a) unsigned b) signed in two's-complement.....

5. Mark all logic functions that have another equivalent logic function here :

$f1 \leq (A \text{ xor } C) \text{ or } (A \text{ and } \text{not } C);$
 $f2 \leq (B \text{ or } C) \text{ and } (\text{not } A \text{ or } B \text{ or } C);$
 $f3 \leq ((C \text{ and } \text{not } B) \text{ or } (B \text{ and } A));$
 $f4 \leq (A \text{ or } C) \text{ and } (\text{not } A \text{ or } \text{not } C);$
 $f5 \leq (A \text{ and } \text{not } B) \text{ xor } (A \text{ and } C);$
 $f6 \leq (A \text{ and } \text{not } C) \text{ or } (C \text{ and } \text{not } A);$

f1 ☐

f2 ☐




f3 ☐

f4 ☐

f5 ☐

f6 ☐

   6. By adding gates (4 NAND and 3 NOT) and wires, create internal schematic of master-slave flip-flop DFF.




12

7. An editor ask you if you could analyze wrong formatted VHDL code:

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity test20140214 is port (a, b, c, d : in std_logic; e : out std_logic); end;
architecture rtl of test20140214 is begin
  process(a, b) variable z:std_logic_vector(0 to 3); begin
    if b = '0' then z:=(others=>'0'); elsif rising_edge(a) then
      if c='1' then z:=d & & z(0 to 2); else z:=z(3) & z(0 to 2); end if; end if; e<=z(3); end process; end rtl;
```

12

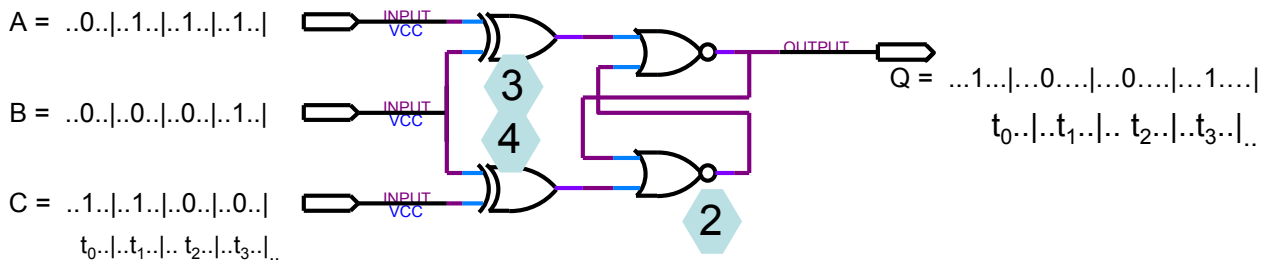Draw a logical circuit diagram corresponding to this VHDL code and give it appropriate title that describes its function. Guide: First, rewrite this program in the correct formatting.



$$f_0 := f(A, B, C, '0') := (A \equiv B) \cdot ('0' + (B \neq C)) := (A \equiv B) \cdot ('0' + (B \neq C)) := (A \equiv B) \cdot (B \neq C)$$

$$f_1 := f(A, B, C, '1') := (A \equiv B) \cdot ('1' + (B \neq C)) := (A \equiv B) \cdot '1' := (A \equiv B)$$

Obě nalezené funkce $f_0 := (A \equiv B) \cdot (B \neq C)$ a $f_1 := (A \equiv B)$ zapíšeme jako Karnaughovy mapy

$f_0 =$

	A			
	B			
C	0	0	1	0
	1	0	0	0

$(A \equiv B)$ (blue dashed box)
 $(B \neq C)$ (red dashed box)

$f_1 =$

	A			
	B			
C	1	0	1	0
	1	0	1	0

$(A \equiv B)$ (red dashed box)

5. Mark all logic functions that have another equivalent logic function here :

- $f_1 \leq (A \text{ xor } C) \text{ or } (A \text{ and not } C);$
- $f_2 \leq (B \text{ or } C) \text{ and } (\text{not } A \text{ or } B \text{ or } C);$
- $f_3 \leq ((C \text{ and not } B) \text{ or } (B \text{ and } A));$
- $f_4 \leq (A \text{ or } C) \text{ and } (\text{not } A \text{ or not } C);$
- $f_5 \leq (A \text{ and not } B) \text{ xor } (A \text{ and } C);$
- $f_6 \leq (A \text{ and not } C) \text{ or } (C \text{ and not } A);$

f_1 ☒
 f_2 ☐
 f_3 ☐
 f_4 ☒
 f_5 ☐
 f_6 ☒