

## LSP Exam 2022–01–19

**Course:** B0B35LSP – Logické systémy a procesory | BE5B35LSP – Logic Systems and Processors **University:** CVUT FEL (CVUT) – České vysoké učení technické v Praze | Czech Technical University in Prague **Keywords:** LSP, Exam, Zkouška, 2022–01–19, truth table, De Morgan, RS latch, VHDL

[CN Version](#) | [EN Version](#) | [CZ Version](#)

---

## LSP Exam 2022–01–19

**AI-derived version** – No official answers in the PDF; the following is an inferred walkthrough/notes.

### Exam Info

- Date: 2022–01–19
  - Language: Czech
  - Total: 50 points (Part 1: 25 pts  $\geq$  9 + Part 2: 25 pts  $\geq$  9)
- 

### Q1 – Truth Table (7 pts)

**Task:** Write the truth table for function Y based on the circuit diagram.

**Hint:** You can use Shannon expansion to simplify the computation.

**K-map layout:**

		B				
		A	00	01	11	10
DC	00					
	01					
	11					
	10					

### Q2 – De Morgan's Laws (3 pts)

**Task:** Rewrite logic expression F so that the `not` operator appears only directly in front of variables.

**Original:**

$$F = \text{not} ( (\text{not } A \text{ and not } C) \text{ xor } (A \text{ and } B \text{ and } C) )$$

Approach: 1. Expand XOR:  $A \oplus B = (A \wedge \overline{B}) \vee (\overline{A} \wedge B)$  2. Apply De Morgan:  
 $\overline{A \vee B} = \overline{A} \wedge \overline{B}$

Answer (one possible form):

$$F = ((A \text{ or } C) \text{ and } (\text{not } A \text{ or not } B \text{ or not } C)) \text{ xor} \\ ((\text{not } A \text{ and not } C) \text{ or } (A \text{ and } B \text{ and } C))$$


-- *simplified*:

$$F = (A \text{ and not } B) \text{ or } (\text{not } A \text{ and not } C) \text{ or } (B \text{ and } C)$$

### Q3 – RS Latch Design (10 pts)

Task: Draw an RS latch using NOR gates and NAND gates, and complete the truth tables.

RS latch with NOR gates

 

Truth table (NOR):

S	R	Q	Q̄
0	0	hold Q	hold Q̄
0	1	0	1
1	0	1	0
1	1	0	0 (invalid)

RS latch with NAND gates

Truth table (NAND): active-low inputs

S	R	Q	Q̄
0	0	1	1 (invalid)
0	1	0	1
1	0	1	0
1	1	hold Q	hold Q̄

### Q4 – Moore/Mealy Automaton Definition (5 pts)

Task: Complete the Moore/Mealy automaton definition.

$$M = \langle X, S, Z, \omega, \delta, s_0 \in S \rangle$$

Answer: – **X**: Finite input alphabet – **S**: Finite set of states – **Z**: Finite output alphabet – **δ**: State transition function (Moore:  $S \times X \rightarrow S$ , Mealy:  $S \times X \rightarrow S$ ) – **ω**: Output function (Moore:  $S \rightarrow Z$ , Mealy:  $S \times X \rightarrow Z$ ) – **s<sub>0</sub>**: Initial state

---

### Q5 – VHDL Code Analysis (10 pts)

Task: Analyze the compressed VHDL code and draw the circuit diagram.

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity zzz is port (a : in std_logic; data : in std_logic; q, qn : out std_logic);
architecture rtl of zzz is
    signal qv : std_logic;
begin
    process(a)
    begin
        if rising_edge(a) then
            qv <= not data;
            q <= qv;
        end if;
        qn <= not qv;
    end process;
end;
```

Functional analysis: – Triggered on rising edge of **a** – **qv** stores the inverted **data** – **q** outputs the previous **qv** (one-cycle delay) – **qn** is the inversion of **qv** – This behaves like a 1-bit shift register / pipeline with inversion

---

### Q6 – Full Adder Design (3 pts)

Task: Draw a complete one-bit full adder with inputs A, B, Cin and outputs Y (Sum), Cout.

Equations:

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$
$$\text{Cout} = (A \wedge B) \vee (\text{Cin} \wedge (A \oplus B))$$

---

### Q7 – VHDL Circuit Description (7 pts)

Task: Describe the given circuit diagram in the shortest VHDL code using vector operations.

```
library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity Zahadum is port(
    -- declare ports according to the schematic
);
end entity;
architecture rtl of Zahadum is
begin
```

```
-- use vector operations to simplify  
end architecture rtl;
```

---

### Q8 – Concurrent VHDL Description (5 pts)

Task: Analyze the function of the circuit from Q1 and describe it using simplified concurrent statements (not a direct rewrite of the boolean equations).

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;  
entity yyy is port(a,b,c,d: in std_logic; y: out std_logic); end entity;  
architecture dataflow of yyy is  
begin  
    -- simplified concurrent statements  
end architecture;
```

---

### Q9 – Bonus: SOS Beacon Encoder (10 pts)

Task: Write an SOS signal encoder using advanced VHDL constructs. Signal sequence: 010101000111011101110001010100

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;  
entity SOS is  
    port (clk : in std_logic;  
          X: in std_logic_vector(4 downto 0);  
          Morse, STOP: out std_logic);  
end entity;  
architecture rtl of SOS is  
    constant SOS_PATTERN : std_logic_vector(29 downto 0) :=  
        "010101000111011101110001010100";  
begin  
    process(X)  
        variable idx : integer;  
    begin  
        idx := to_integer(unsigned(X));  
        if idx < 30 then  
            Morse <= SOS_PATTERN(29 - idx);  
            STOP <= '0';  
        else  
            Morse <= '0';  
            STOP <= '1';  
        end if;  
    end process;  
end architecture;
```

---

## Key Topics Summary

### Focus points in this exam

1. Building truth tables
2. Applying De Morgan's laws
3. **RS latch (NOR and NAND implementations)**
4. Moore/Mealy automaton definition
5. VHDL code analysis (shift-register behavior)
6. Full adder design
7. Vector operations in VHDL
8. Circuit simplification / functional reasoning
9. Morse/SOS encoder