


# Logic Systems and Processors

## *cz:Logické systémy a procesory*

Lecturer: Richard Šusta

[richard@susta.cz](mailto:richard@susta.cz), [susta@fel.cvut.cz](mailto:susta@fel.cvut.cz),  
+420 2 2435 7359

 *Version V1.1 - Oct 20, 2024*  
*- corrections of typos*




CTU-FEE in Prague, CR – subject BE5B35LSP
 
# Two Examples




*Both tasks focus on the coding styles appropriate for the description of circuits, which we consider to be more important than the perfect knowledge of the catalog of VHDL or Verilog statements.*




# Create Sign Extension Circuit

# Unsigned / Signed Extensions

 


The **sign extension** is commonly abbreviated as **sext**

 
```
library ieee; use ieee.std_logic_1164.all;  
entity Sext is  
port( se : std_logic;  
      DataIn : in std_logic_vector(7 downto 0);  
      DataOut : out std_logic_vector(15 downto 0));  
end entity;
```



# VHDL -> We describe Architecture - Step 2


Let's draw a schematic...

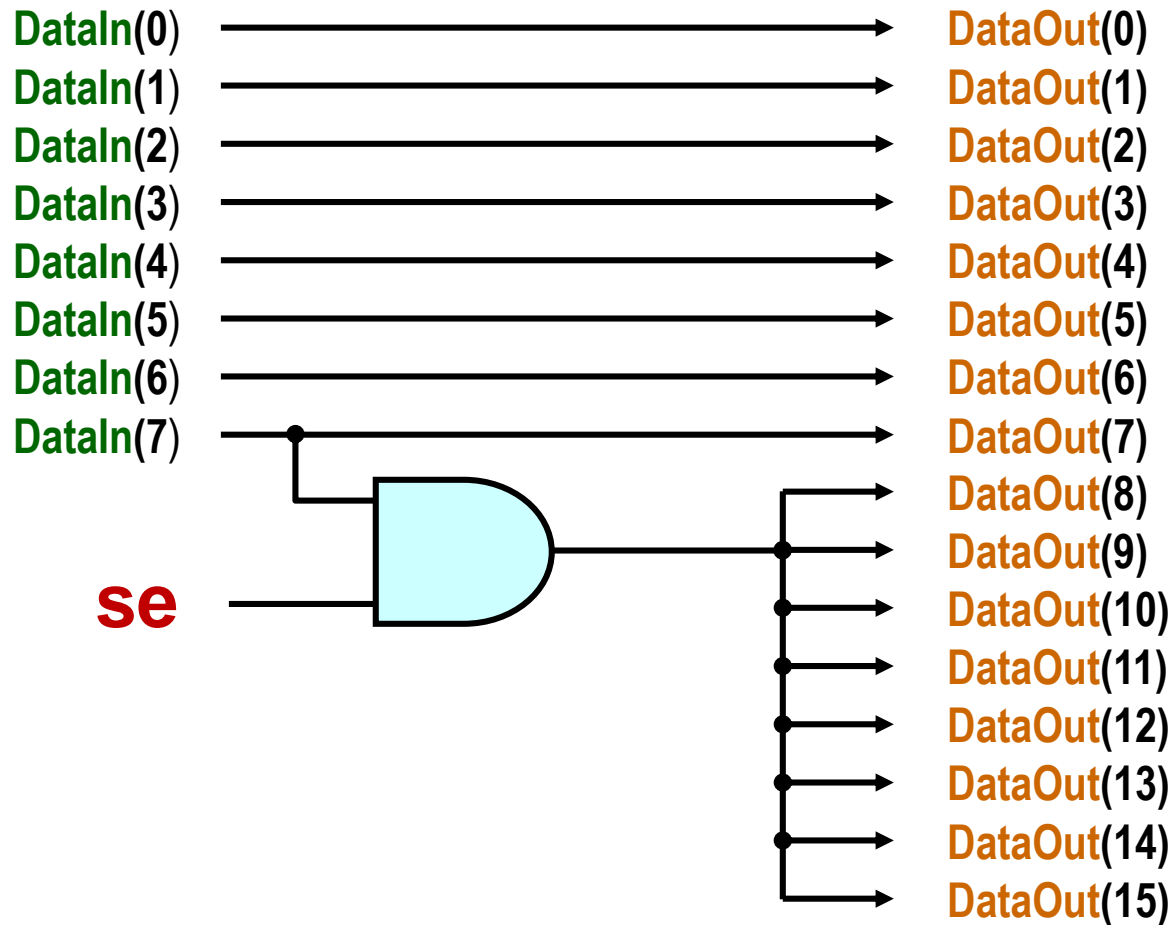

 


A	Q		
0			
1			
2			
3			

# Create Bar Indicator

 
 
```
library ieee; use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity BarIndicator is  
  port  
    ( A : in std_logic_vector(1 downto 0);  
      Q : out std_logic_vector(2 downto 0) );  
end entity;
```



*Let's together discuss several possible VHDL architectures.*



# Overview of Descriptions discussed during the lecture

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity BarIndicator is port ( A : in std_logic_vector(1 downto 0); Q : out std_logic_vector(2 downto 0) );
end entity;
```

*/\* C algorithm is great for compilation to assembler but improper for circuits.*

```
uint bar(uint A) { return (1<<A)-1; }
*/
```

*-- A list of values without hint ☹*

```
architecture rtlMux of BarIndicator is
```

```
begin with A select Q <= "000" when "00", "001" when "01", "011" when "10", "111" when others;
end architecture;
```

*-- We add hint*

```
architecture rtlWhen of BarIndicator is
```

```
signal ua:unsigned(A'RANGE):="00";
```

```
begin ua<=unsigned(A);
```

```
Q(0) <= '1' when ua>=1 else '0';
```

```
Q(1) <= '1' when ua>=2 else '0';
```

```
Q(2) <= '1' when ua>=3 else '0';
```

```
end architecture;
```

*-- The description that can be quickly extended to wider output*

```
architecture rtlGenerate of BarIndicator is
```

```
signal ua:unsigned(A'RANGE):="00";
```

```
begin ua<=unsigned(A); iloop:for i in 0 to 2 generate Q(i) <='1' when i<ua else '0'; end generate;
```

```
end architecture;
```

# LCD Synchronization Generator

---

in VHDL

*Image pixels are nowadays sent to LCDs over serial lines. The RGB colors are in screens stored in capacitors that require periodic refreshing.*

*// its code is a circuit implementation of the C code*

unsigned short int **xcolumn**, **yrow**;

unsigned int **RGBcolor**;

bool **LCD\_DE**, **XEND\_N**, **YEND\_N**;

for (**yrow** = 0; **yrow** < 525; **yrow**++)

{ for (**xcolumn** = 0; **xcolumn** < 1024; **xcolumn**++)

{ **LCD\_DE** = **xcolumn** >= 800 || **yrow** >= 480 ? 0 : 1;

**XEND\_N** = **xcolumn** == 1023 ? 0 : 1;

**YEND\_N** = **yrow** == 524 ? 0 : 1;



**RGBcolor** = **LCDlogic**( **xcolumn**, **yrow** ); *// LCD Task*

}


}



# Sample of the course

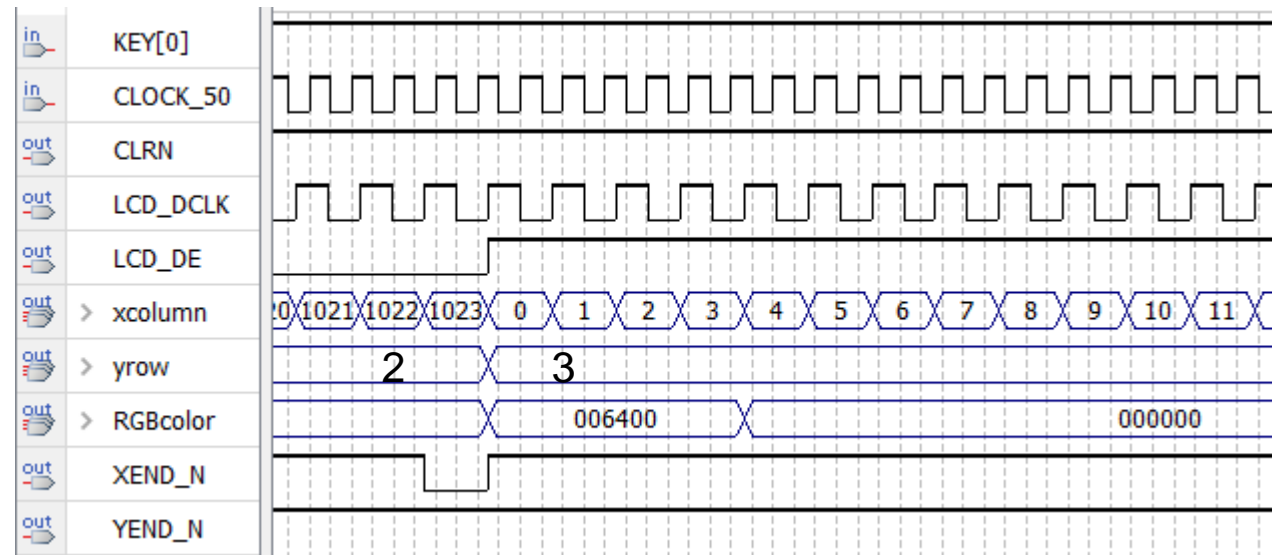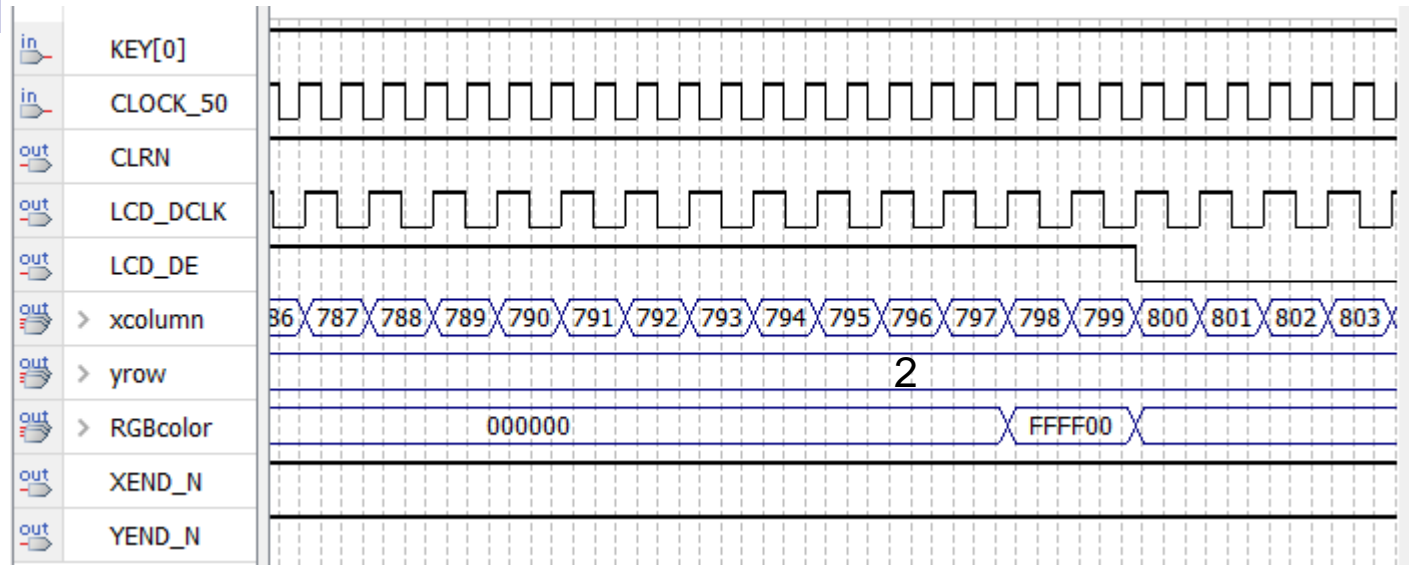


# Diagram 2nd Tasks

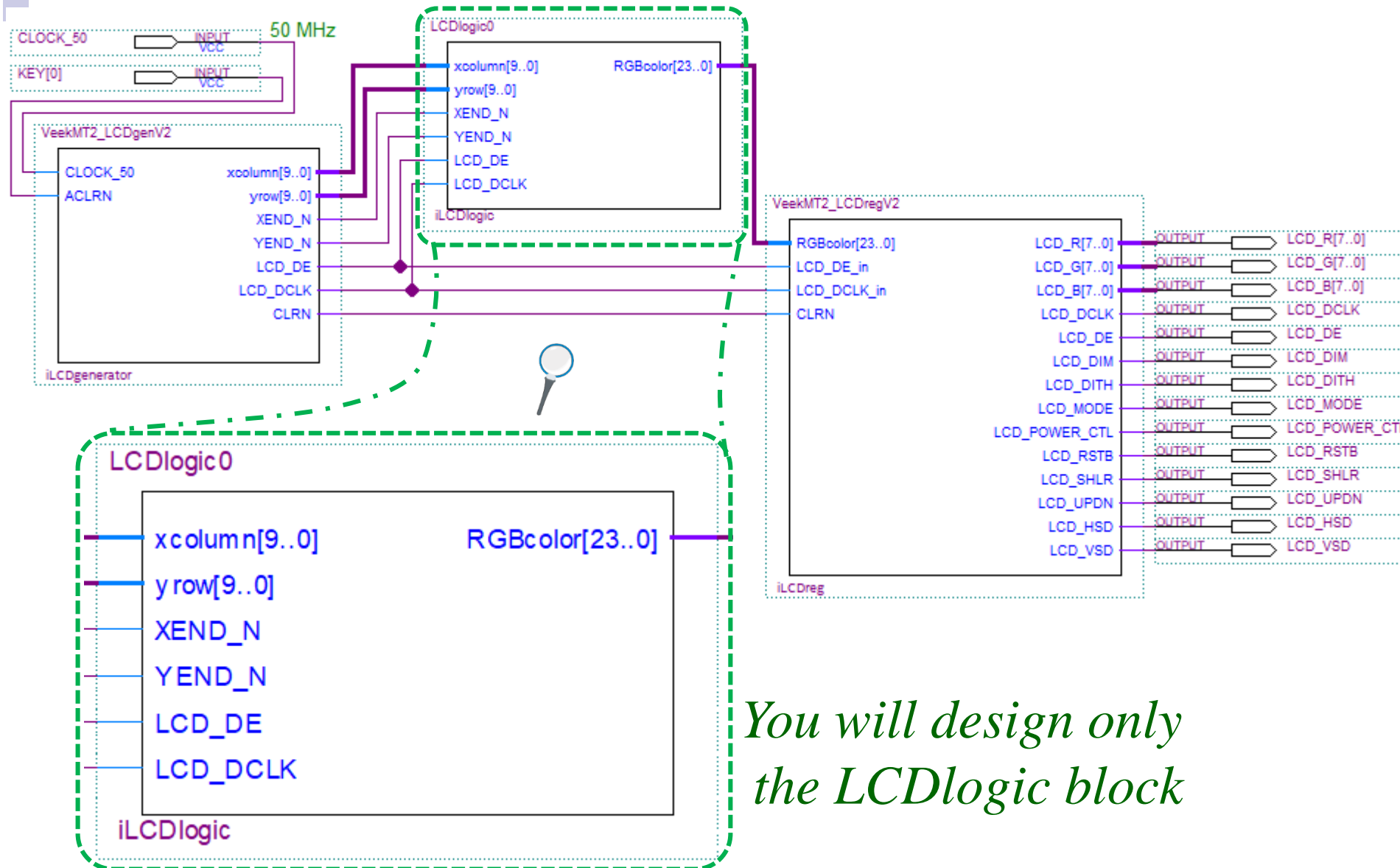

*You will design only  
the LCDlogic block*


```
library ieee, work; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity LCDlogic0 is
port(
  xcolumn, yrow : in unsigned(9 downto 0) := (others => '0'); -- x,y pixel
  XEND_N, YEND_N : in std_logic := '0';    -- max xcolumn/yrow
  LCD_DE : in std_logic := '0';            -- DataEnable control signal of LCD
  LCD_DCLK : in std_logic := '0';          -- LCD data clock, exactly 33 MHz
  RGBcolor : out std_logic_vector(23 downto 0):=(others=>'0') ); -- color data
end;
```

 
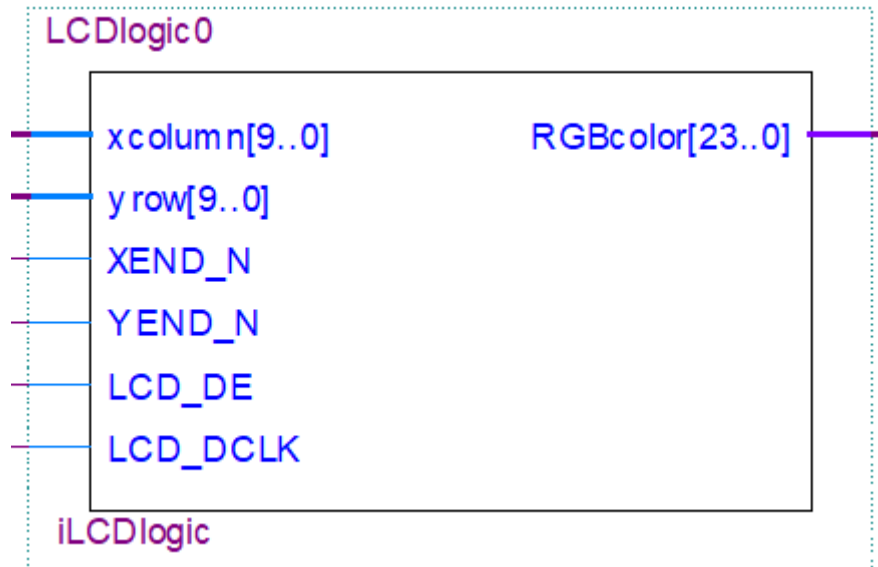
# Let's wrap up handy definitions

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
package LCDpackV2 is
  constant LCD_WIDTH : integer := 800; -- the visible xcolumn axis
  constant LCD_HEIGHT : integer := 480; -- the visible yrow axis
  constant XCOLUMN_MAX : integer := 1023; -- max. xcolumn lies in invisible part)
  constant YROW_MAX : integer := 524; -- max. yrow lies in invisible part)
  subtype xy_t is unsigned(9 downto 0); --xcolumn and yrow coordinates
  constant XY_ZERO : xy_t := (others=>'0');
  subtype RGB_t is std_logic_vector(23 downto 0); --color R:23..16, G:15..8, B:7..0
  -- 16 Windows colors palette
  constant BLACK : RGB_t:=X"000000"; constant BLUE : RGB_t:=X"0000FF";
  constant GREEN : RGB_t:=X"008000"; constant NAVY: RGB_t:=X"000080"; -- plus others
  -- Some useful functions
  function ToRGB(r, g, b:natural) return RGB_t; -- plus others
end package LCDpackV2;
package body LCDpackV2 is /* bodies of functions */
end package body LCDpackV2;
```


```
library ieee, work; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity LCDlogic0 is
  port( xcolumn, yrow : in xy_t := XY_ZERO; -- x,y-coordinates of pixel
        XEND_N, YEND_N : in std_logic := '0'; -- the last xcolumn/yrow
        LCD_DE      : in std_logic := '0';      -- DataEnable LCD
        LCD_DCLK    : in std_logic := '0';      -- LCD data clock, 33 MHz
        RGBcolor    : out RGB_t := BLACK ); -- color assigned to x,y pixel
end;
```






# *Priority task*

## *- visibility in a picture*

 


# Image by Cascade of Multiplexers

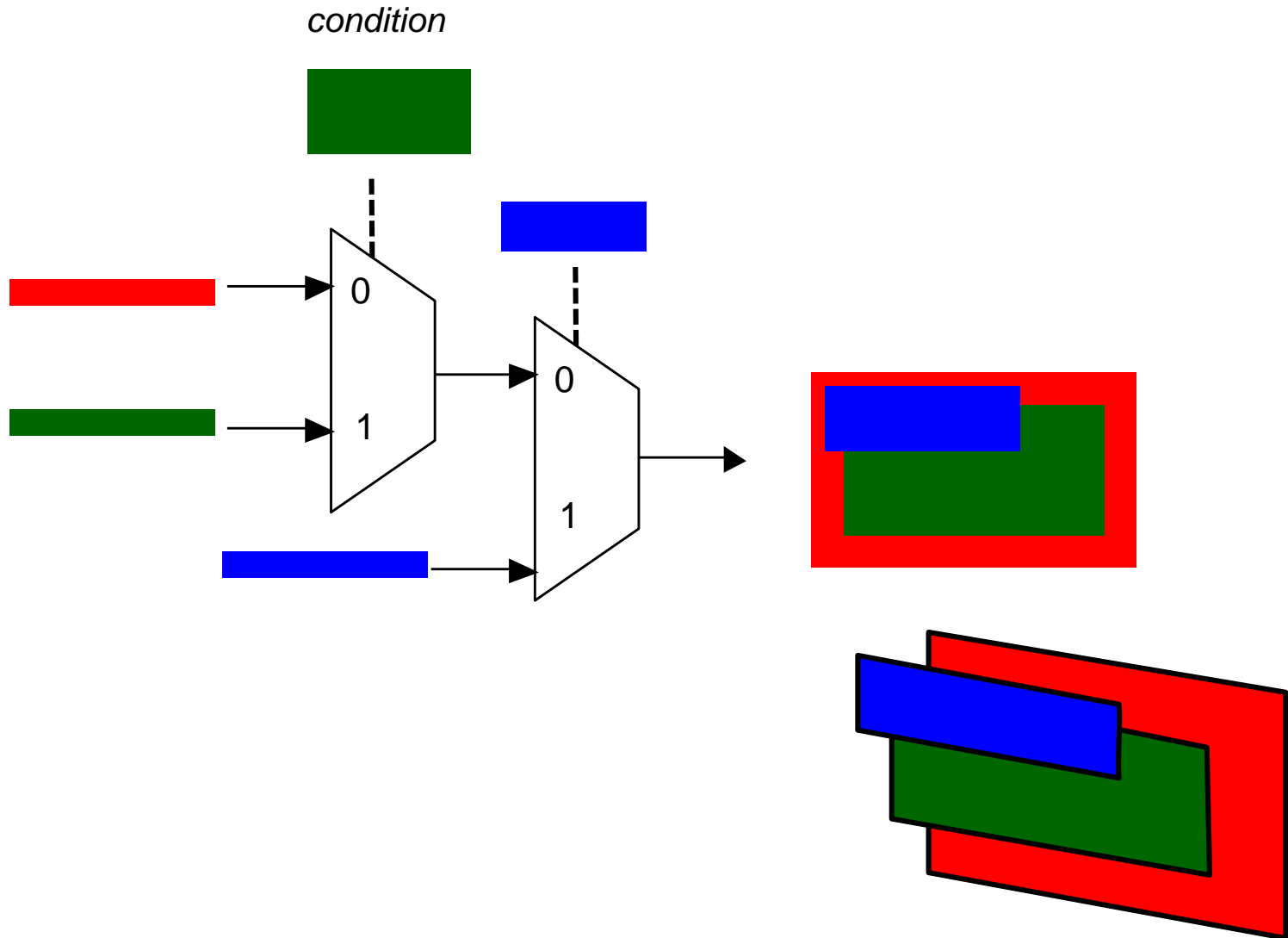

*We create the image below in two ways*

 - 1. In Concurrent Domain**
- 2. In Sequential Domain**



```
library ieee, work; use ieee.std_logic_1164.all;
```

```
use ieee.numeric_std.all; -- num
```

```
use work.LCDpackV2.all; -- our definitions
```

```
entity LCDlecture is
```

```
port( xcolumn, yrow : in xy_t := XY_ZERO; -- x,y-coordinates of pixel
```


```
      XEND_N, YEND_N : in std_logic := '0'; -- the last xcolumn/yrow
```


```
      LCD_DE      : in std_logic := '0'; -- DataEnable LCD
```

```
      LCD_DCLK     : in std_logic := '0'; -- LCD data clock, 33 MHz
```

```
      RGBcolor     : out RGB_t := BLACK); -- color data
```

```
end entity;
```

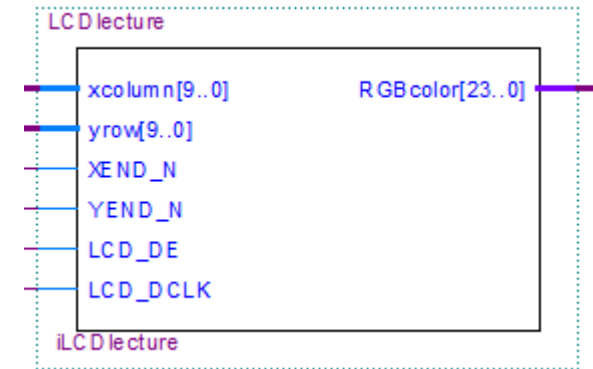

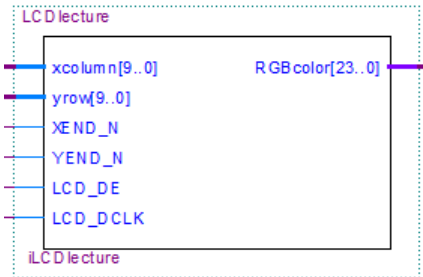


**architecture** concurrentImage **of LCDlecture** is

**begin** -- *architecture*

    RGBcolor <= BLACK **when** LCD\_DE='0' **else** NAVY;

**end architecture**;


# Appearance of Whole LCD Frame

 


*The red lines in the Viewer only highlight the last row, column. Their pixels have black colors.*
 
# Implementation in Circuit

```
RGBcolor <= X "000000" when LCD_DE='0'  
             --BLACK  
else X "000080"; -- NAVY
```



# Modifying to Two XOR Squares

 



```
architecture concurrentImage of LCDlecture is
  signal x, y : integer range 0 to 2**xy_t'LENGTH-1:=0;
  constant LXC:integer := LCD_WIDTH/2; -- visible xcolumn center
  constant LYC:integer := LCD_HEIGHT/2; -- visible yrow center
begin

  x<=to_integer(xcolumn); y<=to_integer(yrow);


  RGBcolor <= BLACK when LCD_DE='0' else
    GREEN when x<LXC xor y<LYC else
      NAVY;


end architecture;
```



```

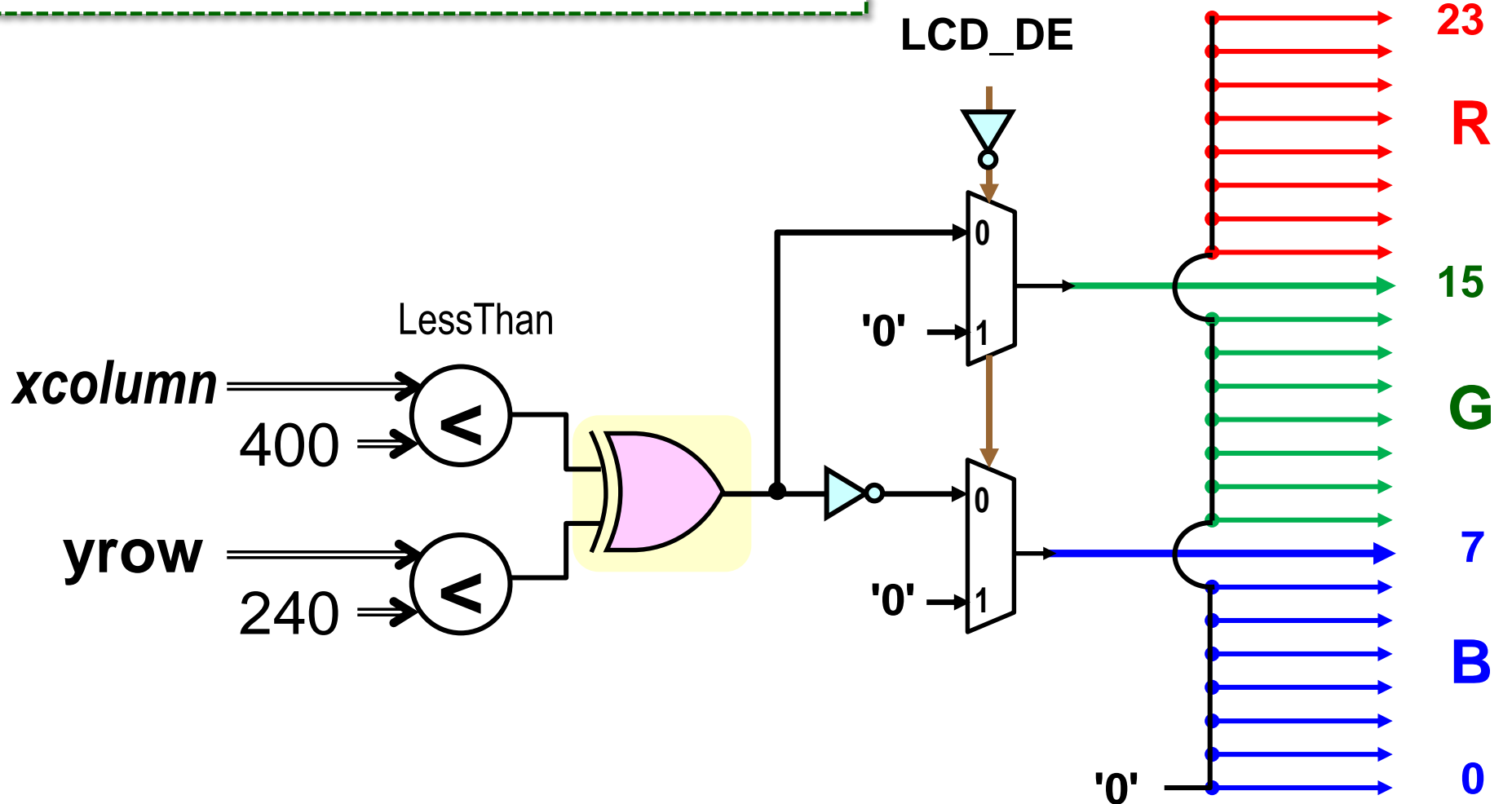RGBcolor <= BLACK when LCD_DE='0' else
  GREEN when x<LXC xor y<LYC else
  NAVY;
  
```



 

# Two Squares plus Circle


```
architecture concurrentImage of LCDlecture is
  signal x,y : integer range 0 to 2**xy_t'LENGTH-1:=0;
  constant LXC:integer := LCD_WIDTH/2; -- visible xcolumn center
  constant LYC:integer := LCD_HEIGHT/2; -- visible yrow center
begin

  x<=to_integer(xcolumn); y<=to_integer(yrow);

  RGBcolor <= BLACK when LCD_DE='0' else
    RED when (x-LXC)**2+(y-LYC)**2<128**2 else
    GREEN when x<LXC xor y<LYC else
    NAVY;

end architecture;
```

# Implementation in the circuit

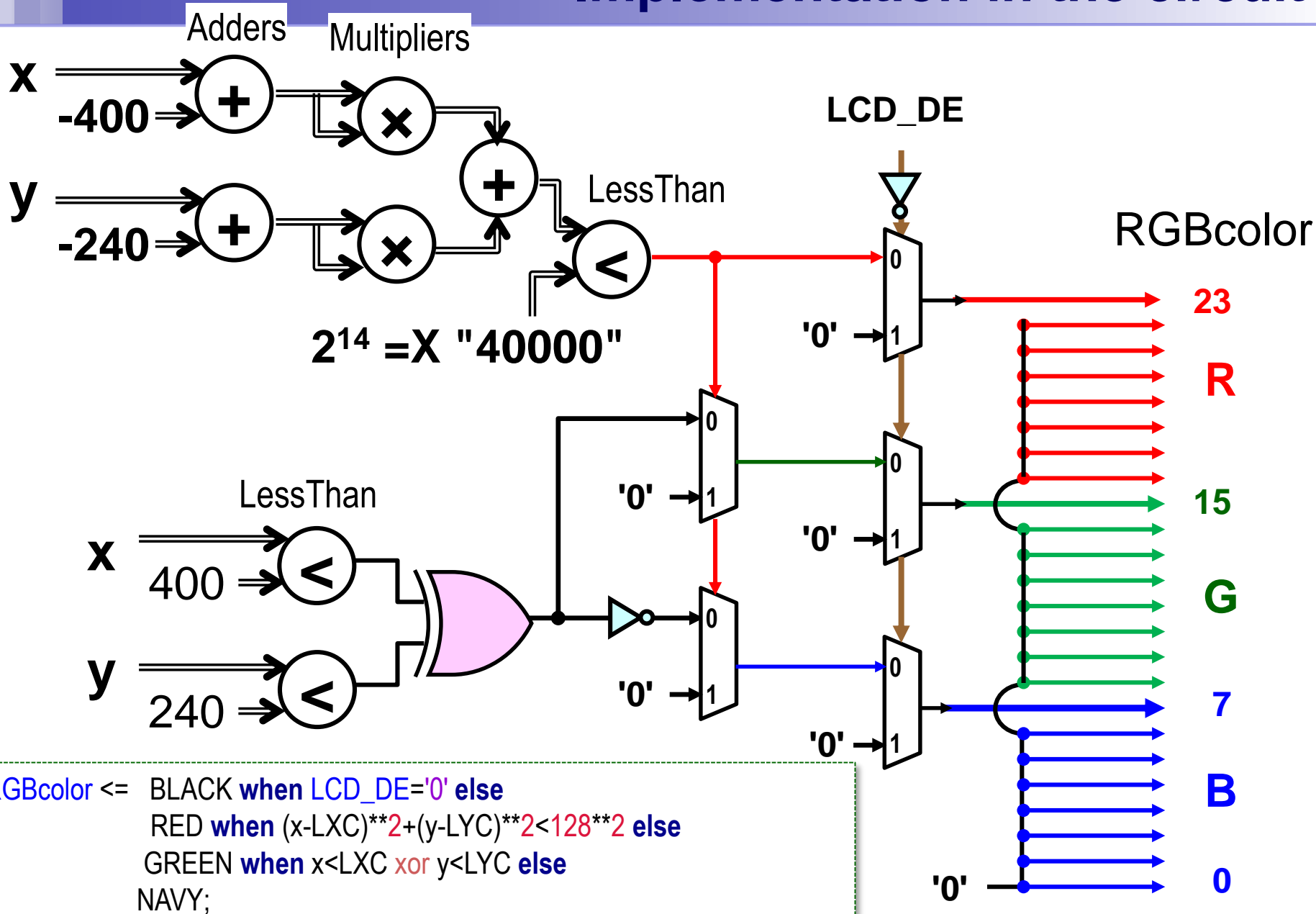

```

RGBcolor <= BLACK when LCD_DE='0' else
  RED when (x-LXC)**2+(y-LYC)**2<128**2 else
  GREEN when x<LXC xor y<LYC else
  NAVY;
    
```

# Arithmetic in Circuits


---

How is it done?


Logic Circuits textbook, chapter 6.

# Multiplication by a Power of 2


$x * 2^1$

 


$x * 2^3$

 


# Division by Powers of 2 - Wires

 


$\text{unsigned}(x) / 2^1$

 


$\text{signed}(x) / 2^1$

 


$x \bmod 2^1$

 

$\text{unsigned}(x) / 2^3$

 

$\text{signed}(x) / 2^3$

 


$x \bmod 2^3$





 
# Multiplication by the Sum of Powers of 2




a binary complement of  $x$

 




*Quartus multiplies by  $2^N - 1$  sometimes*

 - *by using an adder...*
- *by a multiplier*


   
# Combinational Arithmetic Circuits





*By minimizing the SoP or PoS, it is appropriate to design:*



*and other types*  $<=$   $=$   $/=$   $>=$

$\neq$  is  $!=$  in C,  $\sim=$  in Matlab,  $<>$  in Basic or Pascal,  
but  $/=$  in VHDL

    
If a constant  $K \mid 2^N$ , i.e.,  $K$  is divisible by a  $N$  power of 2, where integer  $N > 0$ , then  $K$  has  **$N$  lower bits = '0'**.  
In that case,  $x < K$  and  $x \leq K$  comparators are smaller because they can test only the upper non-zero bits.



# Operation with two general numbers x,y

*SoP and PoS minimization give too complex results for the following circuits. Their decompositions are necessary:*



➤ Comparators

 


*and comparisons*

$\geq$   $>$   $\leq$


➤ Adders and subtractors

  

➤ Multipliers

 

 
Divisions by the constants  $K \neq 2^N$  can be approximated




*Note: In LCD, xcolumn and yrow coordinates can be divided by any number with the aid of counters, see [Task\\_LCDbackground.pdf](#) page 16.*

**Do not use**  
the direct divisions by  
a general number or by constant  $\neq 2^N$   
because they have extremely  
complex circuit implementations

!!!

 

# Use LSP tools Checker of Projects

 

Checker of VEEK-MT2 Project (Alpha version) - C:\SPS2024L\LSP\_WeekMT2\_TestWarningMessages\_Q20\Week...

File

ToDo in Quartus Project | Log of Activities | Adjust VWF

Type	Code	Number of Descriptions	Occurrences in Items
Disallowed	WARNING_DIVIDE	4	The project creates disallowed divider
Disallowed	WARNING_LOOP	2	Info (278004): Inferred divider/modulo megafunction ("lpm_divide") from the following logic: "LCDlogic1.inst Mod0" File: C:/SPS/LSP_WeekMT2
Disallowed	WARNING_LATCH	2	_TestWarningMessages_Q20/LCDlogic1.vhd Line: 148
Disallowed	WARNING_SENSITIVITY	3	Info (12130): Elaborated megafunction instantiation "LCDlogic1.inst lpm_divide:Mod0" File: C:/SPS/LSP_WeekMT2_TestWarningMessages_Q20/LCDlogic1.vhd Line: 148
			Info (12133): Instantiated megafunction "LCDlogic1.inst lpm_divide:Mod0" with the following parameter: File: C:/SPS/LSP_WeekMT2
			_TestWarningMessages_Q20/LCDlogic1.vhd Line: 148

< >


The code created an disallowed division circuit.  
If you need more information than you see here,  
search for 'lpm\_divide' in Quartus compiler messages.

ToDo

# Repeated patterns

---

by divisions and modulo

 



**architecture** concurrentImage of LCDlecture is

**signal** x,y : integer range 0 to 2\*\*xy\_t'LENGTH-1:=0;

**constant** LXC:integer := LCD\_WIDTH/2; -- visible xcolumn center

**constant** LYC:integer := LCD\_HEIGHT/2; -- visible yrow center

**constant** BLOODRED:RGB\_t:=x"660000"; -- web safe color

**signal** myRed:RGB\_t:=BLACK;

**begin**

x<=to\_integer(xcolumn); y<=to\_integer(yrow);

myRed<= RED **when** (xcolumn(3) xor yrow(3)) **else** BLOODRED;

RGBcolor <= BLACK **when** LCD\_DE='0' **else**

myRED **when** (x-LXC)\*\*2+(y-LYC)\*\*2<128\*\*2 **else**

GREEN **when** x<LXC xor y<LYC **else**

NAVY;

**end architecture**;


Alternative:

myRed<= RED **when** ((x/8) mod 2)=0 xor ((y/8) mod 2)=0 **else** BLOODRED;




# Real Implementation in the Circuit

LCDlectureLCDlecture

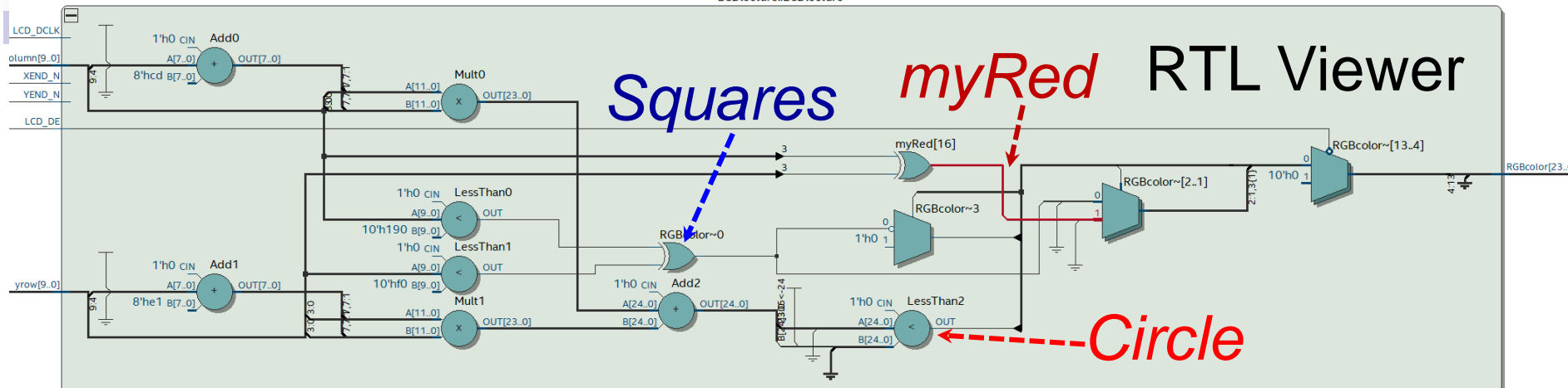

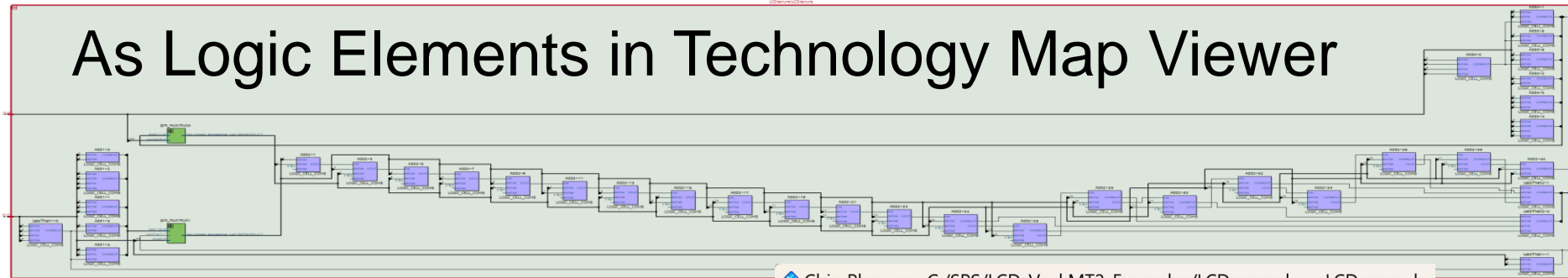
As Logic Elements in Technology Map Viewer



Chip Planner - C:/SPS/LCD\_VeekMT2\_Examples/LCDexamples - LCDexamples

File Edit View Tools Window Help

In Chip Planner

 



# Dataflow Limits

- Their conditions are growing in the case of nested rules.
  - The concurrent **select with** or **when else** statements cannot contain inserted statements, only expressions. So, we must prepare values in auxiliary signals.
- The sequential domain allows nested statements and also overwriting values of variables. The compiler transforms its code into concurrent statements by introducing auxiliary signals.





## Sequential VHDL domain

is surrounded by keywords:

- ➡ **function ... end function;**
- ➡ **procedure ... end procedure;**
- ➡ **process ... end process;**
- ➡ It also includes the passive process that starts with the optional begin keyword inside an entity declaration to its **end**.

# Three types of "concurrent" commands we are familiar with them from the concurrent domain.

**<=**

**with-select-when**

**when-else**

*Visit For*

Concurrent assignments

Selective assignments


Conditional assignments

*implemented using*

logic circuit

multiplexers

multiplexer cascades 2:1

 


**Architecture**

**Concurrent Statements**

**Structural**

port map  
generic map

**Process**  
**Sequential Statements**

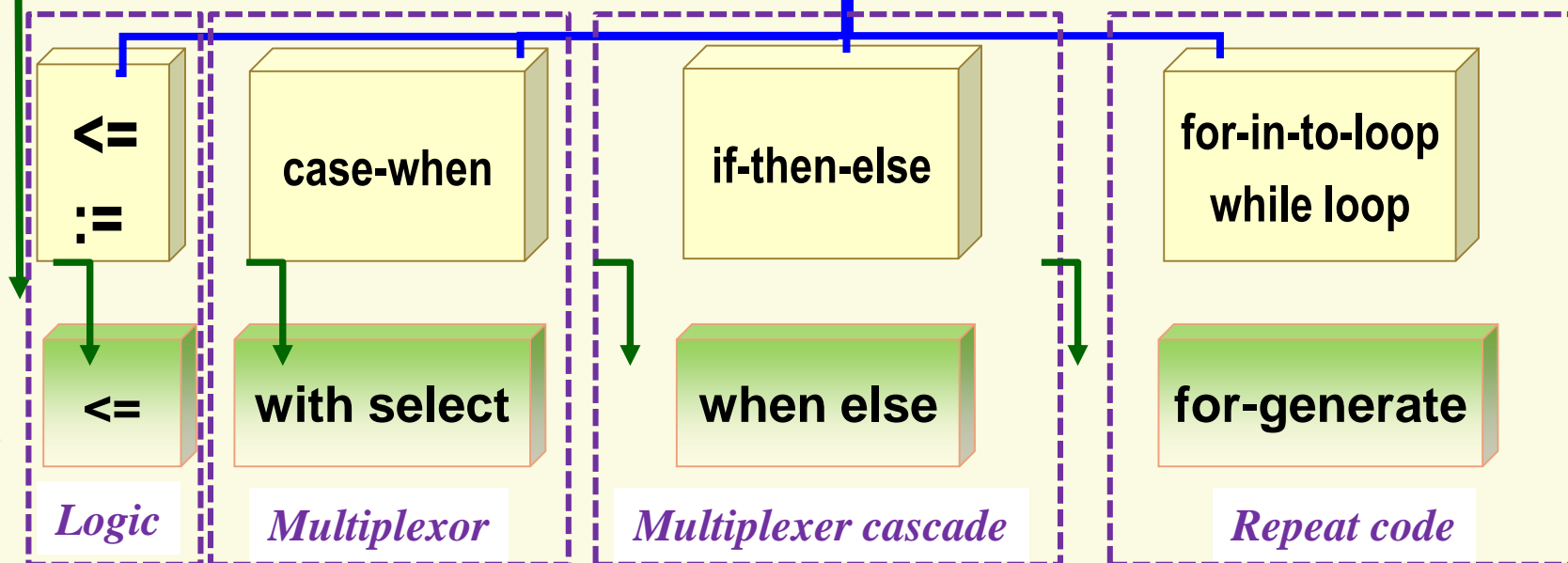

# VHDL Process

*We'll start with  
its application*



# Sequential domain: Variables

- In the sequential domain, we cannot define signals, only variables, but by their declarations are similar to signals:

**variable** variable-name, variable-name , . . . . : **data-type**;

- New values are assigned to variables by **blocking** assignments:

variable-name **:=** value-expression;

- Signals represent connections by wires and need **non-blocking** concurrent assignments:

signal-name **<=** signal-expression;

*The reasons for this will be the topic of the following lecture.*

- In **VHDL 2008**, we can also use "**concurrent statements**" **when-else** and **with-select** in the sequential domain.

**But the Quartus Lite versions do not allow them here.**



**architecture** sequantialImage **of LCDlecture is**

**constant** LXC:integer := LCD\_WIDTH/2; -- visible xcolumn center

**constant** LYC:integer := LCD\_HEIGHT/2; -- visible yrow center

**constant** BLOODRED:RGB\_t:=x"660000"; -- web safe color

**begin**

**process**(LCD\_DE, xcolumn, yrow)

**variable** rgb: RGB\_t:=BLACK;

**variable** x,y : integer range 0 to 2\*\*xy\_t'LENGTH-1:=0;

**begin**

-- Next slides


**end process;**

**end architecture;**
 
# Seq. domain allows overwriting

```
process(LCD_DE, xcolumn, yrow)
  variable rgb:RGB_t:=BLACK;
  variable x,y : integer range 0 to 2**xy_t'LENGTH-1:=0;
begin
  x:=to_integer(xcolumn); y:=to_integer(yrow);
  rgb:=NAVY;
  if x<LXC xor y<LYC then
    rgb:=GREEN;  end if;
  if (x-LXC)**2+(y-LYC)**2<128**2 then
    rgb:=RED;    end if;
  if not LCD_DE then
    rgb:=BLACK;  end if;
  RGBcolor<=rgb;
end process;
end architecture;
```

*The VHDL compiler rewrites the code to its concurrent version and removes all forbidden overwriting of values.*



# Process Format

---

**[label:] process (*sensitivity list*)**

***declarations***

**begin**

***sequential statements***

**end process [label];**

-- *Label* is an optional parameter.


*However, we can see it in the simulation,  
in which it serves as a landmark.*

- A *process* is a **VHDL construct that contains a set of actions to be executed sequentially**. These actions are known as *sequential statements*. **The process itself is a concurrent statement**. It can be interpreted as a circuit part enclosed inside a black box whose behavior is described by the sequential statements. We may or may not be able to construct physical hardware that exhibits the desired behavior.
- The **sensitivity-list is a list of signals to which the process responds (i.e., is “sensitive to”)**. The **declarations part consists of various declarations that are local to the process**.
- The list of sensitivities in the process are not formal parameters, but hints to the compiler as to what inputs will cause the outputs to change.
- Whereas the appearance of a VHDL process is like a function or procedure of a traditional programming language, the behavior of the process is very different. A VHDL process is not invoked (or called) by another routine. It acts like a circuit part, which is either active (known as *activated*) or inactive (*known as suspended*).
- *In simulations, a VHDL process is activated when* a signal in the sensitivity list changes its value, like a circuit responding to an input signal. Once a process is activated, its statements will be executed sequentially until the end of the process. The process is then suspended until the next change of signal.

[VHDL 1993 Reference, IEEE]

# Process Declarations

---

- **type**, **subtype**, **constant** and **variable** 
- **function**, **procedure** - sequential codes of circuit parts for local use. They are not called in the circuit, but inserted by inline expansion technique.
- **use** keyword allows adding additional libraries locally available only here, if they are needed.

❖ No **signal** or **component** declarations are allowed here.





- A **variable** describes the abstract behavior of the system.
- We can declare variables in a process, function or procedure. We are not allowed to declare signals there, they belong only to the architecture.
- Variables are always local, i.e. they cannot be referenced from elsewhere than from the part that declared them.
- *Note: Shared variables were introduced in VHDL 93 for simulation purposes. Although they can be declared outside the process, they are difficult to implement in hardware. As a rule, they are circumvented by complex automatic conversions, which sometimes have unpredictable results.*
- **Shared variables are strictly prohibited in the circuit synthesis portions of LSP projects.** The rule is also applied by professional development companies.


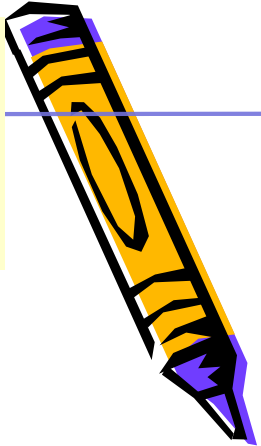
# Beware of signals in sequential domains



- The signal types always emulate the inertial delay of actual wires by postponing updates of their values.
  - If we improperly use a signal, we have unwanted side effects. We will discuss this topic in our lectures.
  - In processes, we should always prefer **variables** that behave here similarly to classic programming, e.g., C language.
  - We freely read values of signals but **assign each signal at most only once**, usually at the end of a process.
- 
- 




**Task\_LCDbackground - pg. 10**


 
# If-then-else can be nested

```
architecture sequentialImage of LCDlecture is
  constant LXC:integer := LCD_WIDTH/2; -- visible xcolumn center
  constant LYC:integer := LCD_HEIGHT/2; -- visible yrow center
  constant BLOODRED:RGB_t:=x"660000"; -- web safe color
begin
  process(LCD_DE, xcolumn, yrow)
    variable rgb:RGB_t:=BLACK;
    variable x,y : integer range 0 to 2**xy_t'LENGTH-1:=0;
  begin
    x:=to_integer(xcolumn); y:=to_integer(yrow);
    rgb:=NAVY;
    if x<LXC xor y<LYC then rgb:=GREEN; end if;
    if (x-LXC)**2+(y-LYC)**2<128**2 then
      if (xcolumn(3) xor yrow(3)) then rgb:=RED; else rgb:=BLOODRED; end if;
    end if;
    if not LCD_DE then rgb:=BLACK; end if;
    RGBcolor<=rgb;
  end process;
end architecture;
```



```
process(LCD_DE, xcolumn, yrow)
  variable rgb:RGB_t:=BLACK;
  variable x,y : integer range 0 to 2**xy_t'LENGTH-1:=0;
begin
  x:=to_integer(xcolumn); y:=to_integer(yrow);
  if not LCD_DE then rgb:=BLACK;
  elsif (x-LXC)**2+(y-LYC)**2<128**2 then
    if (xcolumn(3) xor yrow(3)) then rgb:=RED; else rgb:=BLOODRED; end if;
  elsif x<LXC xor y<LYC then rgb:=GREEN;
  else rgb:=NAVY;
  end if;
  RGBcolor<=rgb;
end process;
```

# IF-ELSIF versus more IFs

```
process(LCD_DE, xcolumn, yrow)
  variable rgb:RGB_t:=BLACK;
  variable x,y : integer
    range 0 to 2**xy_t'LENGTH-1:=0;
  begin
    x:=to_integer(xcolumn); y:=to_integer(yrow);
    if not LCD_DE then rgb:=BLACK;
    elsif (x-LXC)**2+(y-LYC)**2<128**2 then
      if (xcolumn(3) xor yrow(3)) then
        rgb:=RED; else rgb:=BLOODRED;
      end if;
    elsif x<LXC xor y<LYC then rgb:=GREEN;
    else rgb:=NAVY;
    end if;
    RGBcolor<=rgb;
  end process;
```

```
process(LCD_DE, xcolumn, yrow)
  variable rgb:RGB_t:=BLACK;
  variable x,y : integer
    range 0 to 2**xy_t'LENGTH-1:=0;
  begin
    x:=to_integer(xcolumn); y:=to_integer(yrow);
    rgb:=NAVY;
    if x<LXC xor y<LYC then rgb:=GREEN; end if;
    if (x-LXC)**2+(y-LYC)**2<128**2 then
      if (xcolumn(3) xor yrow(3)) then
        rgb:=RED; else rgb:=BLOODRED;
      end if;
    end if;
    if not LCD_DE then rgb:=BLACK; end if;
    RGBcolor<=rgb;
  end process;
```

- Circuits with more **if statements** do not have more complex implementations.
- The **if then elsif else** chains specify that the RTL meta-schemas of the first compile-pass contain cascade of two-input multiplexers starting with the **highest priority** condition.
- More **if then** statements begin with the **lowest priority** condition, and the compiler also transforms them to the chain of two-input multiplexors, usually in the first pass, otherwise in the next one.
- The both methods lead to the optimal circuit. If someone is more familiar with multiple IFs, let them create that way.