

LSP Exam 2022–01–24

Course: B0B35LSP – Logické systémy a procesory | BE5B35LSP – Logic Systems and Processors **University:** CVUT FEL (CVUT) – České vysoké učení technické v Praze | Czech Technical University in Prague **Keywords:** LSP, Exam, Zkouška, 2022–01–24, Shannon expansion, RS latch, VHDL

[CN Version](#) | [EN Version](#) | [CZ Version](#)

LSP Exam 2022–01–24 (English edition)

AI-derived version – No official answers in the PDF; the following is an inferred walkthrough/notes.

Exam Info

- Date: 2022–01–24
 - Language: Czech / English
 - Total: 50 points (Part 1: 25 pts > 8 + Part 2: 25 pts > 8)
-


Q1 – Shannon Expansion (6 pts)

Task: Decompose the circuit functions $X, Y = f(A, B, C)$ using Shannon expansion into:

$$X, Y = (\overline{C} \wedge f_0(A, B)) \vee (C \wedge f_1(A, B))$$

Write f_0 and f_1 as Karnaugh maps.

For both X and Y draw two K-maps:

 

Q2 – Signed/Unsigned Arithmetic (4 pts)

Task: Perform $96+97+98+99$ on an 8-bit adder. What is the decimal value of the result as an 8-bit number?


Computation: – $96+97+98+99 = 390$ – $390 \bmod 256 = 134$

Answer: – a) unsigned: 134 – b) signed (two's complement): $134 - 256 = -122$

Q3 – 1:4 Demultiplexer Design (10 pts)

Task: Draw the logic circuit diagram of a 1:4 demultiplexer.

Symbol:

 

Logic equations:

$x0 = \text{Data and (not } y1) \text{ and (not } y0)$

$x1 = \text{Data and (not } y1) \text{ and } y0$

$x2 = \text{Data and } y1 \text{ and (not } y0)$

$x3 = \text{Data and } y1 \text{ and } y0$

Q4 – RS Latch Simulation (5 pts)

Task: Given inputs A, B, C values at times $t0$ – $t4$, write the values of outputs X and Y.

Input sequence:

A	=	1		0		1		0		1
B	=	0		0		1		0		0
C	=	0		1		0		0		0
		$t0$		$t1$		$t2$		$t3$		$t4$

Q5 – VHDL RTL Analysis (10 pts)

Task: Draw the RTL view of the following VHDL code and correctly name the circuit.

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity XXX is port(a, b : in std_logic; c : out std_logic); end entity;
architecture beh of XXX is
```

```

begin
  process (a,b)
    variable d:std_logic:='0';
    variable e:integer range 0 to 25:=0;
  begin
    if b='0' then
      e:=0; d:='0';
    elsif rising_edge(a) then
      if e<25 then
        e:=e+1;
      else
        e:=0; d:=not d;
      end if;
    end if;
    c<=d;
  end process;
end architecture;

```

Functional analysis: – b='0' is an asynchronous reset – Triggered on rising edge of a – After counting up to 25, the output toggles – **Name: divide-by-26 frequency divider**

RTL view contains: – 5-bit counter (0–25) – comparator(s) (e < 25, e = 25) – D flip-flop to store d – async reset logic

Q6 – Demultiplexer VHDL Description (5 pts)

Task: Describe the demultiplexer from Q3 in the simplest way.

```


library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity yyy is
  port(Data: in std_logic;
        y: in std_logic_vector(1 downto 0);
        x: out std_logic_vector(3 downto 0));
end entity;
architecture dataflow of yyy is
begin
  x <= (others => '0');
  x(to_integer(unsigned(y))) <= Data;
end architecture;

```

Q7 – Divide-by-16 Counter Design (5 pts)

Task: Add the minimum number of components to an incomplete circuit to create a synchronous divide-by-16 of CLK (using a +1 adder).

Idea:

 

- 4-bit counter (0–15 loop)
 - DIV16 = Q3 (MSB)
 - Toggles every 16 clock cycles
-

Q8 – Motor Control Circuit (5 pts)

Task: Design a circuit: press a double-pole button once to start the motor, press again to stop it. After power-up the motor must be OFF.

Key components: – D flip-flop – asynchronous clear (power-up reset) – relay driver – de-bounce circuit

Q9 – Bonus: Edge Detector (10 pts)

Task: When input D changes value, output Y shall be '1' for one clock cycle. RESET is synchronous.

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity Edges is
  port (clk, Reset, D : in std_logic; Y: out std_logic);
end entity;
architecture rtl of Edges is
  signal D_prev : std_logic := '0';
begin
  process(clk)
  begin
    if rising_edge(clk) then
      if Reset = '1' then
        D_prev <= '0';
        Y <= '0';
      else
        if D /= D_prev then
          Y <= '1';
        else
          Y <= '0';
        end if;
        D_prev <= D;
      end if;
    end if;
  end process;
end architecture;
```

```
end process;  
end architecture;
```

Key Topics Summary

Focus points in this exam

1. Shannon expansion (two outputs)
2. **8-bit signed/unsigned arithmetic** (important: 390 mod 256)
3. **1:4 demultiplexer design**
4. RS latch simulation
5. **VHDL RTL analysis** (divider recognition)
6. Demultiplexer VHDL description
7. Divide-by-16 design
8. Motor control circuit
9. Edge detector design

Important formulas

- 8-bit unsigned range: 0–255
- 8-bit signed range: –128 to 127
- overflow handling: $\text{result mod } 2^n$