



Exam 30 January 30.1.15, questions and answers

Logic Systems And Processors (České Vysoké Učení Technické v Praze)



Scan to open on Studocu

Surname and first name:.....

Exam 30.1.2015 - write here only your answers

1. Rewrite the logical expression F so that not operators were only before variables - check your solution in K-map!

$F = \text{not} ((A \text{ or } \text{not } B \text{ or } \text{not } C) \text{ or } ((A \text{ or } B) \text{ and } \text{not} (A \text{ or } \text{not } C)))$



F =

2. Inputs A, B, C have values shown in the figure in times t_0, t_1, t_2, t_3 . Write values of X and Y outputs. Assume that the intervals between changes in the inputs are so long so we can neglect delays of gates.


A = ..0..|..1..|..1..|..1..|

t_0 ..|.. t_1 ..|.. t_2 ..|.. t_3 ..|..

B = ..0..|..0..|..0..|..1..|



t_0 ..|.. t_1 ..|.. t_2 ..|.. t_3 ..|..

C = ..1..|..1..|..0..|..0..|

 

Q =|.....|.....|.....|
 t_0 ..|.. t_1 ..|.. t_2 ..|.. t_3 ..|..

  3. Function $Q=f(A,B,C, Q)$ from question 2, decompose into $X=(\text{not } X \text{ and } f_0(A, B,C))$ or $(X \text{ and } f_1(A,B,C))$ with the aid of Shannon's expansion. Write f_0 and f_1 functions as Karnaugh maps:



4. What decimal value is 10-bit number 10 0000 1111 if we interpret it as an integer


a) unsigned b) signed in two's-complement.....

5. Mark all logic functions that have another equivalent logic function here :






- f1<=(A xor C) or (A and not C);
f2<=(B or C) and (not A or B or C);
f3<=((C and not B) or (B and A));
f4<=(A or C) and (not A or not C);
f5<=(A and not B) xor (A and C);
f6<=(A and not C) or (C and not A);

f1 ☐
f2 ☐
f3 ☐
f4 ☐
f5 ☐
f6 ☐

 5. Draw R-S latch only from NOR gates and the same only from NAND gates



7. Add gates and wires to the unfinished diagram below, you do not need to use everything in picture, to create a asynchronous divider by 18 of CLK clock signal with asynchronous reset ACLRN.

     VCC
TINPUT
CLKOUTPUT
DIV18

12




8. An editor *ask you if you could analyze wrong formatted VHDL code:*

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity test20140214 is port (a, b, c, d : in std_logic; e : out std_logic); end;
architecture rtl of test20140214 is begin
  process(a, b) variable z:std_logic_vector(0 to 3); begin
    if b = '0' then z:=(others=>'0'); elsif rising_edge(a) then
      if c='1' then z:=d & z(0 to 2); else z:=z(3) & z(0 to 2); end if; end if; e<=z(3); end process; end rtl;
```

Draw a logical circuit diagram corresponding to this VHDL code and give it appropriate title that describes its function. Guide: First, rewrite this program in the correct formatting.

12



 

$$f_0 := f(A, B, C, '0') := (A \equiv B) \cdot ('0' + (B \neq C)) := (A \equiv B) \cdot ('0' + (B \neq C)) := (A \equiv B) \cdot (B \neq C)$$

$$f_1 := f(A, B, C, '1') := (A \equiv B) \cdot ('1' + (B \neq C)) := (A \equiv B) \cdot '1' := (A \equiv B)$$

Obě nalezené funkce $f_0 := (A \equiv B) \cdot (B \neq C)$ a $f_1 := (A \equiv B)$ zapíšeme jako Karnoughovy mapy

$f_0 =$

	A			
	B			
C	0	0	1	0
	1	0	0	0

(B ≠ C)

(A ≡ B)

$f_1 =$

	A			
	B			
C	1	0	1	0
	1	0	1	0

(A ≡ B)

5. Mark all logic functions that have another equivalent logic function here :

- $f_1 \leq (A \text{ xor } C) \text{ or } (A \text{ and not } C);$
- $f_2 \leq (B \text{ or } C) \text{ and } (\text{not } A \text{ or } B \text{ or } C);$
- $f_3 \leq ((C \text{ and not } B) \text{ or } (B \text{ and } A));$
- $f_4 \leq (A \text{ or } C) \text{ and } (\text{not } A \text{ or not } C);$
- $f_5 \leq (A \text{ and not } B) \text{ xor } (A \text{ and } C);$
- $f_6 \leq (A \text{ and not } C) \text{ or } (C \text{ and not } A);$

f_1 ☒
 f_2 ☐
 f_3 ☐
 f_4 ☒
 f_5 ☐
 f_6 ☒