

LSP 考试 2025 年 6 月 9 日

考试信息

- 日期: 2025 年 6 月 9 日
- 语言: 捷克语
- 类型: 标准考试
- 已核对 PDF 官方答案

第 1 题 - RS 锁存器仿真 (RS Latch Simulation) (5 分)

题目: 输入 A、B、C 在时间 t0 到 t4 的值如图所示。写出 X 和 Y 输出的值。[English] Inputs A, B, C had values shown in the figure at times t0 to t4. Write the values of X and Y outputs.

输入序列:

```
A = 1 | 1 | 1 | 0 | 1
B = 1 | 1 | 0 | 1 | 1
C = 0 | 1 | 0 | 0 | 0
    t0 t1 t2 t3 t4
```

官方参考答案 (Official Answer):

```
X = 0 | 0 | 1 | 1 | 0   (二进制: 00110)
Y = 1 | 0 | 0 | 0 | 1   (二进制: 10011)
```

详细解析: - t0: A=1 → Reset, X=0; B·C=0 → Y=1 - t1: A=1, B·C=1 → Reset 优先, X=0, Y=0
- t2: A=1, B·C=0 → X 变 1? (需看电路) - t3: A=0, B·C=0 → 保持 - t4: A=1 → Reset

第 2 题 - Shannon 展开 (Shannon Expansion) (6 分)

题目: 将第 1 题电路的函数 $X=f(A,B,C,X)$ 用 Shannon 展开分解为: $X=(\text{not } X \text{ and } f_0(A,B,C)) \text{ or } (X \text{ and } f_1(A,B,C))$ 。
[English] Decompose the function $X=f(A,B,C,X)$ from question 1 into the form $X=(\text{not } X \text{ and } f_0(A,B,C)) \text{ or } (X \text{ and } f_1(A,B,C))$ using Shannon expansion.

官方参考答案 (卡诺图 Karnaugh Map):

f0:	B				f1:	B			
	A	0	1		A	0	1		
C 0	0	0	1	0	C 0	1	0	1	0
1	1	0	0	0	1	1	0	1	0

官方表达式:

```
X = (not C and B and A) or (C and not B and not A)
    or (X and not B and not A) or (X and B and A)
```

第 3 题 - 等价逻辑函数 (Equivalent Logic Functions) (4 分)

题目: 勾选所有与其他函数等价的逻辑函数。[English] Check all logic functions that have another equivalent function here.

```

y1 <= (A or D) and (not A or C);
y2 <= C or (A and C and B) or (not A and C and D);
y3 <= (not A and D) or (A and not D) or (C and D);
y4 <= (C and D) or (not A xor not D);

```

官方参考答案: y3 y4

详细解析:

$$\begin{aligned}
 y1 &= (A + D)(\bar{A} + C) \\
 &= A\bar{A} + AC + D\bar{A} + DC \\
 &= AC + \bar{A}D + CD
 \end{aligned}$$

y2:

$$\begin{aligned}
 y2 &= C + ABC + \bar{A}CD \\
 &= C(1 + AB + \bar{A}D) \\
 &= C
 \end{aligned}$$

y3:

$$\begin{aligned}
 y3 &= \bar{A}D + AD + CD \\
 &= (A \oplus D) + CD \quad \leftarrow \text{异或形式}
 \end{aligned}$$

y4:

$$\begin{aligned}
 y4 &= CD + (\bar{A} \oplus D) \\
 &= CD + (\bar{A} \oplus D) \quad \bar{A} \oplus D = A \oplus D \\
 &= (A \oplus D) + CD
 \end{aligned}$$

$$\text{比较结果: } y1 = AC + \bar{A}D + CD - y2 = C - y3 = (A \oplus D) + CD - y4 = (A \oplus D) + CD$$

答案: y3 y4

关键公式: $\bar{A} \oplus B = A \oplus B$ (取反后的异或等于原异或)

第 4 题 - 8 位寄存器运算 (2 分)

题目: 将 124+125+126+127 运算结果的低位存入 1 字节寄存器, 作为 8 位数的十进制值是多少? [English] If we store the lower bits of 124+125+126+127 operation into a 1-byte register, what decimal value will it hold as an 8-bit number?

计算:

$$124 + 125 + 126 + 127 = 502$$

$$502 \bmod 256 = 246$$

答案: - a) unsigned: **246** - b) signed: **-10** (246 - 256)

第 5 题 - Moore/Mealy 自动机定义 (3 分)

题目: 补全定义——必须数学上精确! [English] Complete the definition - it must be mathematically precise!

定义: Automat Moore (Mealy) je uspořádaná šestice $M = \langle X, S, Z, \delta, \lambda, s \rangle$

- **X** 是有限输入字母表 / is a finite input alphabet
- **S** 是有限状态集合 / is a finite set of states
- **Z** 是有限输出字母表 / is a finite output alphabet
- δ 是状态转移函数 / is the state transition function: Moore: $S \times X \rightarrow S$, Mealy: $S \times X \rightarrow S$
- λ 是输出函数 / is the output function: Moore: $S \rightarrow Z$, Mealy: $S \times X \rightarrow Z$

- s 是初始状态 / is the initial state
-

第 6 题 - +1 加法器设计 (7 分)

题目: +1 加法器可以不用全加器, 用门电路更简单地实现。画出由门组成的电路图。[English] The +1 adder can be implemented much simpler using gates without a full adder. Draw its schematic composed of gates.

电路结构: - $s_0 = x_0 \text{ XOR } 1 = \text{NOT } x_0$ - $s_1 = x_1 \text{ XOR } (x_0)$ - $s_2 = x_2 \text{ XOR } (x_0 \text{ AND } x_1)$ - $s_3 = x_3 \text{ XOR } (x_0 \text{ AND } x_1 \text{ AND } x_2)$ - $\text{carry} = x_0 \text{ AND } x_1 \text{ AND } x_2 \text{ AND } x_3$

第 7 题 - VHDL 位操作 (7 分)

题目: 用并发 (concurrent) VHDL 代码最优地描述图中电路, 不使用顺序语句。整个架构只用一条语句可得满分, 每多一条扣 1 分。[English] Optimally describe the circuit in the figure using concurrent VHDL code without sequential statements. Full points for using only one statement in the architecture block; one point deducted for each additional statement.

```
library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity Test20250609q7 is
    port(x: in std_logic_vector(3 downto 0);
          y: out std_logic_vector(3 downto 0));
end entity;
architecture rtl of Test20250609q7 is
begin
    y <= x and (x(2 downto 0) & '1');
end architecture rtl;
```

第 8 题 - VHDL 电路分析 (7+1 分)

题目: 根据以下代码, 使用门、多路选择器、+1 加法器、比较器和 DFF 寄存器的符号画出方框图。[English] Draw the block diagram for the circuit described by the following code, using symbols for gates, multiplexor, +1 adder, comparator, and DFF registers.

```
library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity Ex20250609q7 is
    port (CLK : in std_logic; Q : out std_logic);
end entity;
architecture rtl1 of Ex20250609q7 is
begin
    iproc: process(CLK)
        constant M: integer := 9;
        variable cntnr : integer range 0 to M := 0;
        variable x : std_logic := '0';
    begin
        if rising_edge(CLK) then
            if cntnr < M then
                cntnr := cntnr + 1;
            else
                cntnr := 0;
            end if;
        end if;
    end process iproc;
    Q <= x;
```

```

        x := not x;
    end if;
end if;
Q <= x;
end process;
end architecture;

```

电路名称：分频器 (Frequency Divider) / 模 10 计数器带输出翻转

第 9 题 - 分支预测 (Branch Prediction) (8 分)

非考点提示 (Not on Exam): 根据 2026 年 1 月考试说明, 分支预测器本次不考, 可战略性跳过。

题目: C 程序在数组中查找最小值。假设 for 循环编译为 do-while 形式, 处理器使用以下预测器, 计算分支预测错误次数。[English] A C program finds the minimum in an array. Assuming the for-loop is compiled as do-while and the processor uses the following predictors, calculate the number of branch mispredictions.

```

int data[] = { 0, 1, -2, -3, 4, -5, 6, -7, -8, 9 };
int min = INT_MAX;
for (int i = 0; i < 10; i++) {
    if (data[i] < min) min = data[i];
}

```

官方参考答案 (Official Answer): - 1 位预测器 (初始 NT) : misses = **9** (if 分支 7 次 + for 循环 2 次) - 2 位预测器 (初始 WT) : misses = **7** (if 分支 6 次 + for 循环 1 次)

官方分支序列分析:

Branch:	N	T	N	N	T	N	T	N	N	T
Data:	0	1	-2	-3	4	-5	6	-7	-8	9

注意: 今年考试不考分支预测! (老师邮件确认) **注意:** 实际答案可能因编译器优化和分支预测器具体实现而略有不同