

```
# LSP Exam - January 21, 2015
```

```
> **CVUT FEL (ČVUT) - České vysoké učení technické v Praze | Czech Technical University in Prague**
>
> [ ](2015-01-21_Exam_CN.md) | [English](2015-01-21_Exam_EN.md) | [Čeština](2015-01-21_Exam_CZ.n
>
> **AI-Generated Solution** - Reference analysis below
```

```
---
```

Question 2: RS Latch Circuit Simulation Frequently Tested

****Problem**:** Given inputs A, B, C values at times t0, t1, t2, t3 as shown, write the Q output value.

```
...
A = ..0../..1../..1../..1../
B = ..0../..0../..0../..1../
C = ..1../..1../..0../..0../
```

```
t0   t1   t2   t3
```

```
...
```

Answer

```
...
```

```
Q = ...1.../...0.../...0.../...1.../
```

```
...
```

```
---
```

Question 3: Shannon Expansion Frequently Tested

****Problem**:** Decompose the function $Q=f(A,B,C,Q)$ from question 2 into:

```
...
Q = (not Q and f0(A,B,C)) or (Q and f1(A,B,C))
...
```

Solution Method

```
...
```

```
f0 := f(A,B,C,'0') := (A B) · ('0' + (B C)) := (A B) · (B C)
f1 := f(A,B,C,'1') := (A B) · ('1' + (B C)) := (A B) · '1' := (A B)
```

```
...
```

f0 Karnaugh Map (A B) · (B C)

f0	C=0	C=1
AB=00	0	1
AB=01	0	0
AB=11	1	0
AB=10	0	0

f1 Karnaugh Map (A B)

f1	C=0	C=1
AB=00	1	1
AB=01	0	0
AB=11	1	1
AB=10	0	0

Question 4: Signed/Unsigned Bit Values Frequently Tested

****Problem**:** What is the decimal value of the 10-bit binary number ``10 0000 1111``?

a) ****Unsigned**:** _____

b) ****Two's-complement (signed)**:** _____

Answer

...

`10 0000 1111` (binary)

a) *Unsigned:* $2^9 + 2^3 + 2^2 + 2^1 + 2^0 = 512 + 8 + 4 + 2 + 1 = 527$

b) *Two's-complement (signed):*
 MSB is 1, indicating negative number
 $= -2^9 + (0\ 0000\ 1111)$
 $= -512 + 15 = -497$

...

Question 5: Equivalent Logic Functions Frequently Tested

****Problem**:** Mark all logic functions that are equivalent to other functions:

```

```vhdl
f1 <= (A xor C) or (A and not C);
f2 <= (B or C) and (not A or B or C);
f3 <= ((C and not B) or (B and A));
f4 <= (A or C) and (not A or not C);
f5 <= (A and not B) xor (A and C);
f6 <= (A and not C) or (C and not A);
```

```

Solution Method

Draw Karnaugh maps for each function and compare to find equivalent ones!

****Hint**:** f4 and f6 are both equivalent to A XOR C

Question 6: RS Latch Drawing Frequently Tested

****Problem**:** Draw RS latch using only NOR gates, and draw RS latch using only NAND gates.

NOR Gate RS Latch

S *[NOR]* *Q*

R *[NOR]* *Q*

NAND Gate RS Latch

S *[NAND]* *Q*

R *[NAND]* *Q*

****Note**:** NAND-type RS latch inputs are active-low!

Question 7: Asynchronous Divider Design

****Problem**:** Add gates and connections to the incomplete diagram to create an asynchronous divide-by-18

Use 5 DFF flip-flops for implementation.

Design Approach

- $18 = 2 \times 9 = 2 \times 3 \times 3$
- Need to detect count value 17 (10001) and reset

Question 8: VHDL Code Analysis

****Problem**:** Analyze the following poorly formatted VHDL code, draw the corresponding logic circuit diagram

```
```vhdl
library IEEE; use IEEE.STD_LOGIC_1164.all;
entity test20140214 is port (a, b, c, d : in std_logic; e : out std_logic); end;
architecture rtl of test20140214 is begin
process(a, b) variable z:std_logic_vector(0 to 3); begin
if b = '0' then z:=(others=>'0');
elsif rising_edge(a) then
 if c='1' then z:=d & z(0 to 2);
 else z:=z(3) & z(0 to 2);
end if;
end if;
end process;
end architecture;
```

```

 end if;
end if;
e<=z(3);
end process;
end rtl;
```

```

Code Analysis

- ****Function****: 4-bit shift register
- ****Inputs****: a (clock), b (async clear), c (mode select), d (data input)
- ****Output****: e = z(3)
- When c='1': Serial input d, shift right
- When c='0': Circular right shift

Knowledge Summary

| Question Type | Concept | SEL Reference |
|----------------------|-------------------------|---------------|
| Shannon Expansion | Function decomposition | p.11-14 |
| Signed/Unsigned | Bit value calculation | p.2-3 |
| Equivalent Functions | Karnaugh map comparison | p.4-7 |
| RS Latch | NOR/NAND implementation | p.11-14 |
| Divider | Digital counter design | - |
| VHDL Analysis | Code understanding | - |