
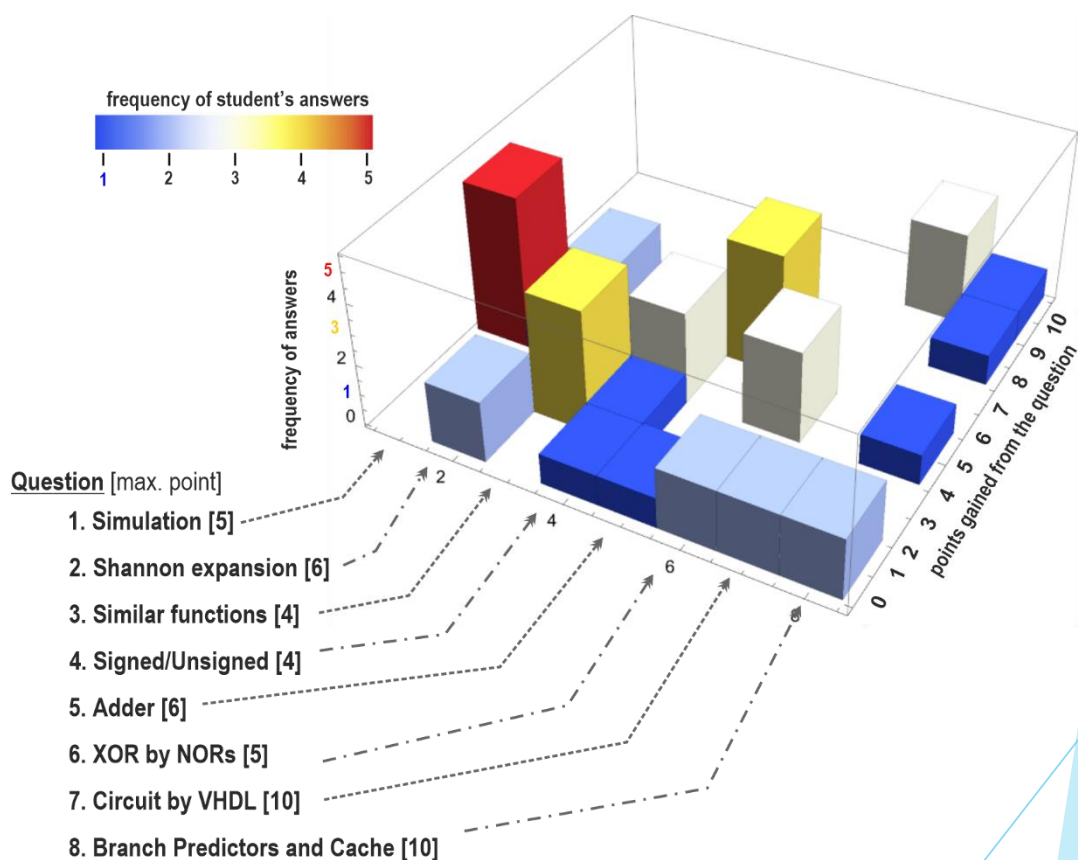


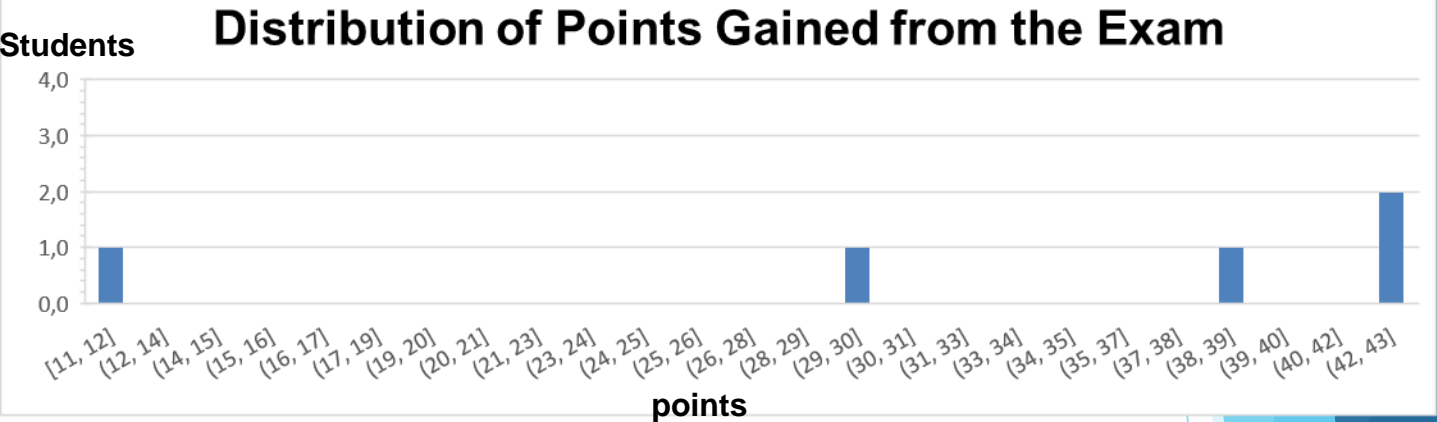
Statistical results of the LSP written exam on Monday 20 January 2025





Surname and first name :.....

Exam Jan 20, 2025 - write here only your answers

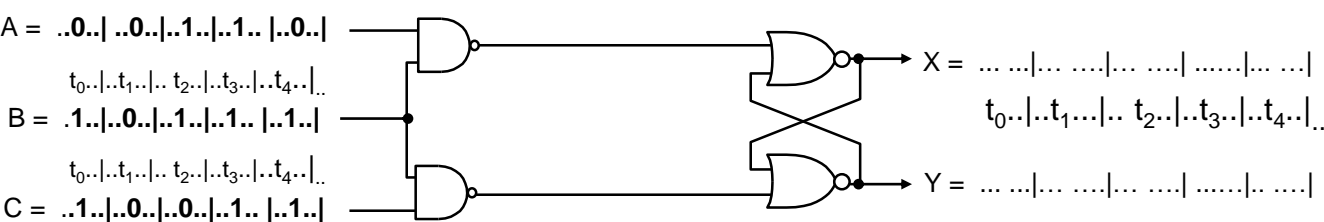1. Inputs A, B and C have values shown in the figure for times t_0, t_1, t_2, t_3, t_4 . Write values of X and Y outputs. The intervals between input changes are long so that we can neglect the delays of gates.



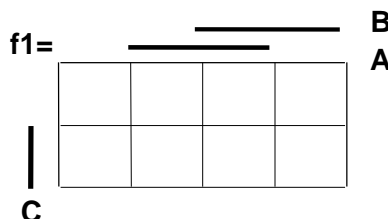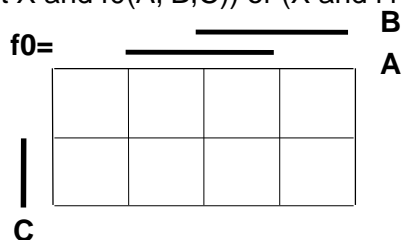2. Decompose function $X=f(A,B,C, X)$ from question 1 with the aid of Shannon's expansion into $X=(\text{not } X \text{ and } f_0(A, B,C))$ or $(X \text{ and } f_1(A,B,C))$. Write f_0 and f_1 functions as Karnaugh maps:



3. Mark all logic functions that have another equivalent logic function here:

$y1 \Leftarrow ((\text{not } A \text{ or } C) \text{ and } B \text{ and not } D) \text{ or } (A \text{ and } D);$

$y1$ ☐

$y2 \Leftarrow ((B \text{ and } (\text{not } A \text{ or } C)) \text{ or } D) \text{ and } (A \text{ or not } D);$

$y2$ ☐

$y3 \Leftarrow (A \text{ or } C \text{ or } D) \text{ and } (A \text{ or } B) \text{ and } (\text{not } D \text{ or } C);$

$y3$ ☐

$y4 \Leftarrow (((\text{not } A \text{ and not } D) \text{ or } (A \text{ and } C)) \text{ and } B) \text{ or } (A \text{ and } D);$

$y4$ ☐

4. . If we perform the addition $1023+1023+1023+1023$ by a 10-bit adder, what will be its result converted to a decimal number as:

a) unsigned b) signed in two's-complement.....

5. Complete the schema of the full one-bit adder.


Carry_{in} —

A —

B —

→ S

→ Carry_{out}

A  Y

5

```

graph LR
    x3[x(3)] --> y3[y(3)]
    x3 --> or2((OR))
    x2[x(2)] --> or2
    or2 --> y2[y(2)]
    x2 --> or1((OR))
    x1[x(1)] --> or1
    or1 --> y1[y(1)]
    x1 --> or0((OR))
    x0[x(0)] --> or0
    or0 --> y0[y(0)]
  
```

```
begin
.....
.....
.....
.....
.....
.....
.....
.....
end architecture;
```

8. Consider a simple C program designed for testing the performance of a processor:

```
int i, j; double arr[2000];  
for (i=0; i<5; i++) { for (j=0; j<2000; j++) arr[j]++;  
}
```

A) How many erroneous branch predictions occur in the program if we assume that for-loops with constant ranges are optimally compiled by **do-while loops** and the processor only uses:

1-bit predictors with default states of Not-Taken, **NT**. Misses=.....

2-bit predictors with default states of Weakly Taken, **WT**. Misses=.....

B) Let the program run on a 64-bit processor that has a **directly mapped data cache** of **32 kilobytes** with **blocks of length 4 words** and the array "arr" starts at address **0x100000**.

What will be the number of cache misses triggered by accesses to **arr** if the cache is empty at the beginning?


Cache misses

6

4

10

Results

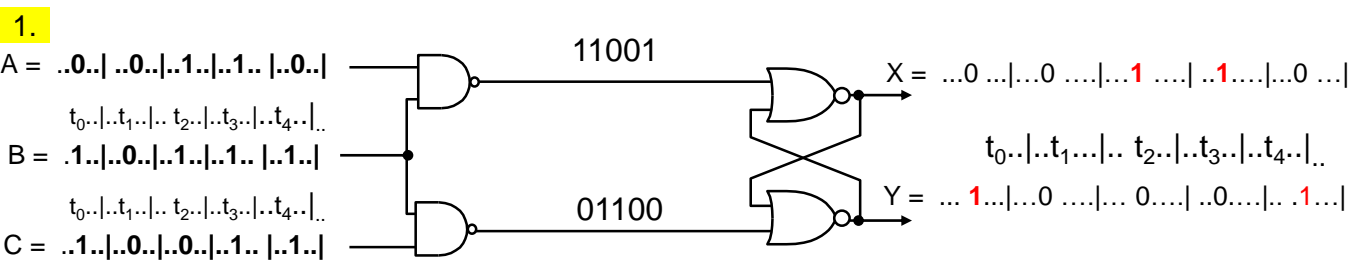

2.

f0=

	B			
A	0	0	1	0
C	0	0	0	0

f1=

	B			
A	0	0	1	0
C	0	0	1	0


3.

$y1 \leftarrow ((\text{not } A \text{ or } C) \text{ and } B \text{ and not } D) \text{ or } (A \text{ and } D);$
 $y2 \leftarrow ((B \text{ and } (\text{not } A \text{ or } C)) \text{ or } D) \text{ and } (A \text{ or not } D);$
 $y3 \leftarrow (A \text{ or } C \text{ or } D) \text{ and } (A \text{ or } B) \text{ and } (\text{not } D \text{ or } C);$
 $y4 \leftarrow (((\text{not } A \text{ and not } D) \text{ or } (A \text{ and } C)) \text{ and } B) \text{ or } (A \text{ and } D);$

y1 ☒
 y2 ☒
 y3 ☐
 y4 ☒

4. If we add $1023+1023+1023+1023$ by a 10-bit adder, what will be its 10-bit result converted to a decimal number.
 a) unsigned $..(1024-1)*4=1024-4=1020$ b) signed in two's-complement.. 1023 represents -1, $4*-1=-4$
 Note: $1024 = 0$ at 10-bit adder. Thus, $N*1024=0$, for any integer N, see [Binary Prerequisite](#)

5. lecture 13

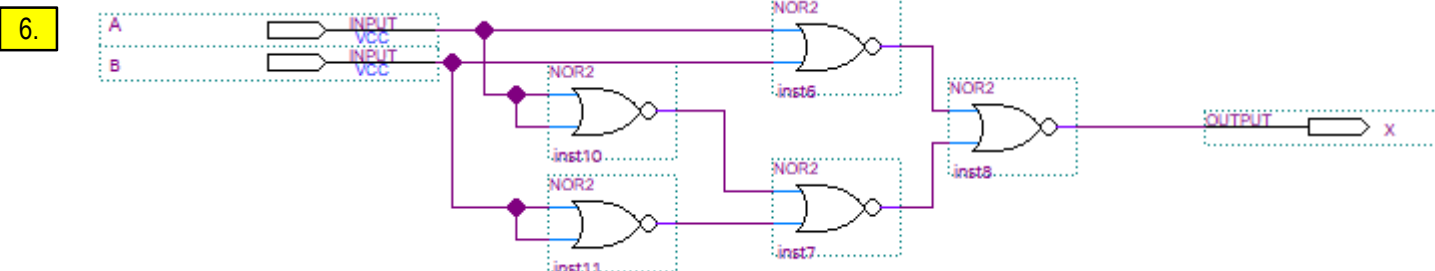

7.

```

library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity Test20240605q7 is port( x: in std_logic_vector(3 downto 0); y: out std_logic_vector(3 downto 0)); end
entity;
architecture rtl of Test20240605q7 is
begin
    y<= ('0' & x(3 downto 1)) xor x; -- the lecture 4th, slide 8
end architecture rtl;
  
```

8. for-loop: 1-bit predictors, init. Not-Taken, NT 2 wrong predictions in outer for loop + $5*2(\text{inner}) = 12$,
 2-bit predictors, init. WT, 1 wrong prediction in outer for loop + $5*1(\text{inner loop}) = 6$

2000 elements of the double array need $2000*8$ (double) = 16000 bytes - the 32 kB cache can contain the whole array. Thus, its first read will only generate cache misses, the following will have cache hits! The array elements are loaded into the cache in whole blocks during the first read. Each block contains 4 words (a word has 8 bytes on a 64-bit processor). 1st access of any block always generates a cache miss; the other three words from the already loaded block result in cache hits. The array begins at the address dividable by 4 (size of blocks), i.e., cache misses

$$= \text{array_elements/size_of_block} = 2000/4 = 500.$$