 


# Logic Systems and Processors *cz:Logické systémy a procesory*

Lecturer: Richard Šusta

[richard@susta.cz](mailto:richard@susta.cz), [susta@fel.cvut.cz](mailto:susta@fel.cvut.cz),  
+420 2 2435 7359


*Version V1.0*



CTU-FEE in Prague, CR – subject BE5B35LSP
 
# DFF - Data Flip-Flop




also contains memory loops  
from invertors



# Repeat: *Identity Law* and *Annulment Law*



## *Identity Law*








Neutral values

   

## *Annulment Law*

Aggressive values

  

  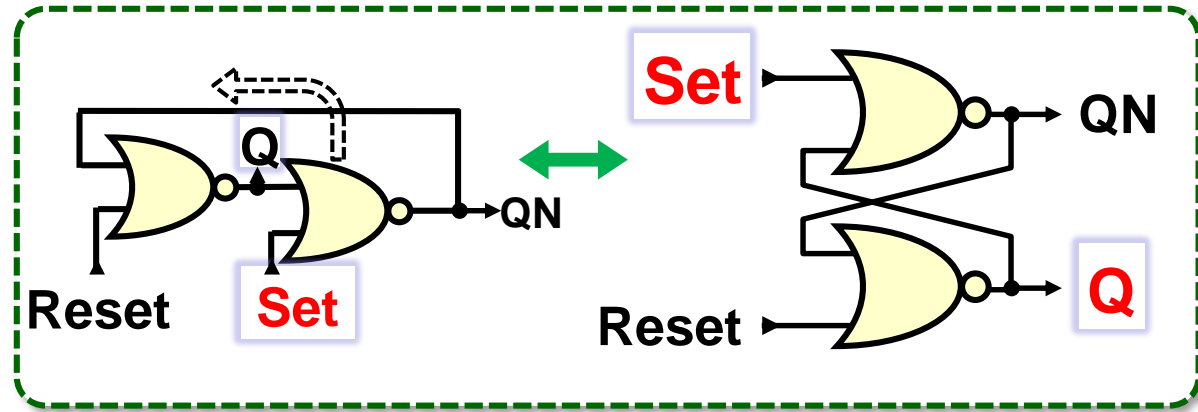   
 



  
## How do I remember the flip-flop circuit from NAND gates?


**NAND** - the *reasoning is symmetric to NOR*.

- AND is the selection of the minimum. A NAND (not AND) latch has a pivotal input value of '0' - if any of its inputs are at '0', then the output will definitely be '1' regardless of the values of the other inputs; hence, a NAND latch circuit has active inputs at '0'.
- If the input goes to '0', the output of the NAND gate will be '1', and therefore Q will be at the same gate as the S input, but S is active here at '0' and so will be negated.


 
# How do I remember the flip-flop circuit from NOR gates?

- ❑ The OR gate is the maximum selection.
- ❑ The NOR (not OR) gate has a key input value of '1' - if any of its inputs is at '1', then the output will be '0' regardless of the values of the other inputs. It follows that the NOR flip-flop circuit has active inputs R and S at '1'.
- ❑ When R and S are '1', both outputs will be '0'. This condition is considered forbidden only if it is required by an external constraint,  $Q = \text{not } Q'$ . The circuit itself does not impose any forbidden states.
- ❑ Since the output of the NOR gate goes to '0' when the input is '1', the output Q cannot be connected to the gate with input S; instead, it will be connected to the other gate.







# Latch




Image: <https://simple.wikipedia.org/wiki/Latch>

 



RS Latch

 

D Latch

 

RS Latch Symbol

  


D Latch Symbols




# Transparent Latch(D-latch) in CMOS


## Solution switches

 



## Gate scheme

 

## CMOS scheme



 


## Transmission gates

  

It has two states:  
**Transparent** and **Memory**

# D-latch behaviour

  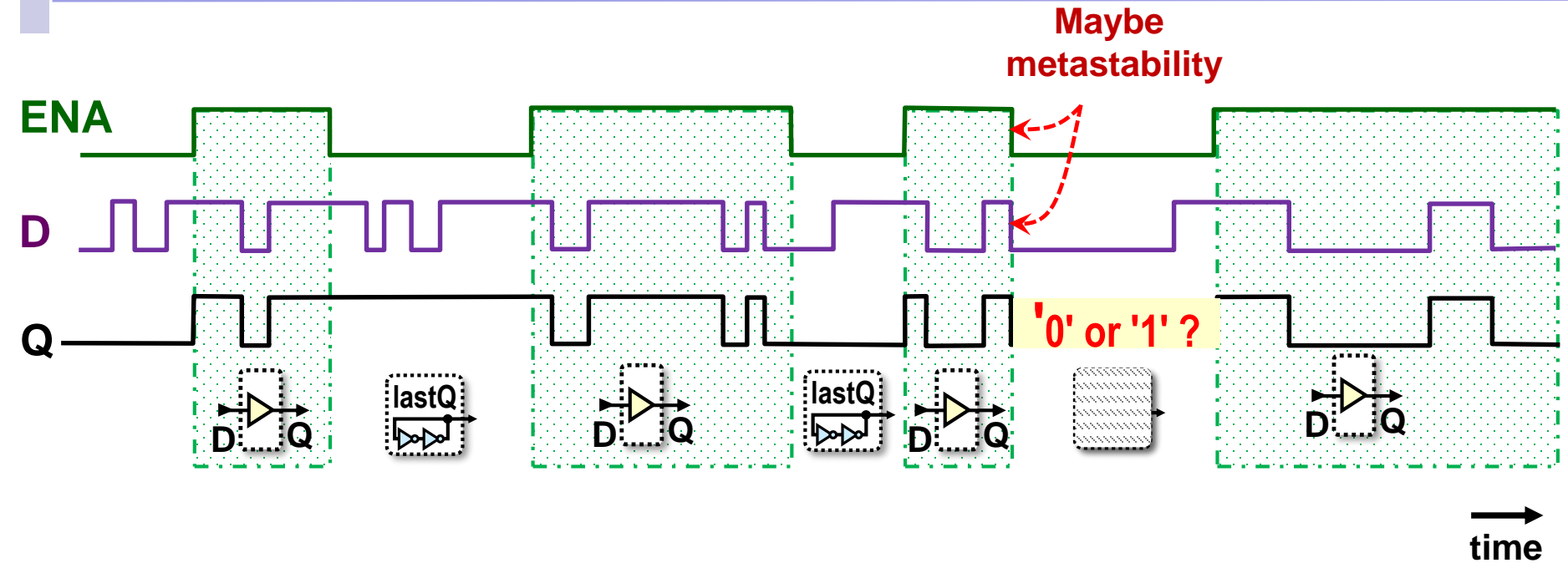

*We will discuss the metastability in the next lecture.*



# Flip-Flop Circuits



"Computer  
flip-flops"

*Flip-flop = a) flip-flops b) reverse direction*

# Latch - Flip-flop in English

We will use English terminology of circuit development tools:


- **Latch** defines only asynchronous latch circuits, such as RS latch and D-latch.
- **Transparent latch** - although it is a precise technical term, it is more often written as **D-latch** instead.
- **Edge-triggered latch** includes a whole category of latch circuits that change their output only when an edge of a clock signal arrives.
- **Flip-flop** - (original term for a back flip, 180-degree turn)  
= In circuits, it denotes the most commonly used implementation known as *edge-triggered* latch, with the established abbreviation DFF, **Data Flip-Flop**.

For more details see the textbook [Logic Circuits](#), chapter 7.1 on page 94




*Note: Czech language does not distinguish between latches and gates.*



# Primary-Replica DFF

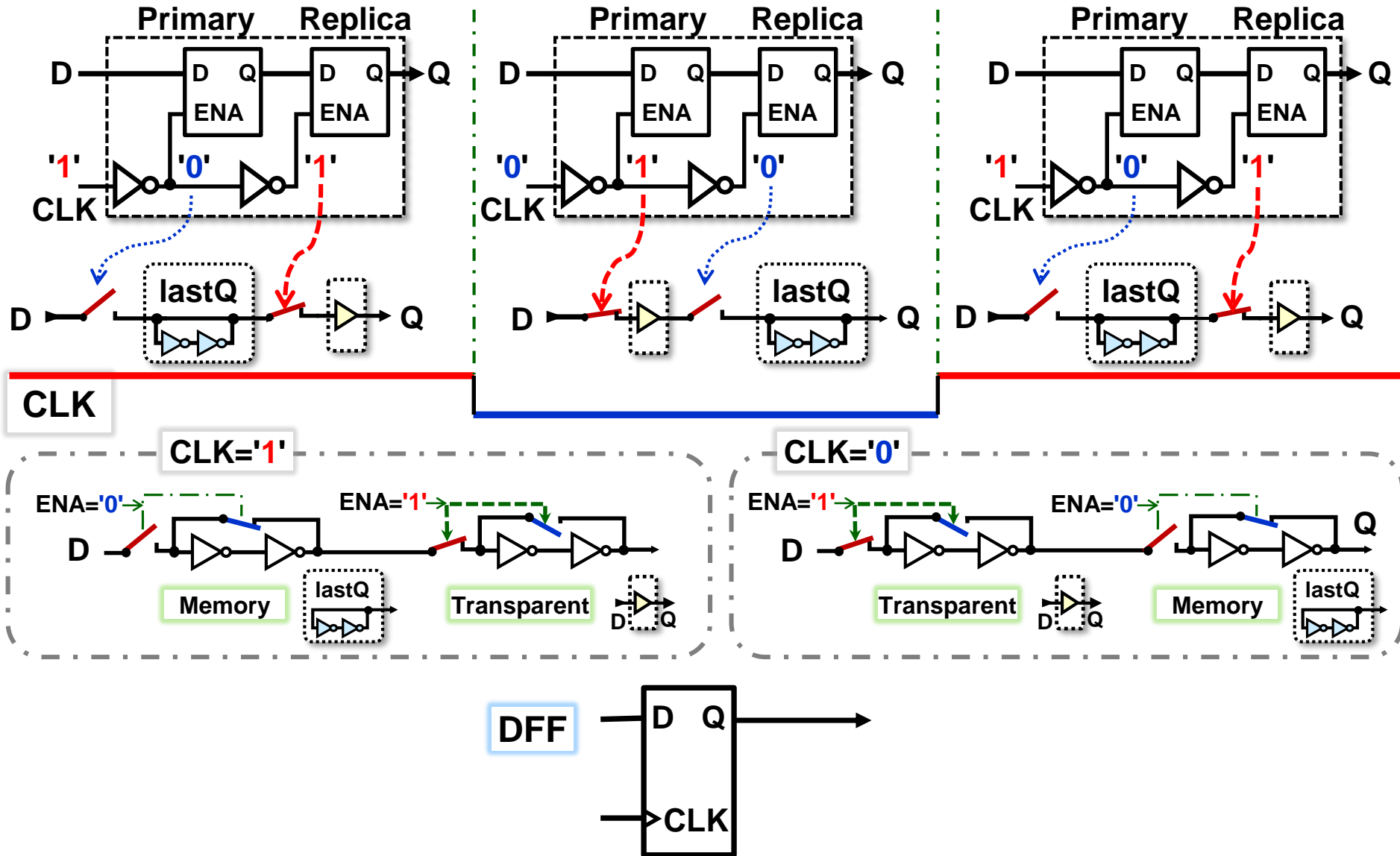


# Actual wiring Primary - Replica

   


*By alternating the clocks, the data flow is interrupted in a similar way to the transition chamber, only one door opens.*

# DFF activity chart

D-Latch

 

DFF

 

CLK

D

D

$t_{setup}$







$t_{hold}$

CLK

$t > t_{min1}$


$t > t_{min0}$



 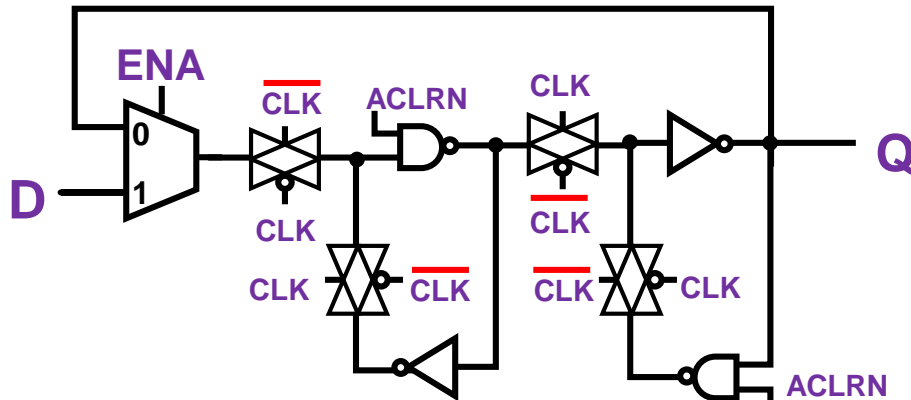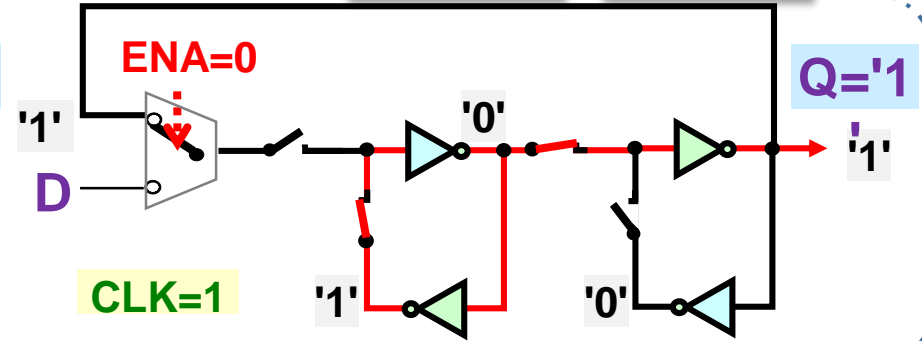   


Asynchronous clear (negative logic)  
after power-up

possible transient  
power-up values

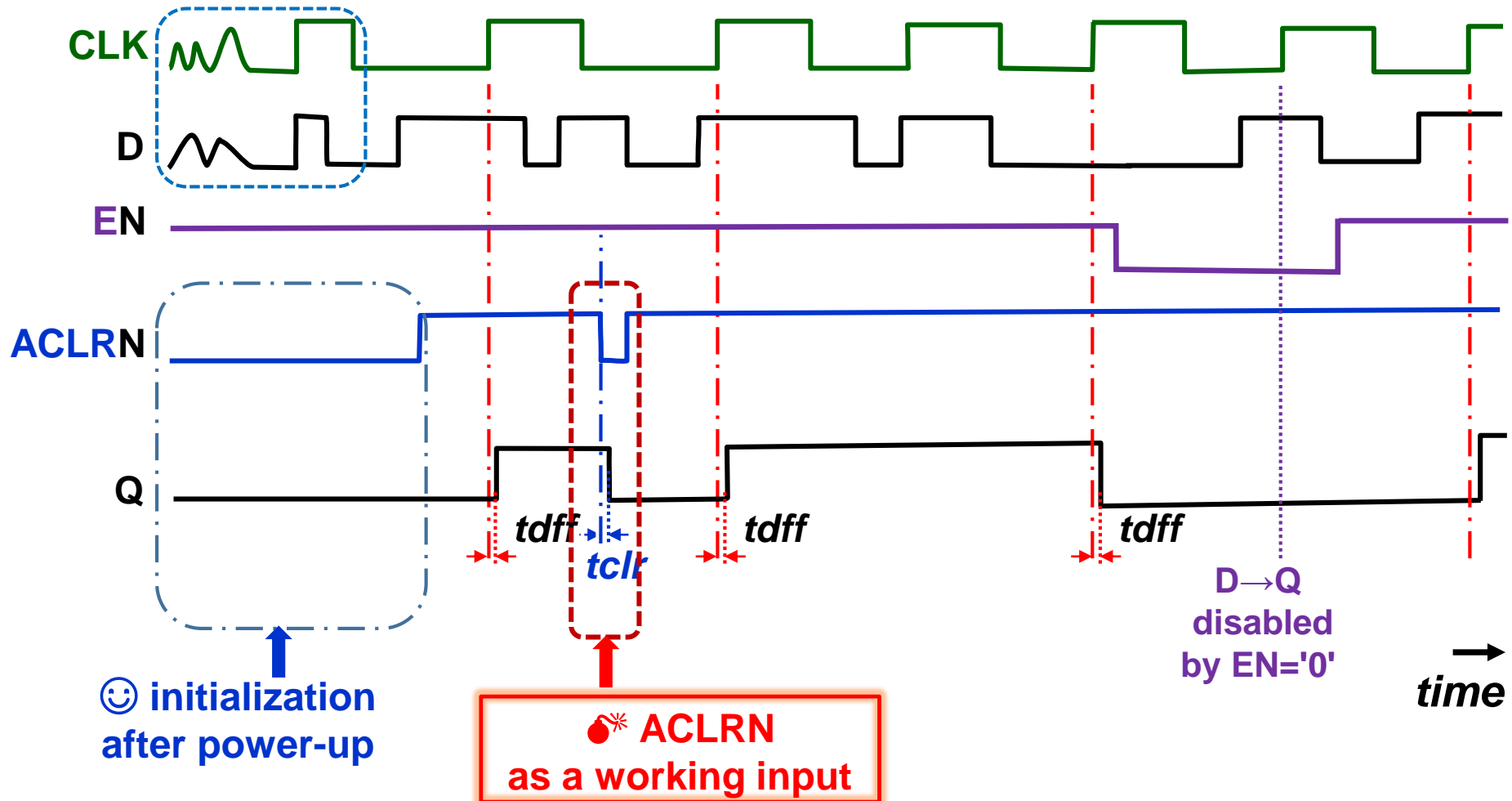

# Divider of ten

with 50% duty cycle)

 

- Let us denote the clock signal frequency at the CLK input as  $f_{\text{clk}}$ .
- The highest active bit of the counter logically changes from '0' to '1' and from '1' to '0'. Let us denote the frequency of this signal as  $f_{\text{out}}$ .
- If the binary counter counts by 1's in the range 0 to  $M-1$ , where  $M$  is any natural number greater than 1, then the counter also divides the input frequency by  $M$ :


$$f_{\text{out}} = \frac{f_{\text{clk}}}{M}$$

In the literature, the word divider (frequency) is sometimes used as a synonym for a binary counter in increments of +1, since its design is virtually identical. The two circuits differ only in the resulting application and the range of functions. Divisors typically only count up and have only a 1-bit output.
 
# 1-bit counter / Divider 2 (1/2)

The output will be 0, 1, 0, 1... The  $\delta$  function of the next state is just an inverter.

```
library ieee;
use ieee.std_logic_1164.all;
entity DivBy2 is
  port (CLK : in std_logic;
        Q : out std_logic);
end entity;
architecture rtl1 of DivBy2 is
begin
  process(CLK)
    variable q2 : std_logic := '0'; -- simulations require initialization!
  begin
    if rising_edge(CLK) then
      q2 := not q2; -- the delta function - the next value = 1 bit adder + 1
    end if;
    Q <= q2; -- the omega function is only a wire
  end process;
end architecture;
```



# 1-bit counter / Divider 2 (2/2)

```
architecture rtl2reg of DivBy2 is begin
```

```
  process(CLK)
```

```
    variable q2 : std_logic := '0';
```

```
  begin
```

```
    if rising_edge(CLK) then
```


```
      Q <= q2; -- here, omega adds 1 register
```

```
      q2 := not q2; -- the delta function
```

```
    end if;
```

```
  end process;
```

```
end architecture;
```

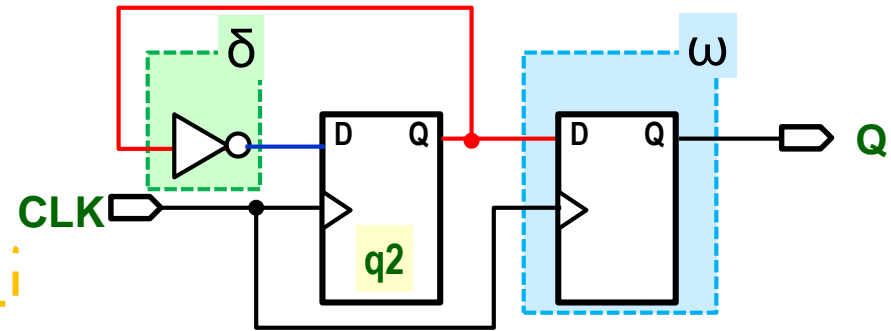

*The placement of omega section affects the circuit!*

```
architecture rtl3wrong of DivBy2 is begin
```

```
  process(CLK)
```

```
    variable q2 : std_logic := '0';
```

```
  begin
```

```
    if rising_edge(CLK) then
```


```
      q2 := not q2; -- the delta function
```

```
      Q <= q2; -- now, omega uses the next value
```

```
    end if;
```

```
  end process;
```

```
end architecture;
```


 


# Counter 5 / Divider 5 (1/2)

```
library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity DivBy5 is
  port ( CLK : in std_logic; Q : out std_logic);
end entity;
architecture rtl1 of DivBy5 is
begin
```

```
  process(CLK)
    constant DivBy: integer:=5;
    variable cntr : integer range 0 to DivBy-1:=0;
  begin
    if rising_edge(CLK) then
      if cntr<DivBy-1 then cntr:=cntr+1; else cntr:=0;
    end if;
    end if;

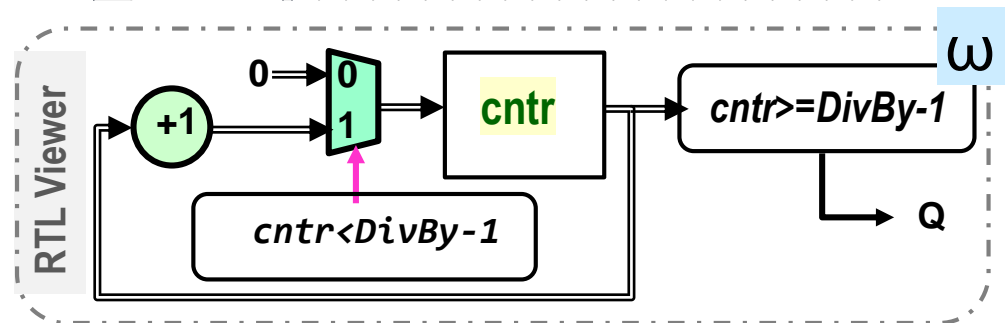     if cntr<DivBy-1 then Q<='0'; else Q<='1';
    end if;
  end process;
end architecture;
```



$\delta$

$\omega$

$\omega$  - implementation?  
It delays Q output and  
generate glitches.



# Counter 5 (2 of 2)

architecture rtl3universal of DivBy5 is  
begin

process(CLK)

constant DivBy: integer:=5;

variable cntr : integer range 0 to DivBy-1:=0;

begin

if rising\_edge(CLK) then



if cntr<DivBy/2 then Q<='0'; else Q<='1'; end if; -- more robust w output function

if cntr<DivBy-1 then cntr:=cntr+1; else cntr:=0; end if; --  $\delta$  function

end if;

end process;



end architecture;

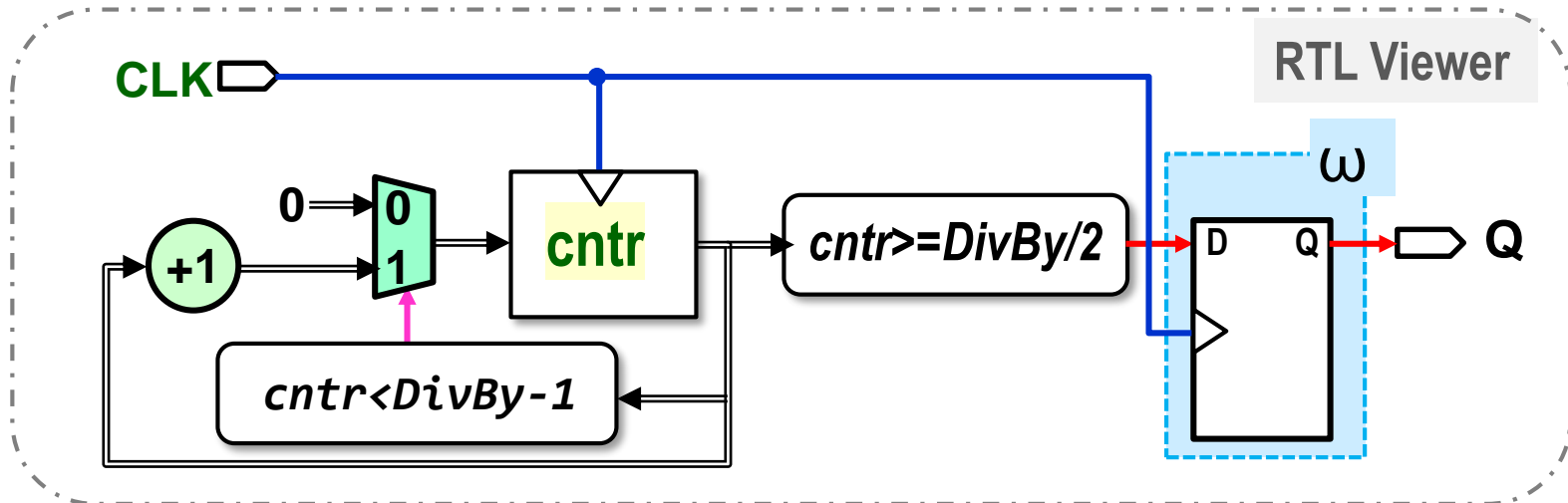 

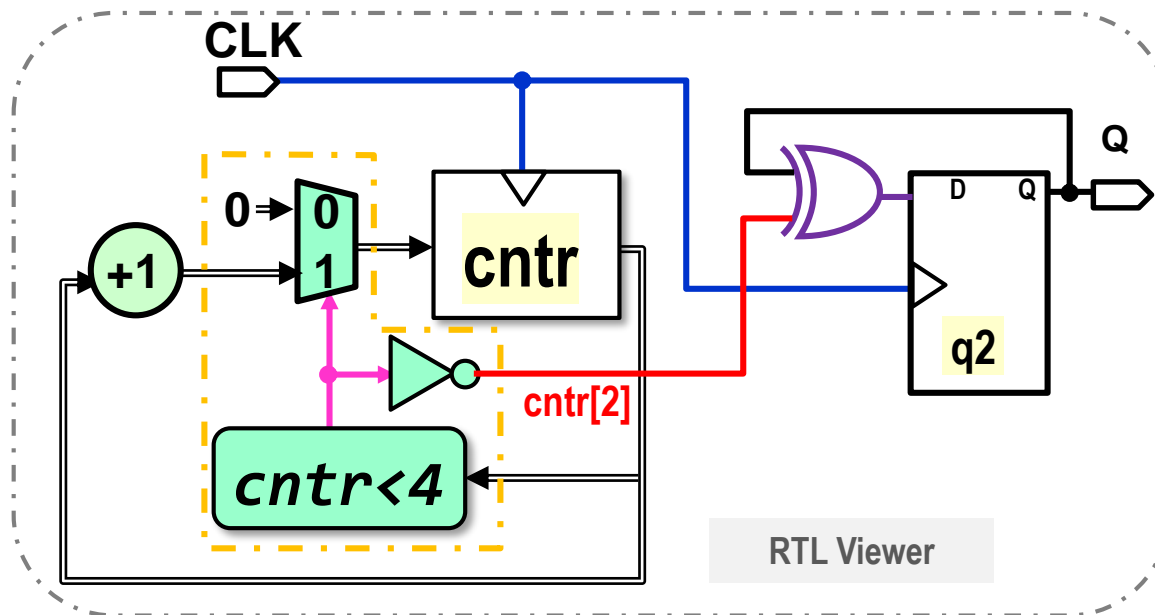 
# Divider by ten with 50% duty cycle

```


library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity DivBy10 is
    port ( CLK : in std_logic; Q : out std_logic);
end entity;
architecture rtl1 of DivBy10 is
begin
    process(CLK)
        constant DivBy: integer:=5;
        variable cntr : integer range 0 to DivBy-1:=0;
        variable q2 : std_logic:='0';
    begin
        if rising_edge(CLK) then
            if cntr < DivBy-1
            then cntr:=cntr+1;
            else cntr:=0;
                q2:=not q2; -- DivBy2
            end if;
        end if;
        Q<=q2; -- the omega - only a wire
    end process;
end architecture;
    
```



# Divider 10 without and with Enable

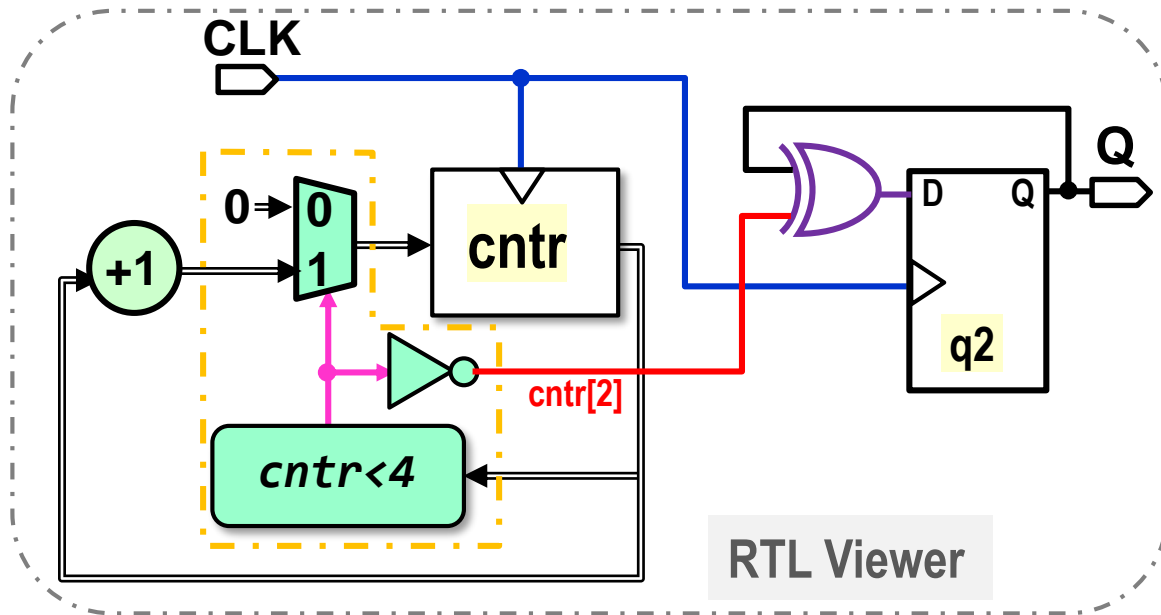

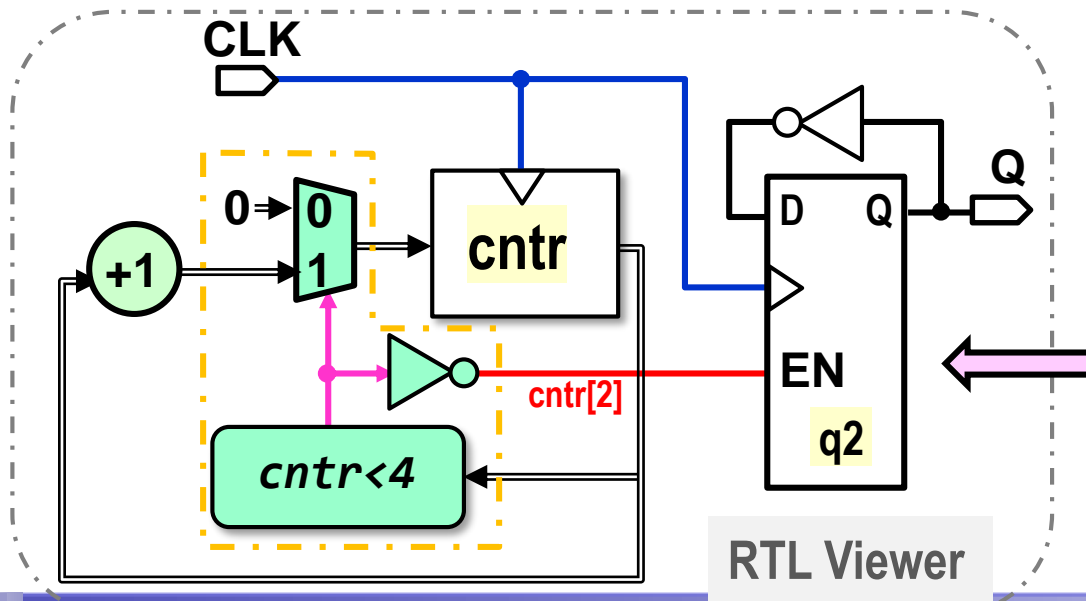*Both solutions are completely equivalent. The compiler selects the one it considers more appropriate after considering the necessary couplings and other parameters.*



**EN = ENABLE**  
But how do we plug it in?  
We don't have to, the Cyclone  
FPGA family DFF has it.





# WE'RE TESTING OUR DESIGN...


*by uploading it to the technology*



Goleta Air & Space Museum  
[www.Air-and-Space.com](http://www.Air-and-Space.com)  
© 2004, Brian Lockett  
[www.Air-and-Space.com](http://www.Air-and-Space.com)  
© 2004, Brian Lockett



# Sci-fi Detector of Bugs

 

Testing our design by

**TESTBENCHES IN VHDL**




# Testing & Simulation



- Cannot cover **all** possible cases
- Possibility of surviving subtle (corner case) bugs

# Formal Verification

 

- Equivalent to simulating **all** cases in simulation
- No **bug** according to the specified property

■ It is always possible

■ Sometimes it is possible

# TECH URBAN LEGENDS

- ✧ The first "Bug" of the modern era is traditionally attributed to Grace Murray Hopper for finding a bug in the contacts of the Mark I computer based on relay logic.



**Log!**


92  
9/9

0800 Antam started  
1000 " stopped - antam ✓

1300 (032) MP - MC 1.2700 9.037 847 025  
033 PRO 2 2.130476415 9.037 846 985 correct  
correct 2.130676415 4.615925059(-2)


Relays 6-2 in 033 failed special speed test  
in relay 11.000 test.

Relays changed  
1100 Started Cosine Tape (Sine check)  
1525 Started Multi-Adder Test.

1545  Relay #70 Panel F  
(moth) in relay.



First actual case of bug being found.

1630 Antam started.  
1700 closed down.

 



# **Simulation in VHDL**

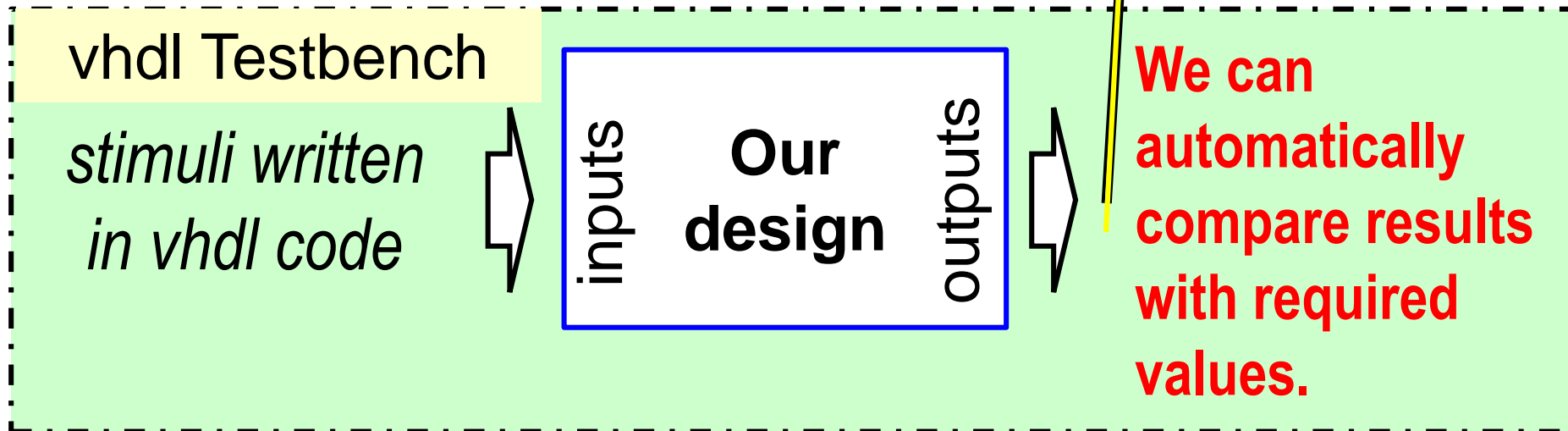 

*stimulus, pl. stimuli (from Latin stilus, stylus->style) - something that rouses the mind or spirits or incites to activity - en: stimulus, stimulus*

# The after command in the simulation

```
signal clk : std_logic := '0'; ←
```


```
signal z, key0 : std_logic;
```

Note: Initialized signals (wires) are suitable for simulation only !!! Their synthesis is very difficult. Quartus often ignores a shows warning.

```
z <= '1', '0' after 5 ns, '1' after 10 ns;
```


```
key0 <= '0', '1' after 30 ns; -- initialization ...
```
 
```
clk <= not clk after 5 ns; -- clock
```



```
library ieee; use ieee.std_logic_1164.all;
entity n2and is port (a, b, isNand : in std_logic; y : out std_logic);
end entity; -----
architecture arch0 of n2and is
begin y <= a and b when isNand='0' else not (a and b);
end architecture; -----
architecture arch1 of n2and is
begin process(a,b, isNand)
    variable tmp : std_logic;
    begin tmp:=a and b; if isNand='1' then tmp:=not tmp; end if;
        y<=tmp;
    end process;
end architecture; -----
architecture arch2 of n2and is
signal tmp : std_logic;
begin process(a,b, isNand, tmp)
    begin tmp<=a and b; if isNand='1' then tmp<=not tmp; end if;
        y<=tmp;
    end process;
end architecture; -----
```

# Let's sketch the waveforms

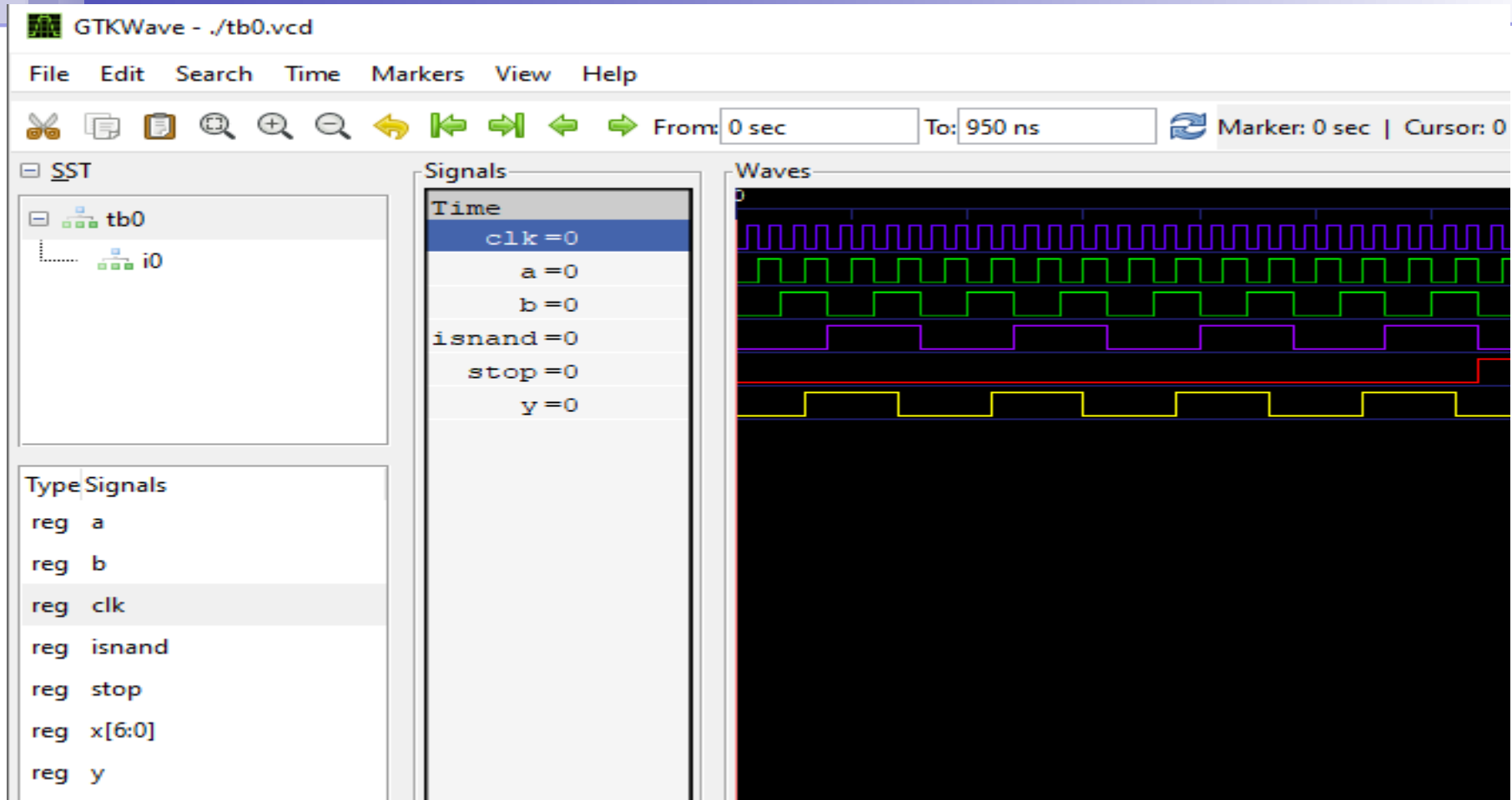

```
signal x: unsigned(6 downto 0):=(others=>'0');  
signal clk, a, b, isNand, stop, y : std_logic:='0';  
begin -- architecture  
    clk<=x(0); a<=x(1); b<=x(2); isNand<=x(3); stop<=x(6); x<= x+1 after 10 ns;
```





```
library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity tb0 is end entity; -- entity for testbench does not contain
declarations
architecture testbench0 of tb0 is
signal x: unsigned(6 downto 0):=(others=>'0');
signal a, b, isNand, stop : std_logic:='0';
signal y : std_logic:='0';
begin -----
    a<=x(1); b<=x(2); isNand<=x(3); stop<=x(6);
    x<= x+1 after 10 ns;
i0 : entity work.n2and(arch0) port map(a, b, isNand, y);
    assert stop/='1' report LF&LF&":-) Done!"&LF severity failure;
end architecture;
```