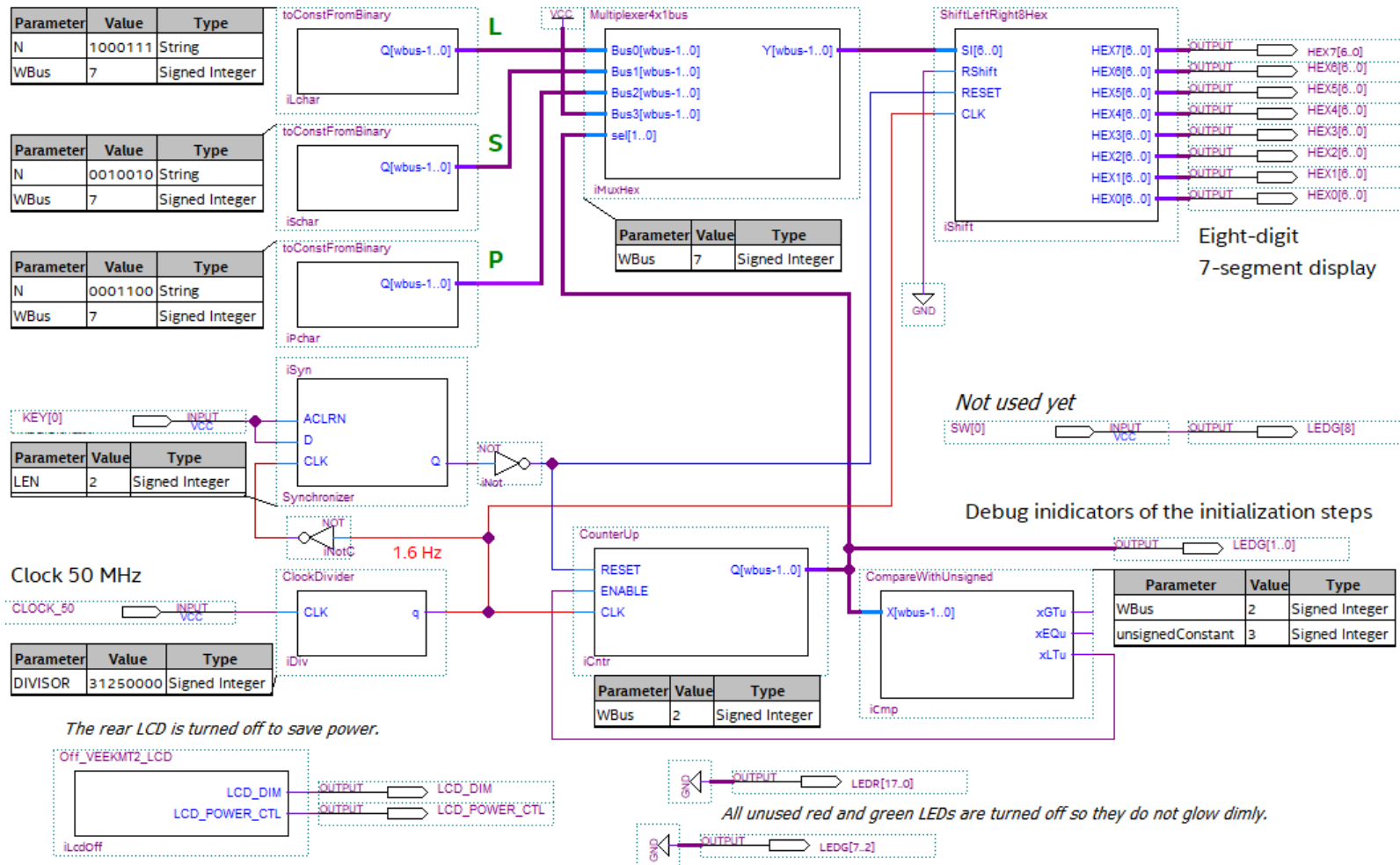


### Task – Advertising Panel - 4 points




Connect the schema and improve its wiring to earn 4 points.

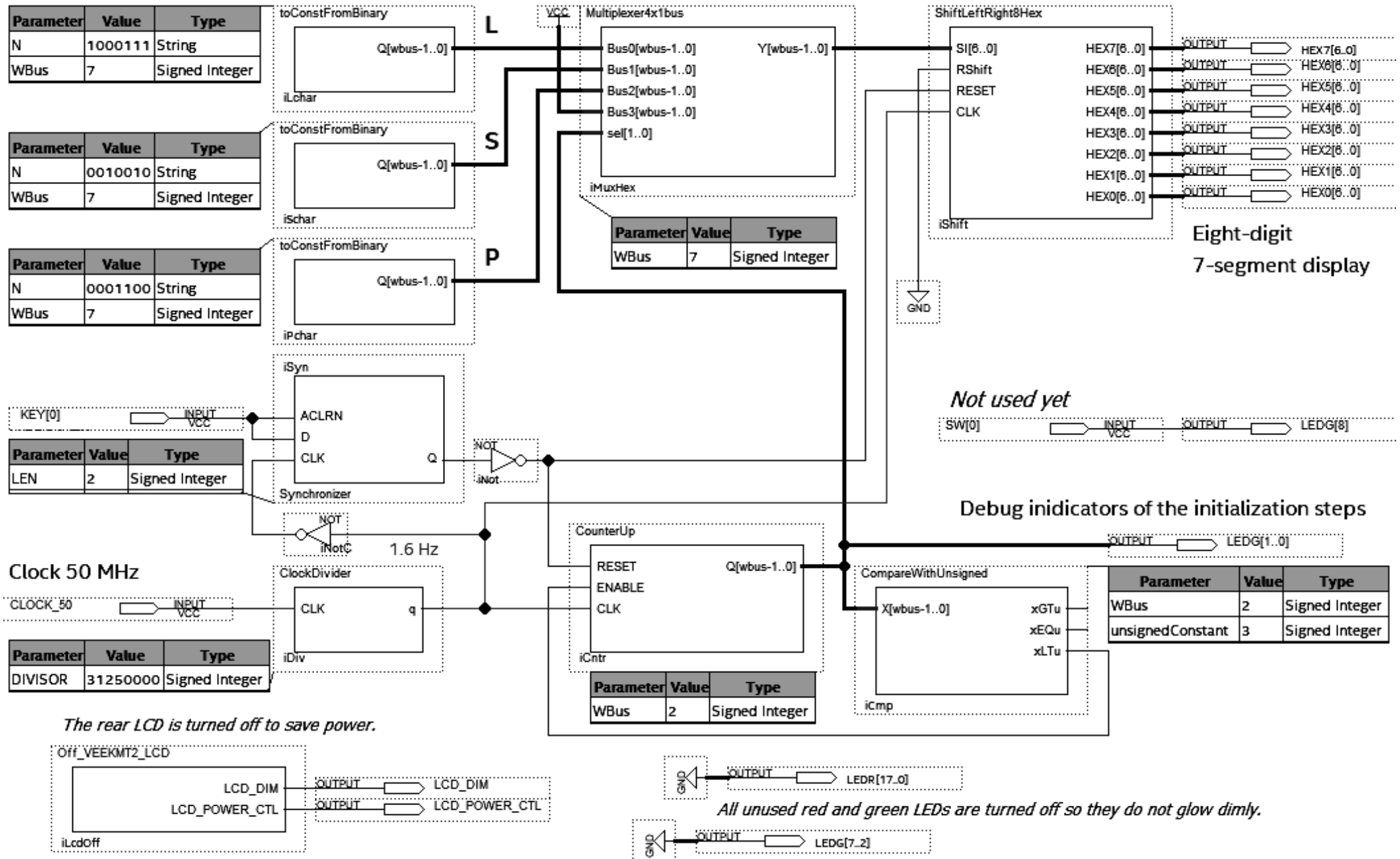
- 1) Correct a small error in the schema so LSP is shown continuously. *Hint: You will find it near a tiny component.*
- 2) Connect the SW[0] switch to the RSHIFT input of the shift register. Then, modify the circuit so that LSP shows correctly from startup, i.e., from pressing the reset KEY[0] for both SW[0] settings, i.e., for shifting left or right.  
The text "LSP" must remain correctly oriented and not run backwards, i.e., as "PSL."
- 3) Add the Lcd16x2Text module from the DCE library that will display your name.
- 4) Change the advertisement to "FEL" or to any word with three different characters.

**Note:** The coding of 7-segment displays is given at the end of the assignment.

The previous diagram — enlarged and optimized for black-and-white printing


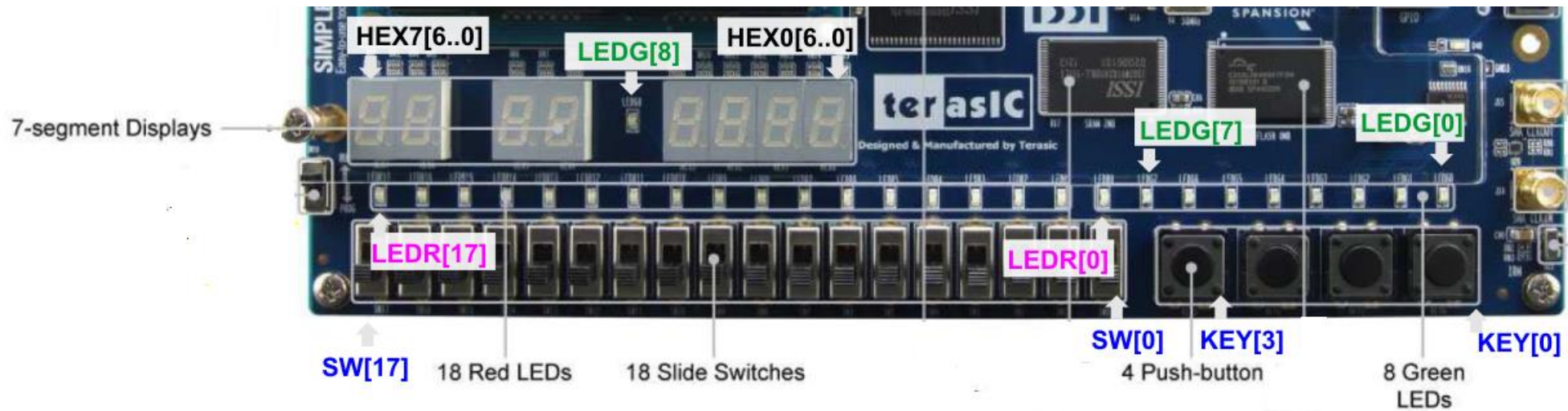
## Selected inputs and outputs of our Veek-MT2 board




### Inputs

- The slide SW[isw] switches give logical '1's when they are up.
- On the contrary, KEY[ik] are in '0's when pressed; otherwise, in '1's.
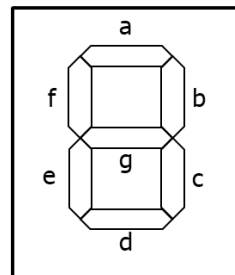
### Outputs

- LEDG[ig] or LEDR[ir] light up when '1' is connected to them
- All HEXn[ix] uses the negative voltage logic. They are lighting up in '0's.



HEXn[ix] / HEXn(ix)							
ix	6	5	4	3	2	1	0
segment	g	f	e	d	c	b	a

On the Veek-MT2, a segment is on, when **HEXn[ix]='0'**.

Note: In block diagram schemas, indexes are enclosed in [], but in VHDL code, they are surrounded by ().