


Logic Systems and Processors

cz:Logické systémy a procesory

Lecturer: Richard Šusta

richard@susta.cz, susta@fel.cvut.cz,
+420 2 2435 7359

Version V1.1 - redrawn slide 20

 

Metastability


 


Image: <https://simple.wikipedia.org/wiki/Latch>


Short pulse-induced metastability

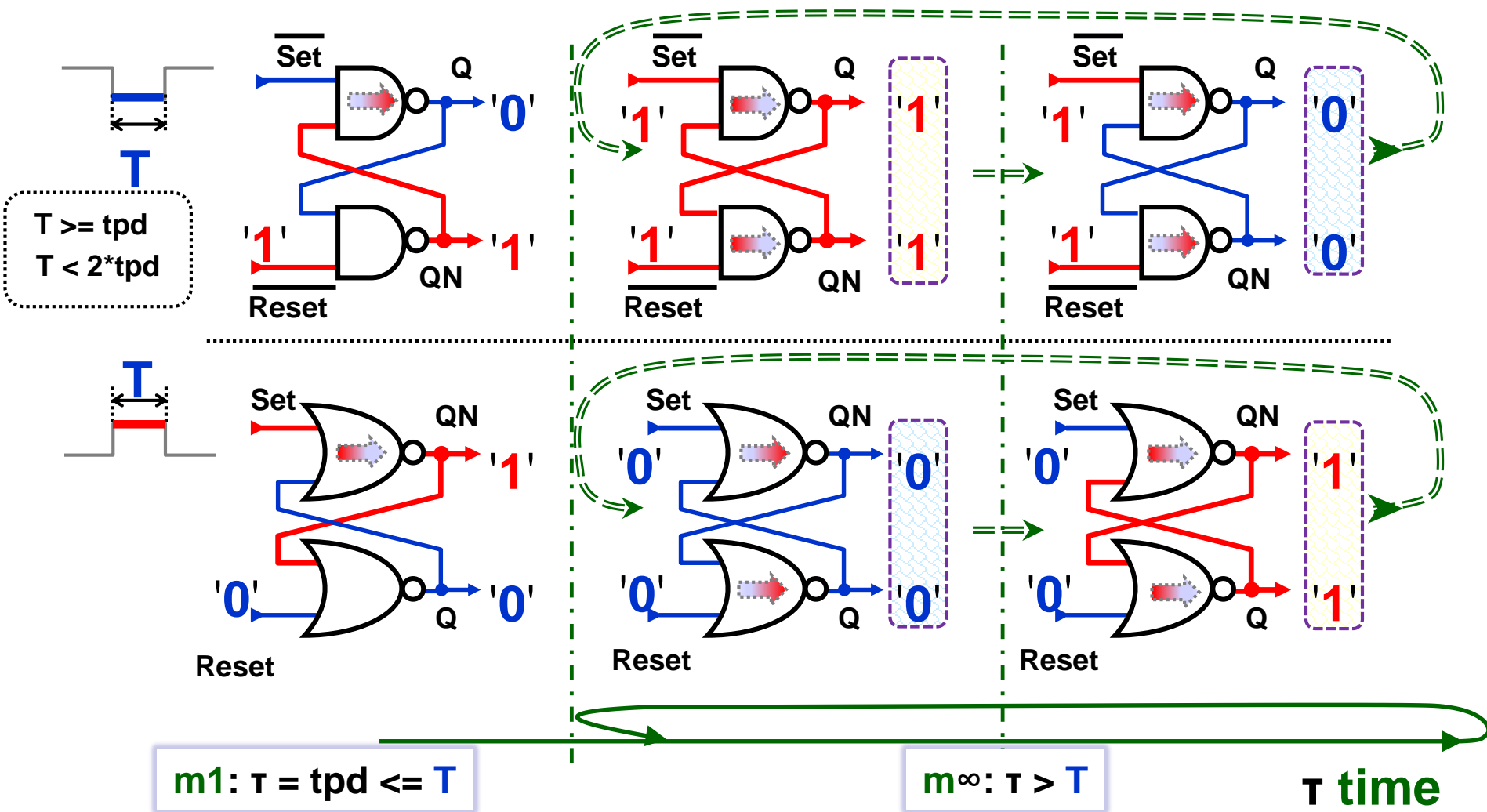


The output of the combination circuit must not be connected to the clock inputs!!!




Stable Loop in D-Latch

 



Transparent

 



Memory

 

  
The risk of metastability has not been eliminated!



Metastability

 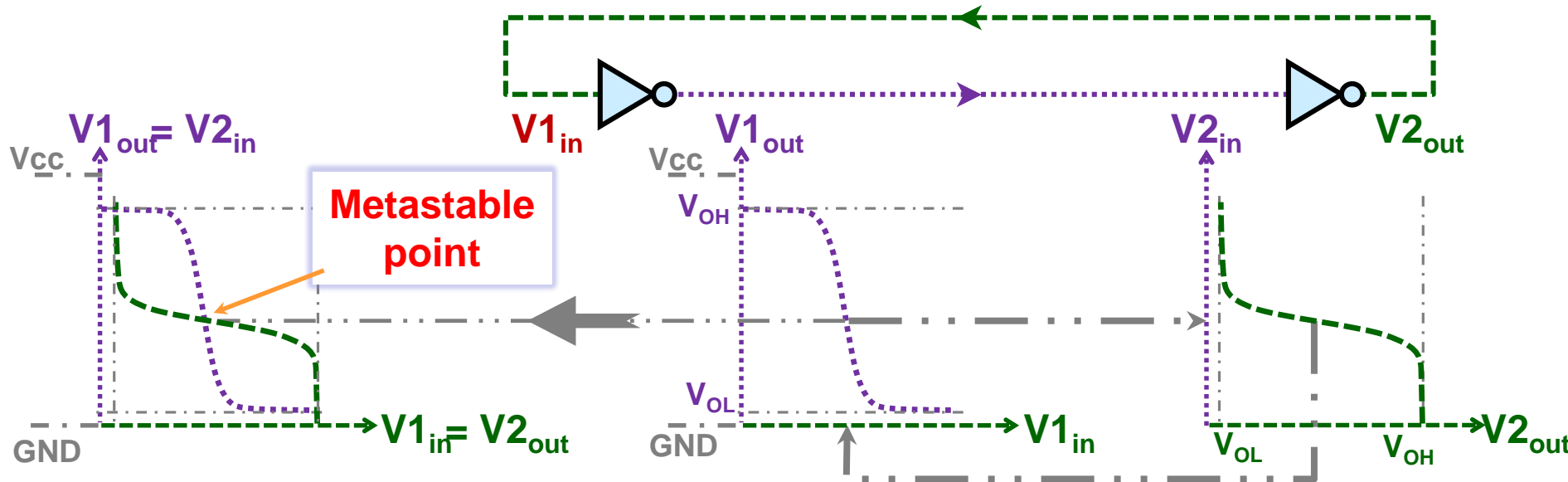

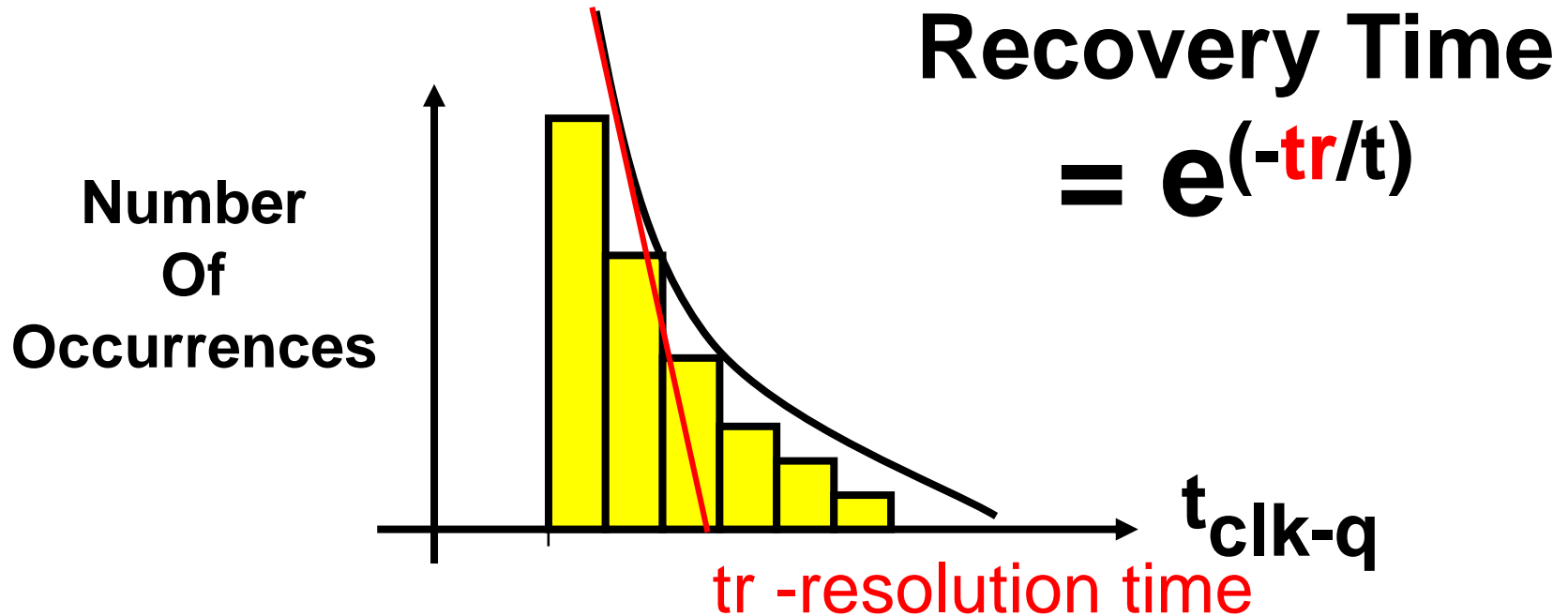- a random variable that depends on the chip technology and has an exponential distribution function;
- its parameter decision time t_r (resolution time) has typical values of about 2 ns for 250 nm technology and below 1 ns for < 60 nm technology.



Manufacturers usually only specify

MTBF = Mean Time Between Failures

(mean time between failures)


which gives considerable value so it looks better, but is just an illusion for terrible designs :-)

The MTBF calculation is more complex and depends on the operating frequencies.

See e.g. Rogina, Branka & Škoda, Peter & Skala, Karolj & Michieli, Ivan. (2010). [Metastability testing in FPGA circuit design using propagation time characterization.](#)

Radioelectronics & Informatics Journal.







51. 4 - 8. 10.1109/EWDTS.2010.5742050.

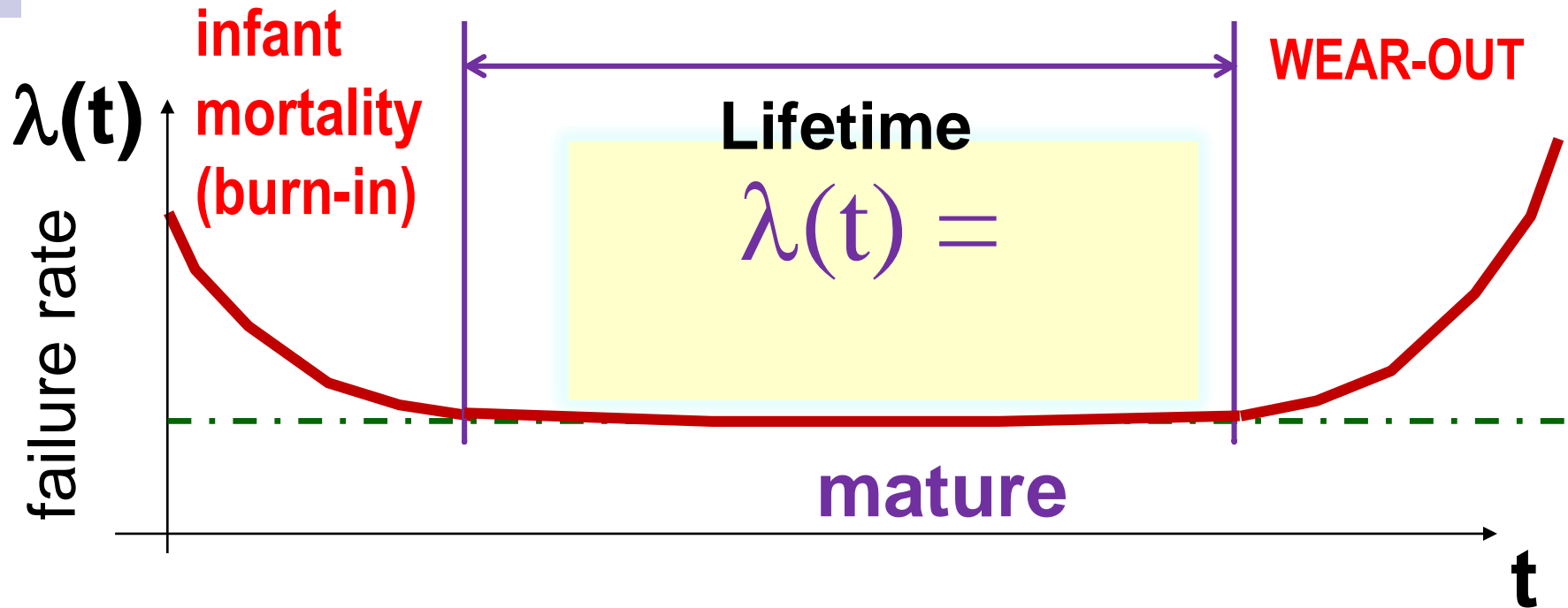

The assumption of constant $\lambda(t)$ (failure rate) in the middle part is based on experience and simplifies the calculations.


Note: In complex systems where high reliability is required, components are first burned in to eliminate the initial part of the curve. Then, their frequent checks prevent the final increase, so their failure rate does not follow the bathtub curve. For a closer look, see, e.g., https://en.wikipedia.org/wiki/Physics_of_failure

DFF or DFFE contains 2 loops

 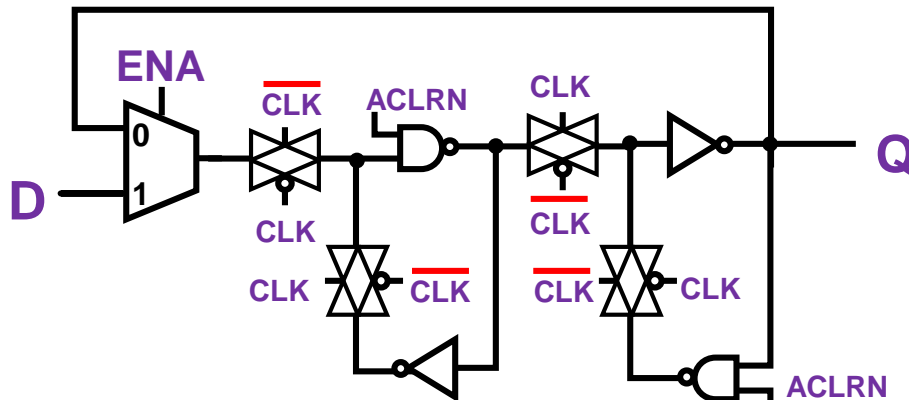  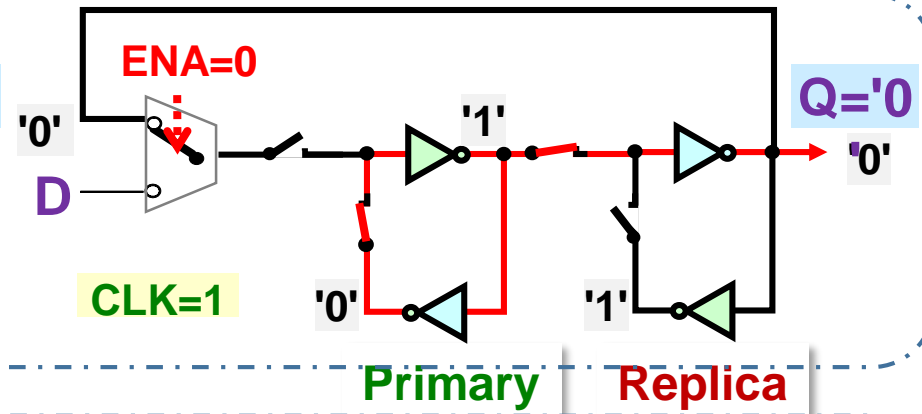 


Asynchronous clear (negative logic)
after power-up

 To prevent metastability, we must meet the circuit operating conditions specified in the manufacturer's catalogs



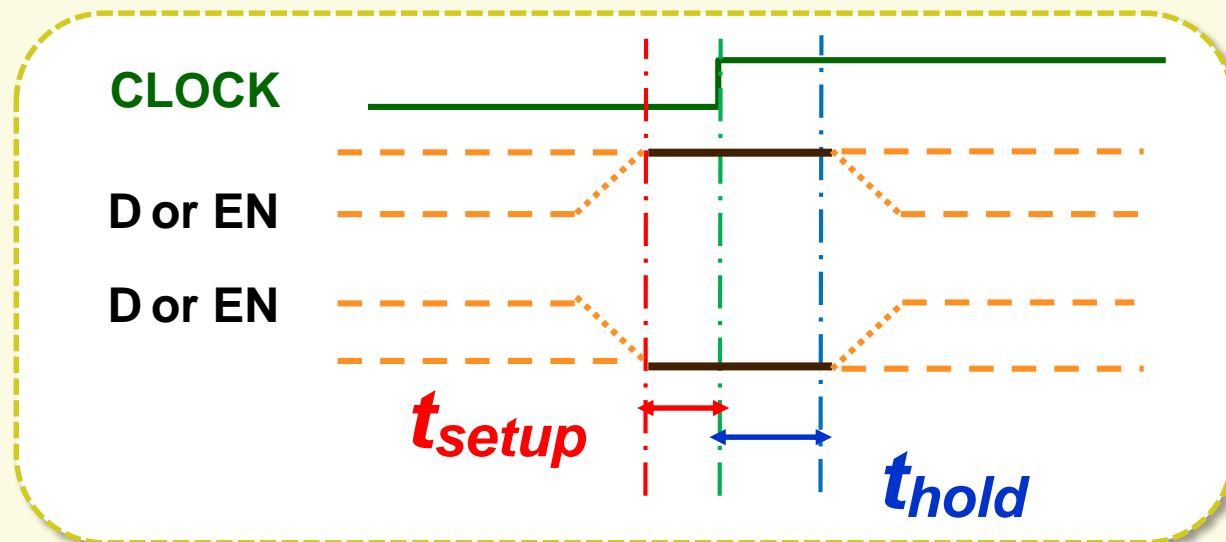- Clocks must be stable for minimum times.
- DFF and DFFE must have stable their D data and EN enable inputs around the rising edges of their clocks.



Some Hardware Abbreviations

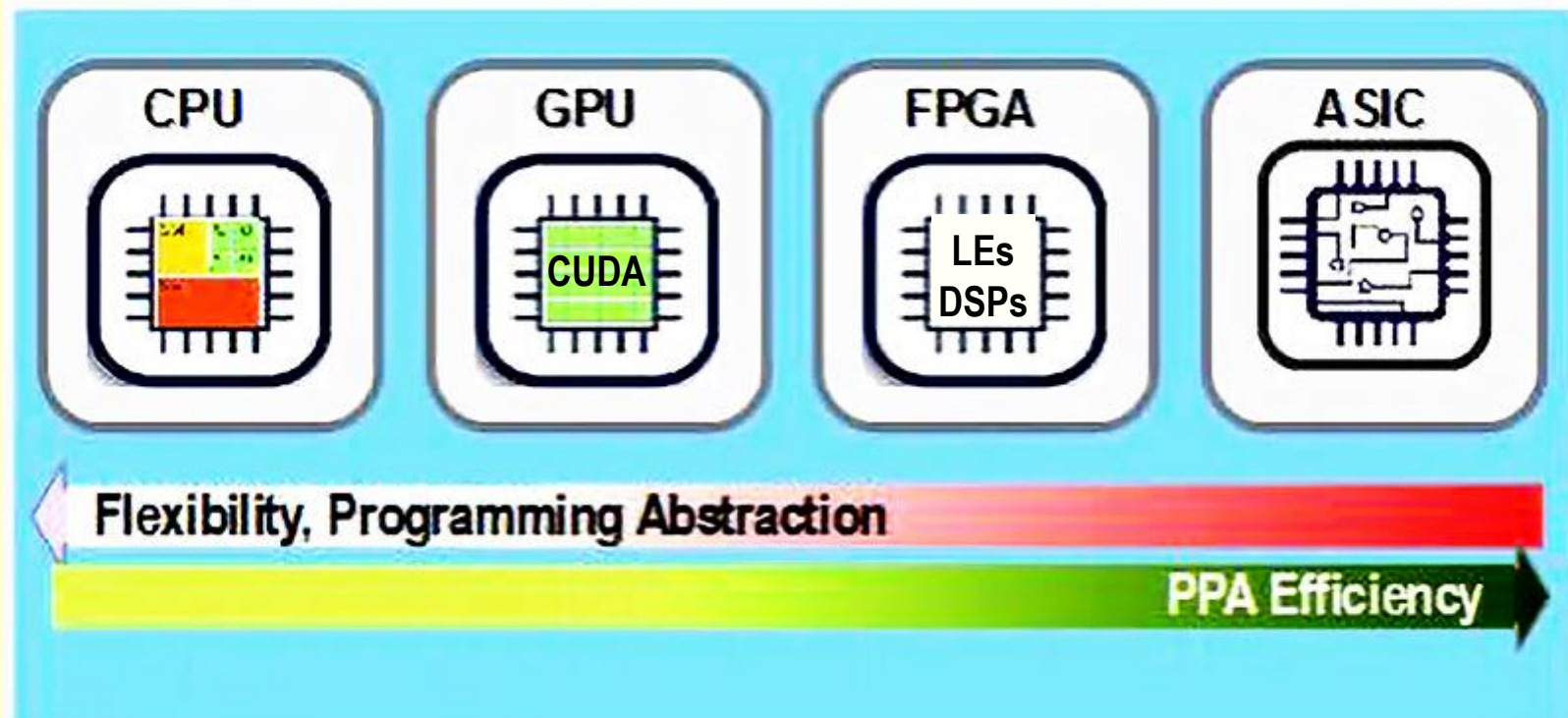


Image: pcbbaa.com

DSP - Digital signal
processor


- ❖ **CPU** - Central Processing Unit aka Processor
- ❖ **GPU** - Graphics Processing Unit
 - ❖ **CUDA** - Compute Unified Device Architecture
- ❖ **FPGA** - Field Programmable Gate Arrays
- ❖ **ASIC** - Application-Specific Integrated Circuit
- ❖ **PPA** - Power, Performance, and Area

- ❑ Float point operations consist of fixed-point binary and an exponent.
- ❑ If we do not have float-point hardware support in DSP blocks of our FPGA, we should prefer faster fixed-point arithmetic.
- ❑ For float point, we can insert soft core float point support, e.g., https://github.com/hVHDL/hVHDL_floating_point

Fixed-points represent rational numbers

Rational numbers can be expressed as **quotients or fractions** = $\frac{n \text{ (numerator)}}{q \text{ (denominator)}}$ where n and q are integers

Binary fixed-point numbers:

 

$$x = \sum_{k=-j}^i b_k 2^k$$

Integers can be considered as special fixed-point cases with $b_k = 0$ for $k < 0$.



- $9/8$
- $29/4$
- 75.75

- ❖ 0.1 by multiplying 2, we never obtain an exact integer
 $0.1, 0.2, 0.4, \dots$ have always inexact representations

- Add and subtract numerators with the same denominators:

$$\frac{X}{q} \pm \frac{Y}{q} = \frac{X \pm Y}{q}$$

- Corrections are necessary after multiplications or divisions

- **Multiplication 2:** *shift left*, **Division 2:** *shift right*

- **Log₂ N:** can be found efficiently by shifts and squares,


https://en.wikipedia.org/wiki/Binary_logarithm

(Paragraph: Iterative approximation)


- Sine, cosine, logarithm: *tables*




Fixed-Point Tricks in FPGA

 

 
"According to my calculation, you should not drown... at least I think so"



"It's an inexact science."

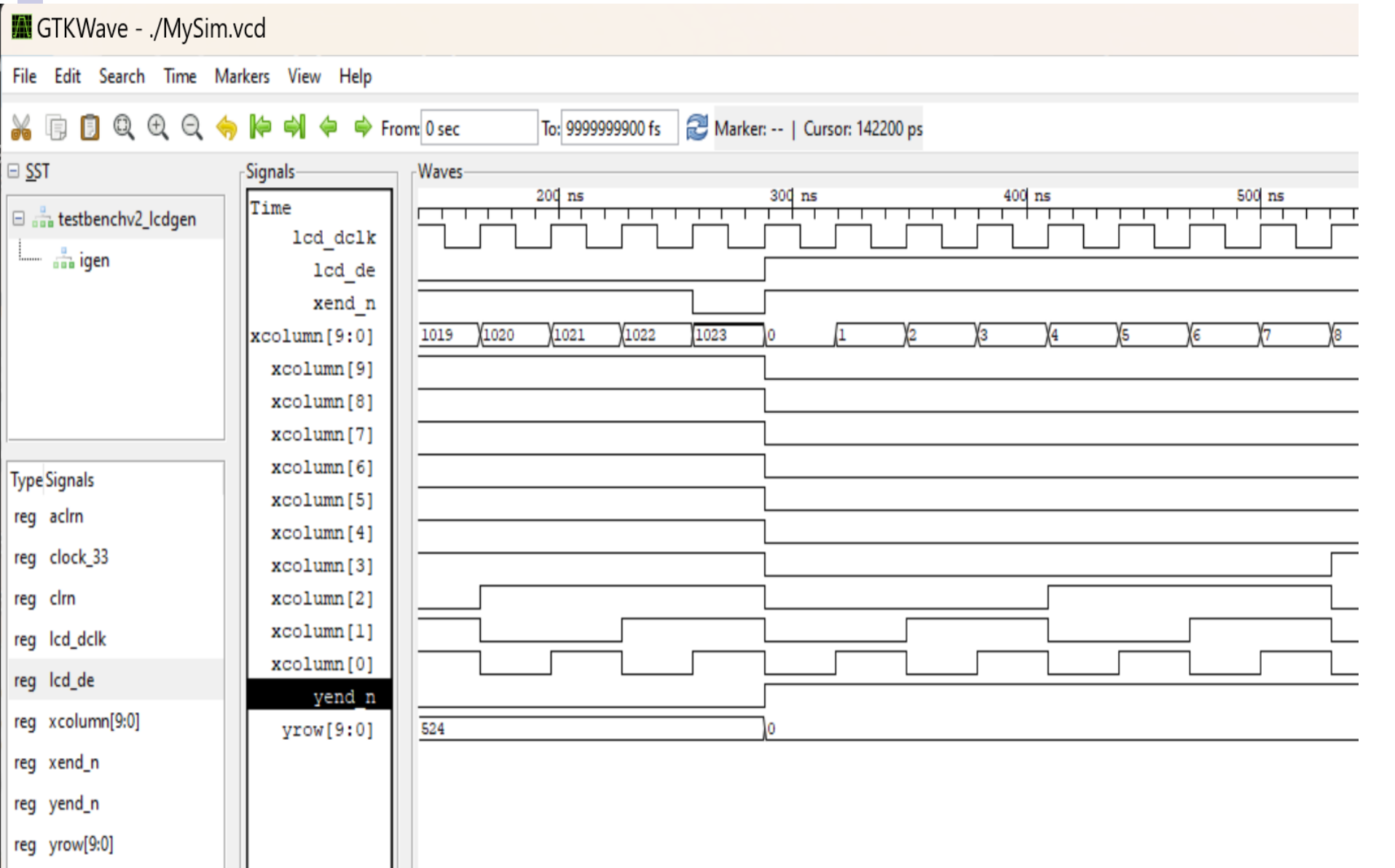

 1D linear transformation: translate + scale



$$i_x = ((x_c - offset) * N) / Q$$


$$x_c = (i_x * Q) / N + offset$$

In circuits, we better divide by powers of 2,
so we select N and Q according to our calculations.

Let: offset=0; **N** = 7; **Q** = 16 ($=2^{**}4$)


1. By multiplication: $x=(xcolumn*7)/16$

2. By a continuous counter

LCD_DCLK 

xcolumn = xt	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	...
counter = 7*xt	0	7	14	21	28	35	42	49	56	63	70	77	84	91	98	...
counter / 16	0	0	0	1	1	2	2	3	3	3	4	4	5	5	6	...

3. By a limited counter

LCD_DCLK 

xcolumn = xt	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	...
counter = (7*xt) mod 16	0	7	14	5	12	3	10	1	8	15	6	13	4	11	2	...
(7*xt) / 16	0	0	0	1	1	2	2	3	3	3	4	4	5	5	6	...

$$3=19-16$$

$$6=22-16$$

$$2=20-16$$

$$5=14+7-16=21-16$$


$$1=17-16$$

$$4=20-16$$

```


process(xcolumn,yrow)
variable RGB :
  RGB_t:=BLACK;
begin -- process
  if 16*yrow > 7*xcolumn
    then RGB:=YELLOW;
    else RGB := DARKBLUE;
  end if;
  RGBcolor <=RGB;
end process;

```


 


We do not see irregularity until we zoom the image.


xcolumn	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	...
x	0	0	0	1	1	2	2	3	3	3	4	4	5	5	6	...

 

Viewer of LCD T

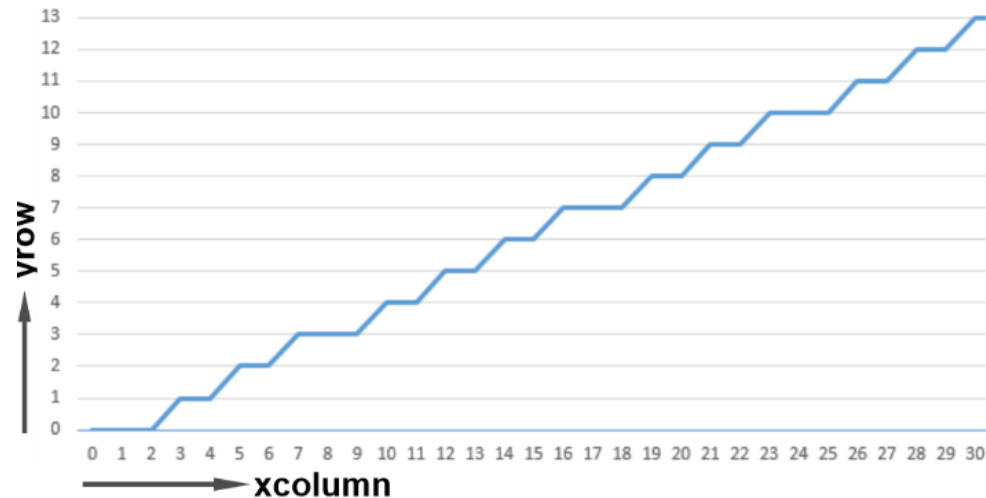 

 - The LCD has its y-axis reversed, i.e., from top to bottom.
- The classic graph has a rising y-axis when showing the counter above.



□ Lines allow any $Q > 0$.

```
x := to_integer(xcolumn); y := to_integer(yrow);
RGB := DARKBLUE;
if 37*y > 7*x then RGB:=VIOLET; end if;
if 29*y > 7*x then RGB:=RED; end if;
if 23*y > 7*x then RGB:=AQUA; end if;
if 19*y > 7*x then RGB:=GREEN; end if;
if 16*y > 7*x then RGB:=YELLOW; end if;
```

- If we do not need modulus then limited counters have lower complexities for any integer $Q > 0$.
- But divisions and continuous fixed-point counters have acceptable complexities only for $Q = 2^K$, where $K \geq 0$.

This example also discovers that the **GHDL** performs simulations much **faster with integers** than with unsigned or signed.

Morse Enlarged by Fixed-point Counter

```

10
 9
 8
 7
 6
 5
 4
 3
 2
 1

```




DECOMPOSITIONS

**into more parts can require
mutual communications**

Clock synchronisation

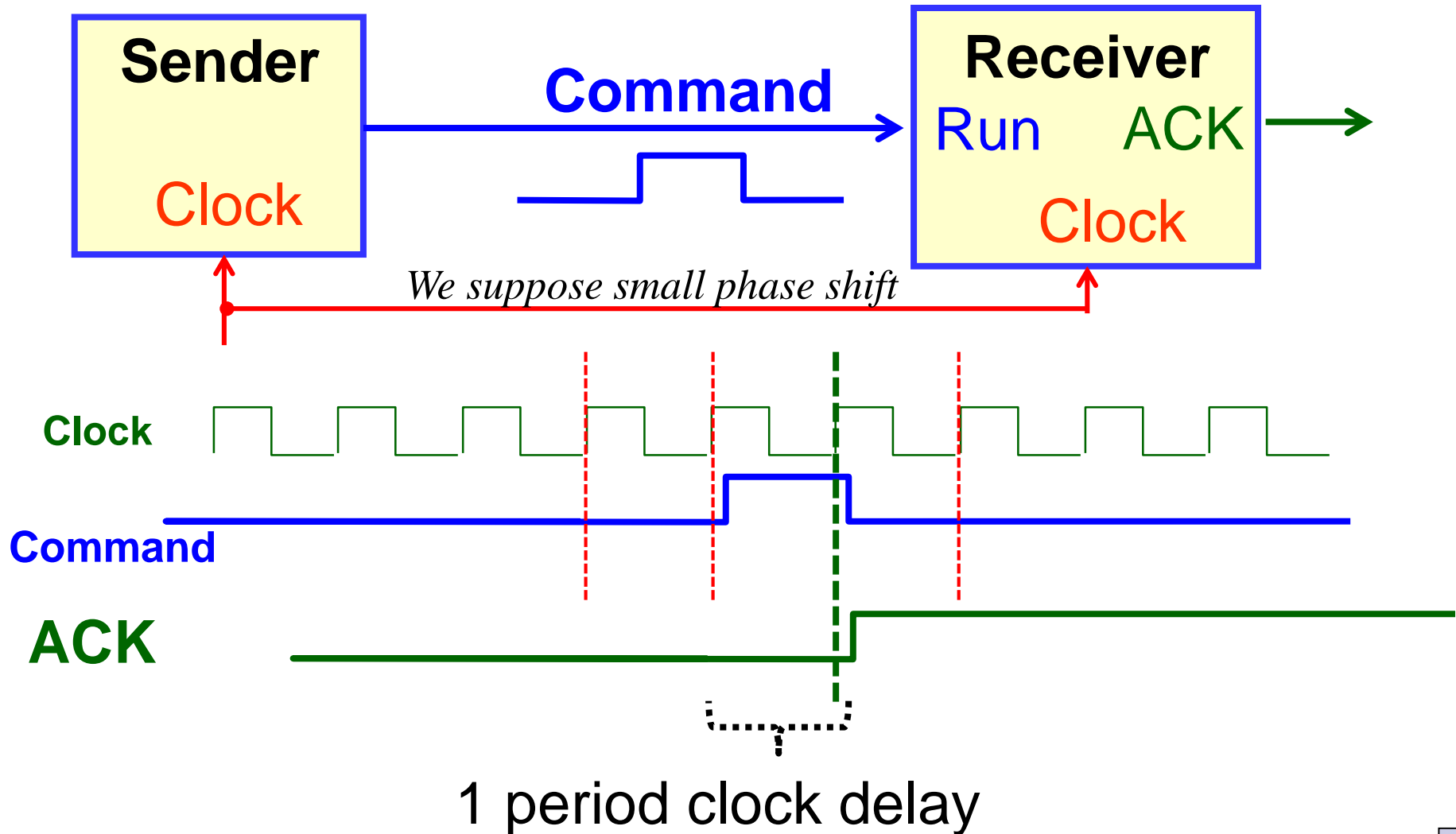We depend on two clocks, assuming that the receiver is always ready :-)





Synchronous command with clock input

■ Advantages:


- ☐ Simple.
- ☐ Suitable for receivers with fast response times that always wait for commands.

■ Disadvantages:

- ☐ A small window for correct command recognition.
- ☐ The solution depends on the exact phase of the clock.
- ☐ Missing verification that the receiver is ready to accept the command.

READY

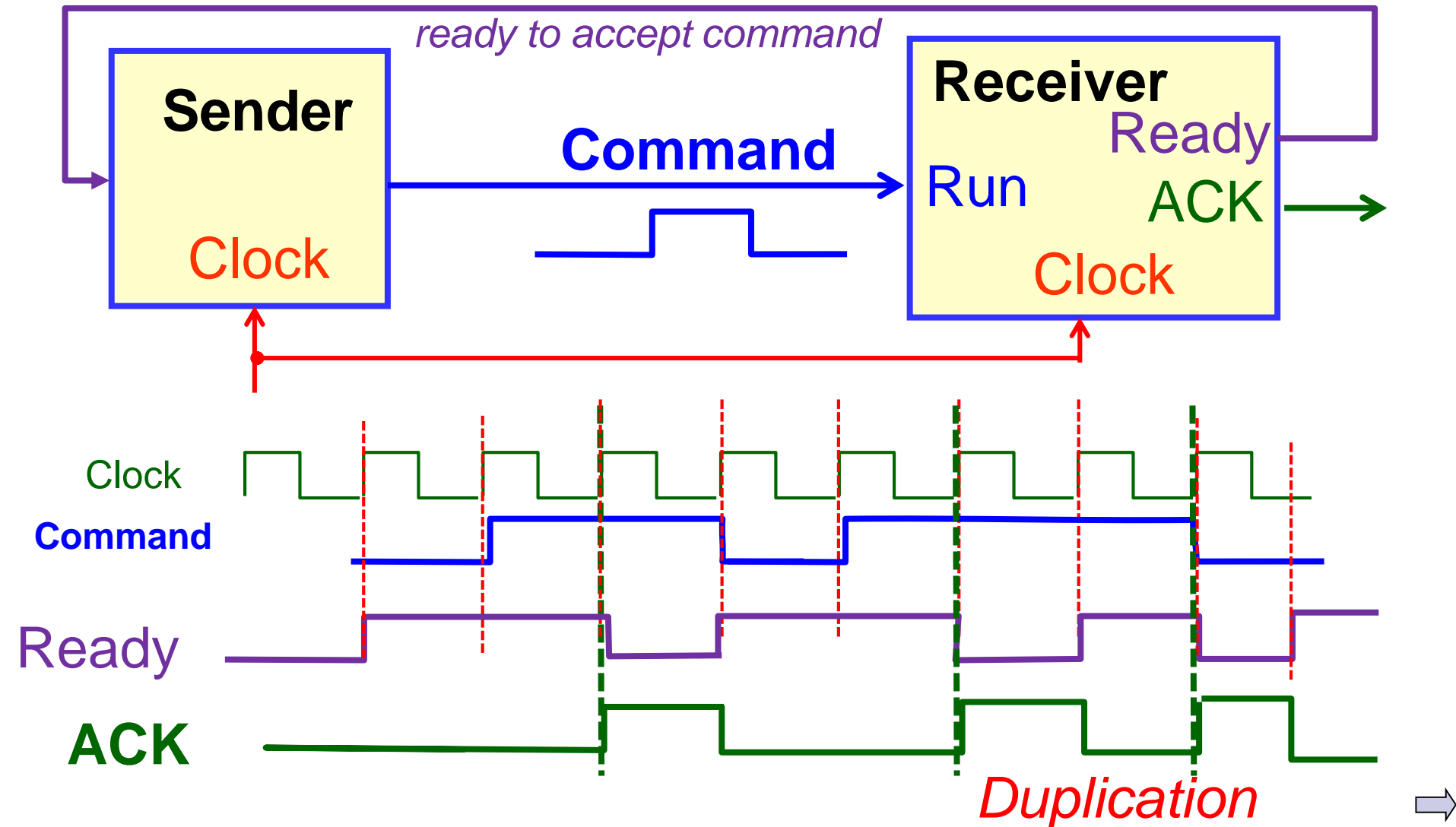Again, we have a dependency on the same clock.
The command must last only an appropriate time:-





Enhancement by READY


■ Benefits

- ☐ Reducing the risk of losing commands.

■ Disadvantages

- ☐ Only applicable when a sender and a receiver have the same clock.
- ☐ If the sender deactivates the command too late, it is accepted multiple times.
- ☐ Delay in the receiver response by multiple clock pulses.

Edge Detection

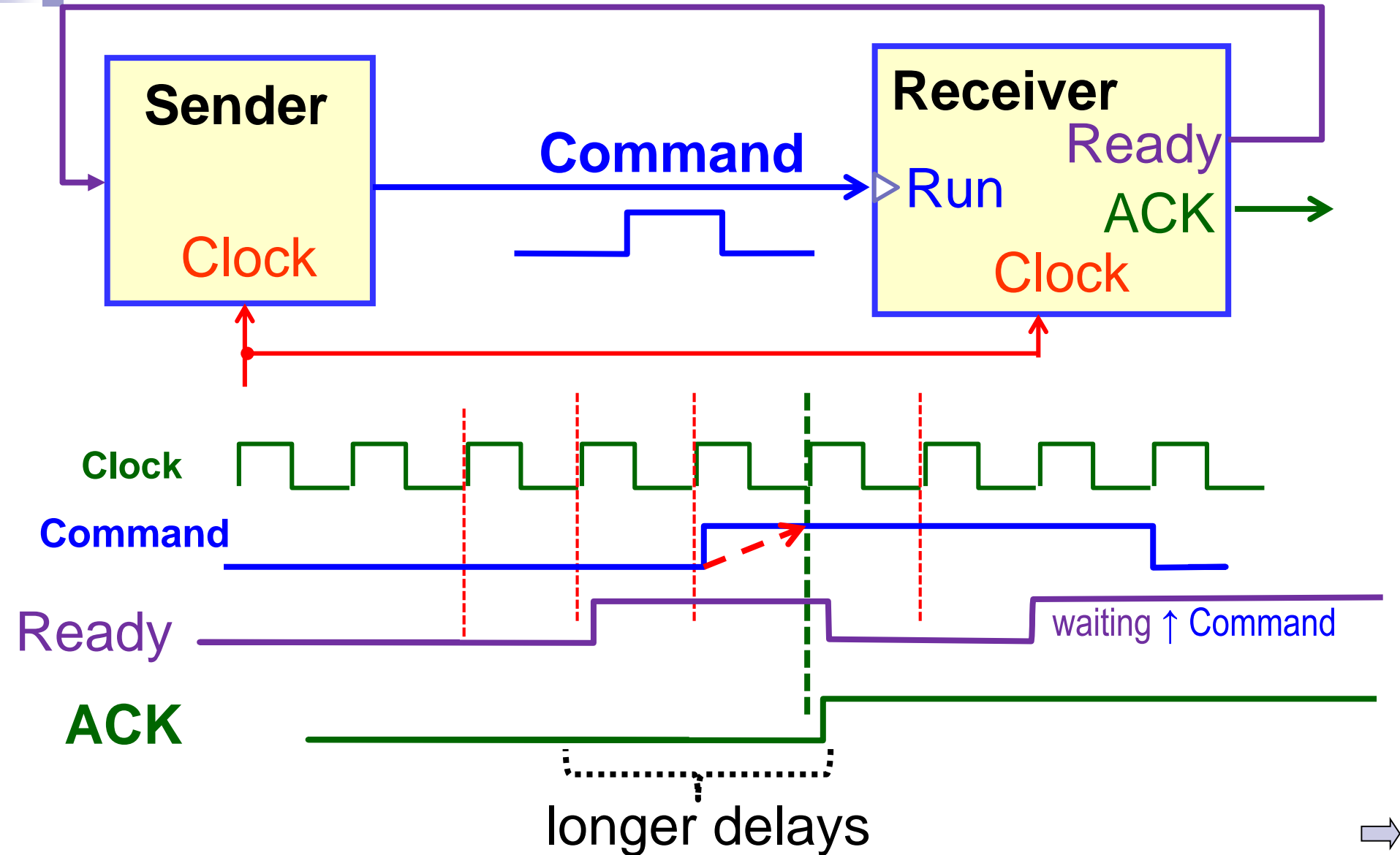



Enhancement by edge detection command

■ Benefits


- ☐ A very robust solution.
- ☐ Senders transmit commands only when the receivers are ready to accept.
- ☐ Receivers detect the rising edge of commands by comparing them with previous values, thus avoiding false repetitions.

■ Disadvantages


- ☐ We still need the same clock.

Clock domain

 a set of synchronous signals with the same clock



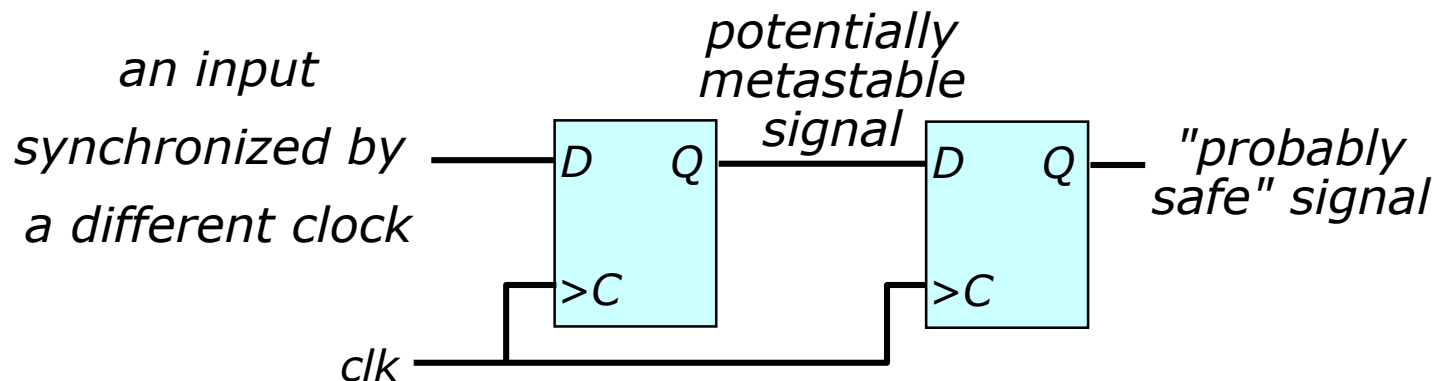Crossing clock domain boundaries requires synchronizers for isolating metastability




Even the Morse Code Buzzer contains a Synchronizer

```


signal soundOnNeg, soundOnNeg0 : std_logic;
begin --architecture
  process(f18_432MHz)
  begin -- Synchronizer for crossing clock domains
    if rising_edge(f18_432MHz) then
      soundOnNeg <= soundOnNeg0; soundOnNeg0 <= not SoundON;
    end if;
  end process;
end architecture;

```

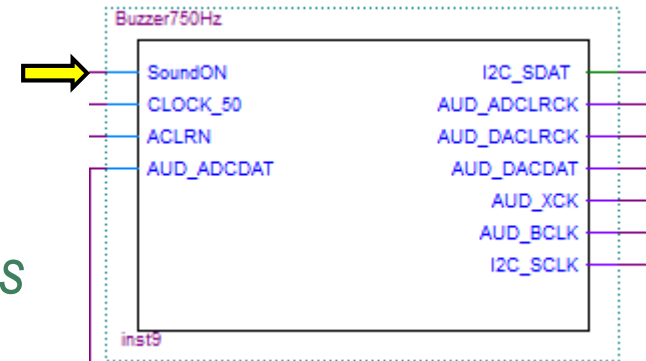

We synchronize here between CLOCK_50 domain (50 MHz) and the audio clock domain 18.432 MHz

RTL Viewer

 

Time Quest Analyzer Report


Slow 1200mV 85C Model Metastability Report

MTBF Summary		Synchronizer Summary	
	Source Node	Synchronization Node	
1	ShiftLeft18:inst2 \pshift:rg[0]	Buzzer750Hz:inst9 Buzzer:inst_Buzzer soundOnNeg0	

Synchronizer Chain #1: Worst-Case MTBF is Not Calculated

Chain Summary		Statistics	
	Property	Value	
1	Source Node	ShiftLeft18:inst2 \pshift:rg[0]	
2	Synchronization Node	Buzzer750Hz:inst9 Buzzer:inst_Buzzer soundOnNeg0	

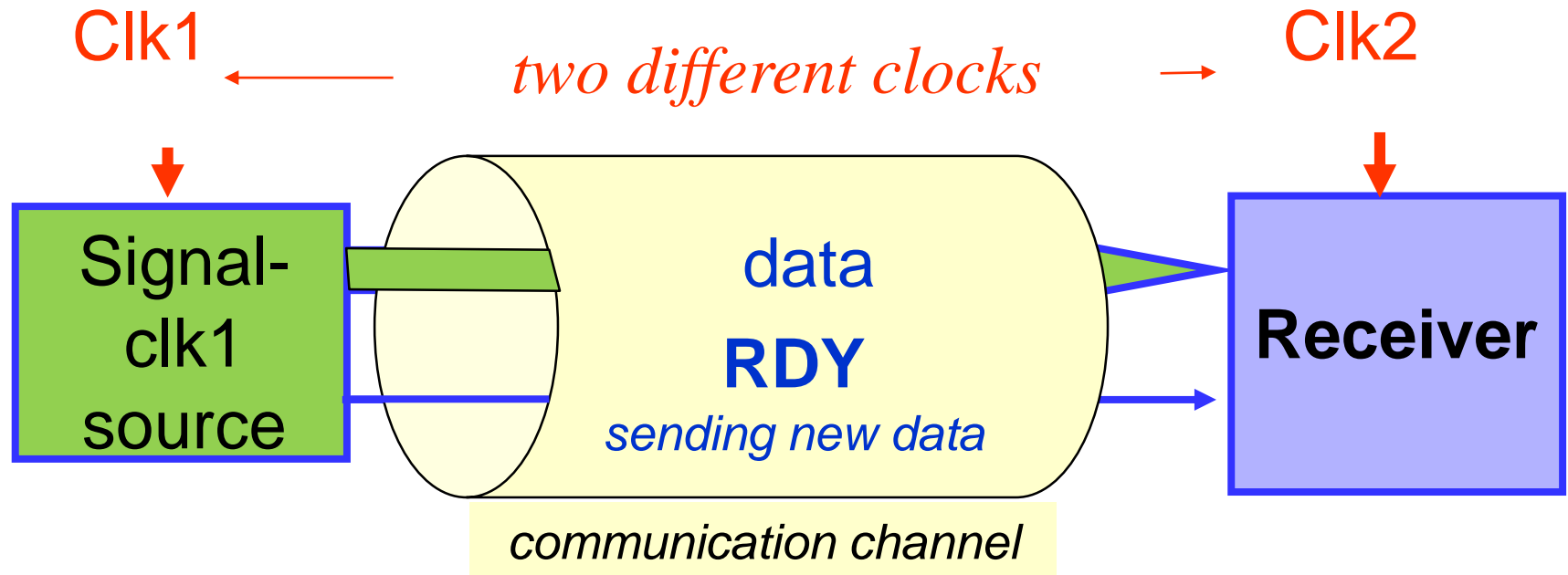Transfer between devices with different clocks



Sending without implicit confirmation.

We assume either a fast response from the receiver or a command input queue (FIFO) implementation.


*Similar to the UDP network protocol
(UDP - User Datagram Protocol)*





Hand-shaking

data are synchronous with Clk1


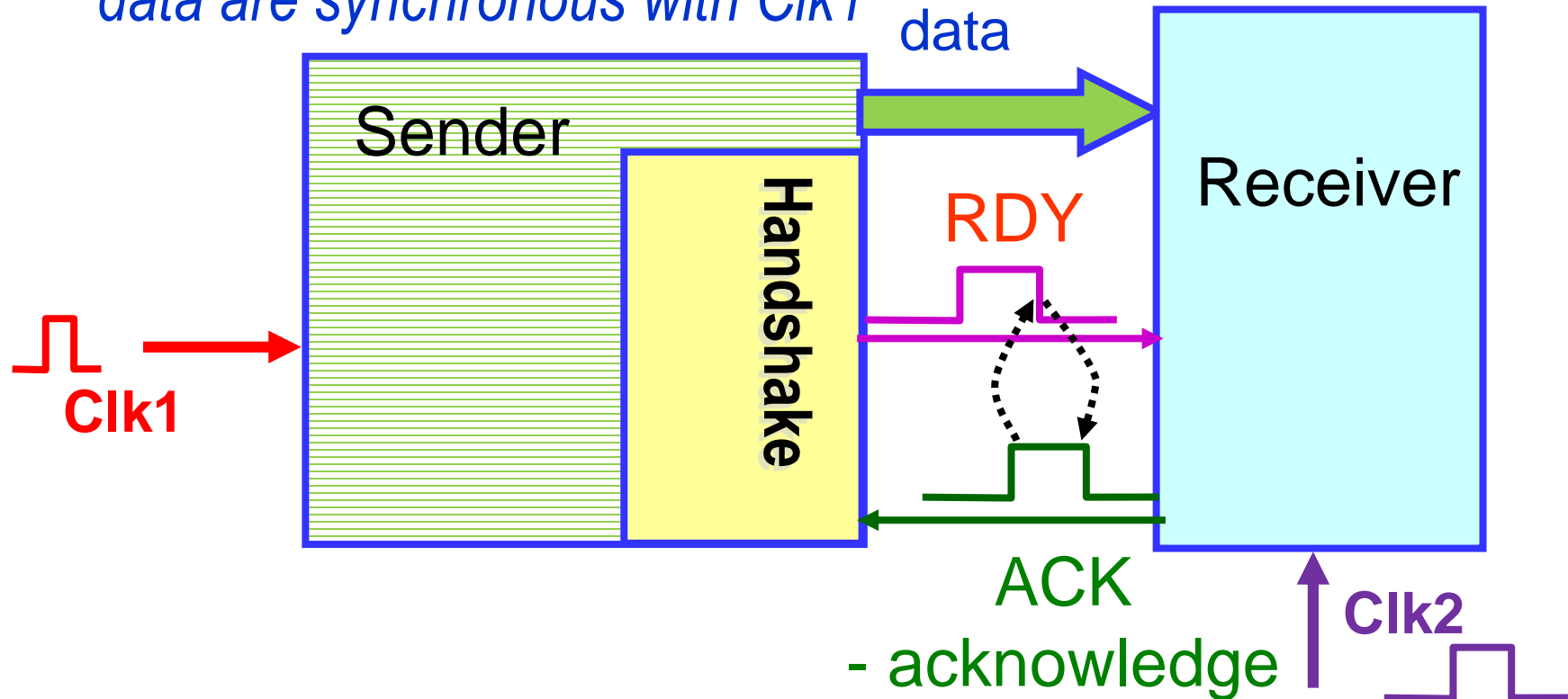


Positively confirmed transmission (hand-shaking)
analogy of the TCP network protocol
(Transmission Control Protocol)





Handshake

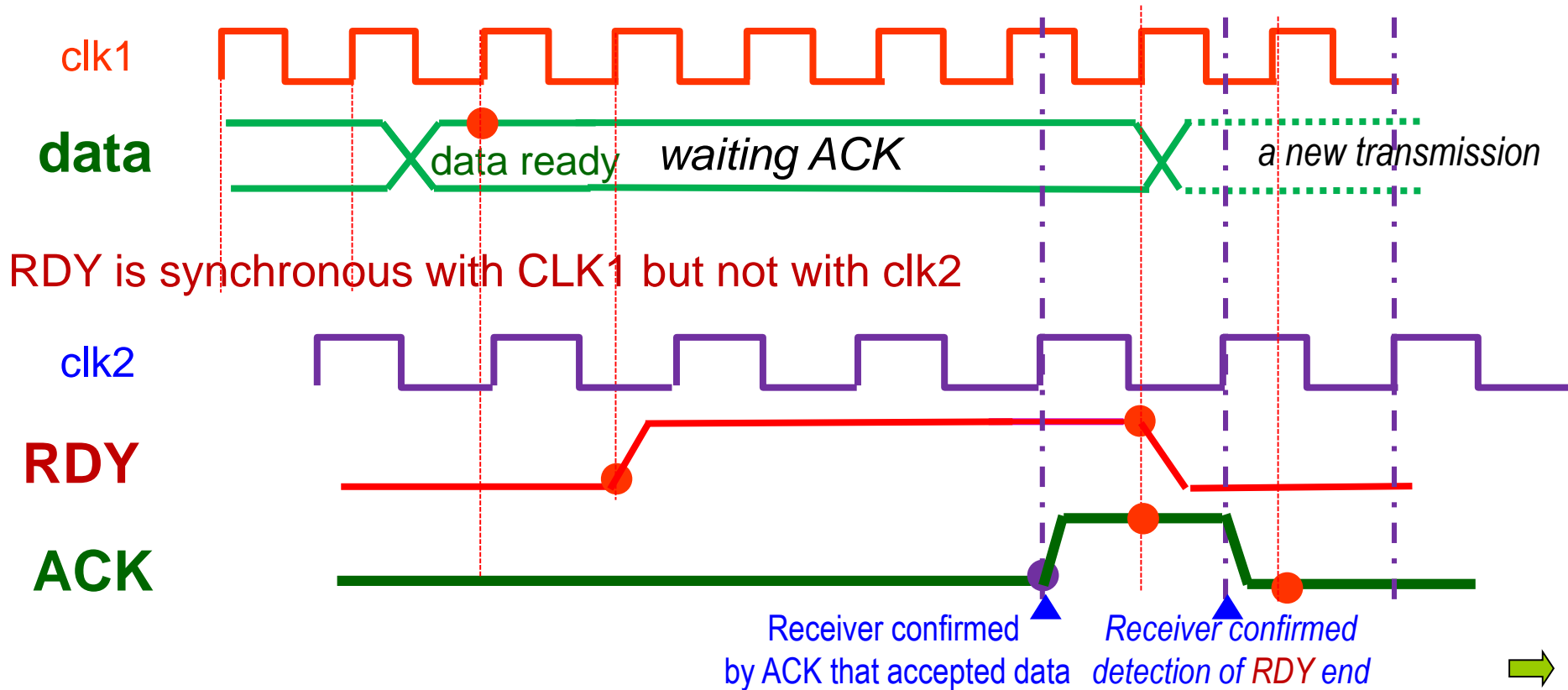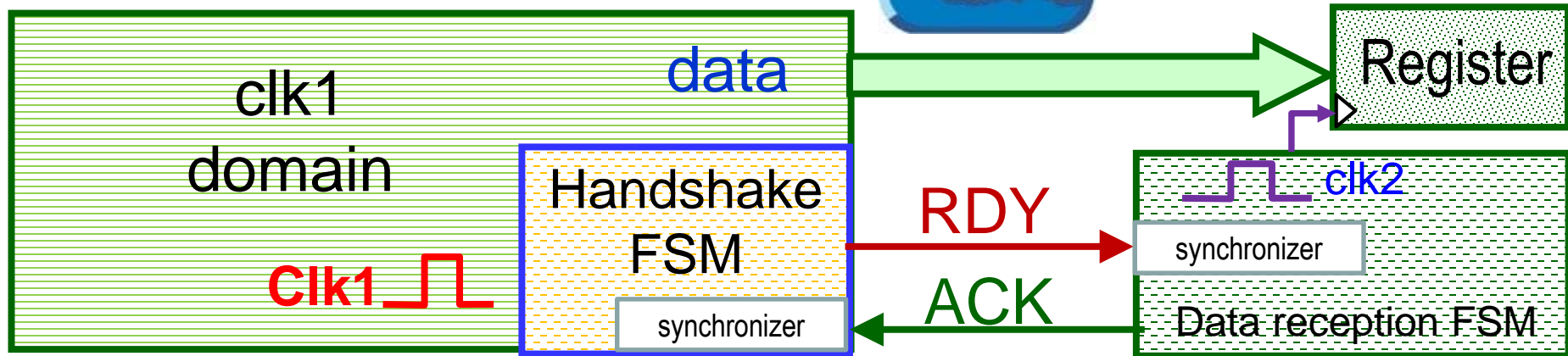

Forbidden Structures



- Asynchronous Counters (Ripple Counter)
- Asynchronous input priority violation
- Dependency on the double clock


Ripple Counters 2^n

cz: asynchronous counters

Simple counters,
but with phase delays...

Asynchronous and Synchronous



asynchronous chain

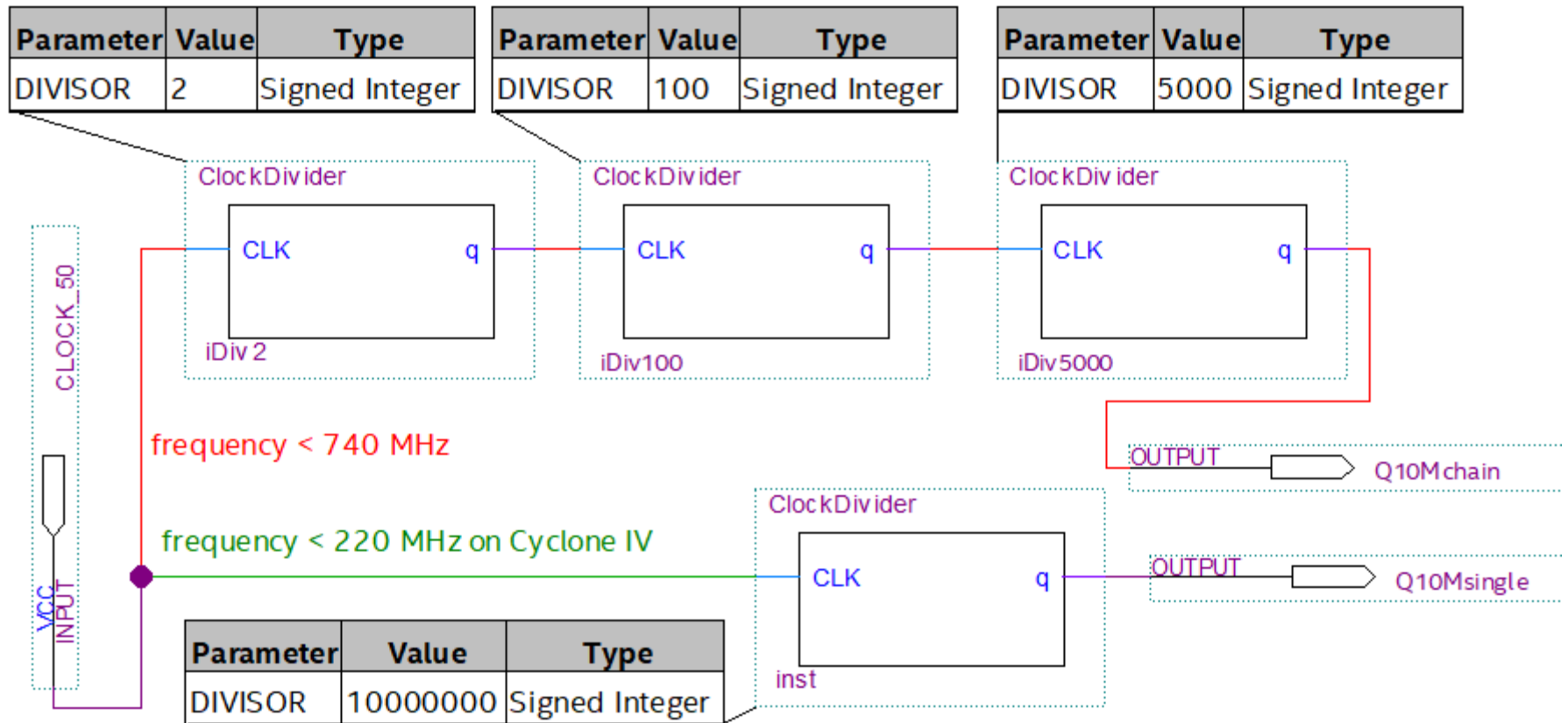

synchronous

4-bit Ripple counter

cz: asynchronous counter

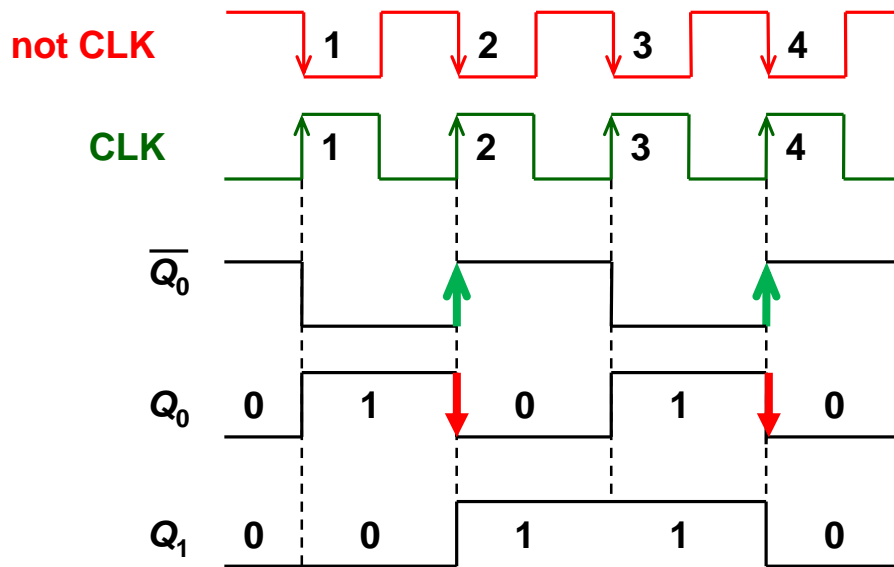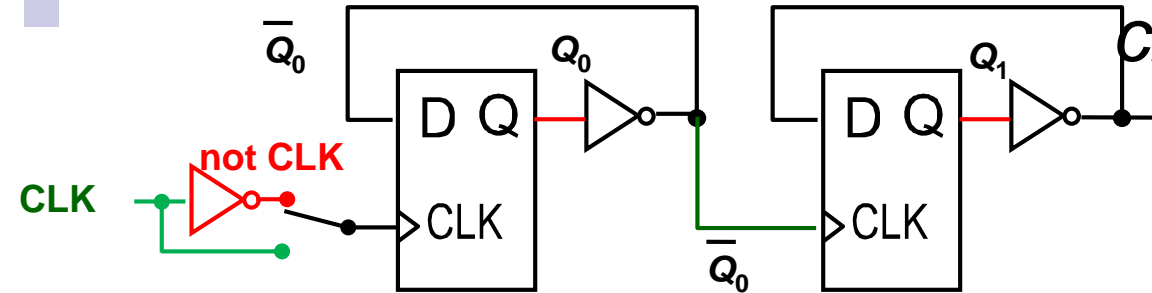

Timing diagram


00 → 01 → 10 → 11 → 00 ...

The first DFF can operate on the rising or falling edges of the clock signal, depending on our needs, but subsequent DFFs must knock on the falling edges to count up. This follows from the binary sequence = its high bit changes to the opposite just as the low bit goes from 1 to 0.




Frequency counter/gunner 16


Reading up

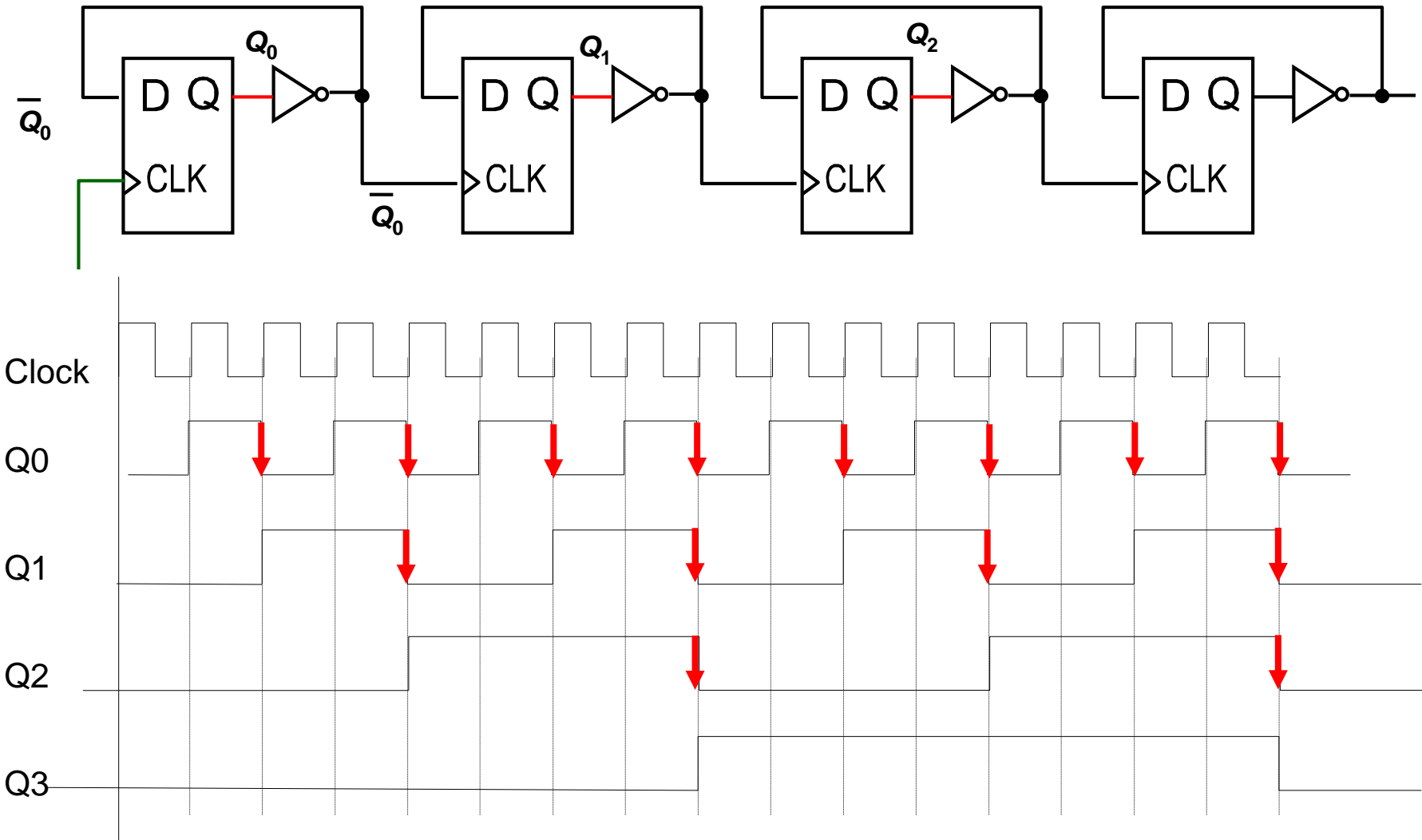

Counter down

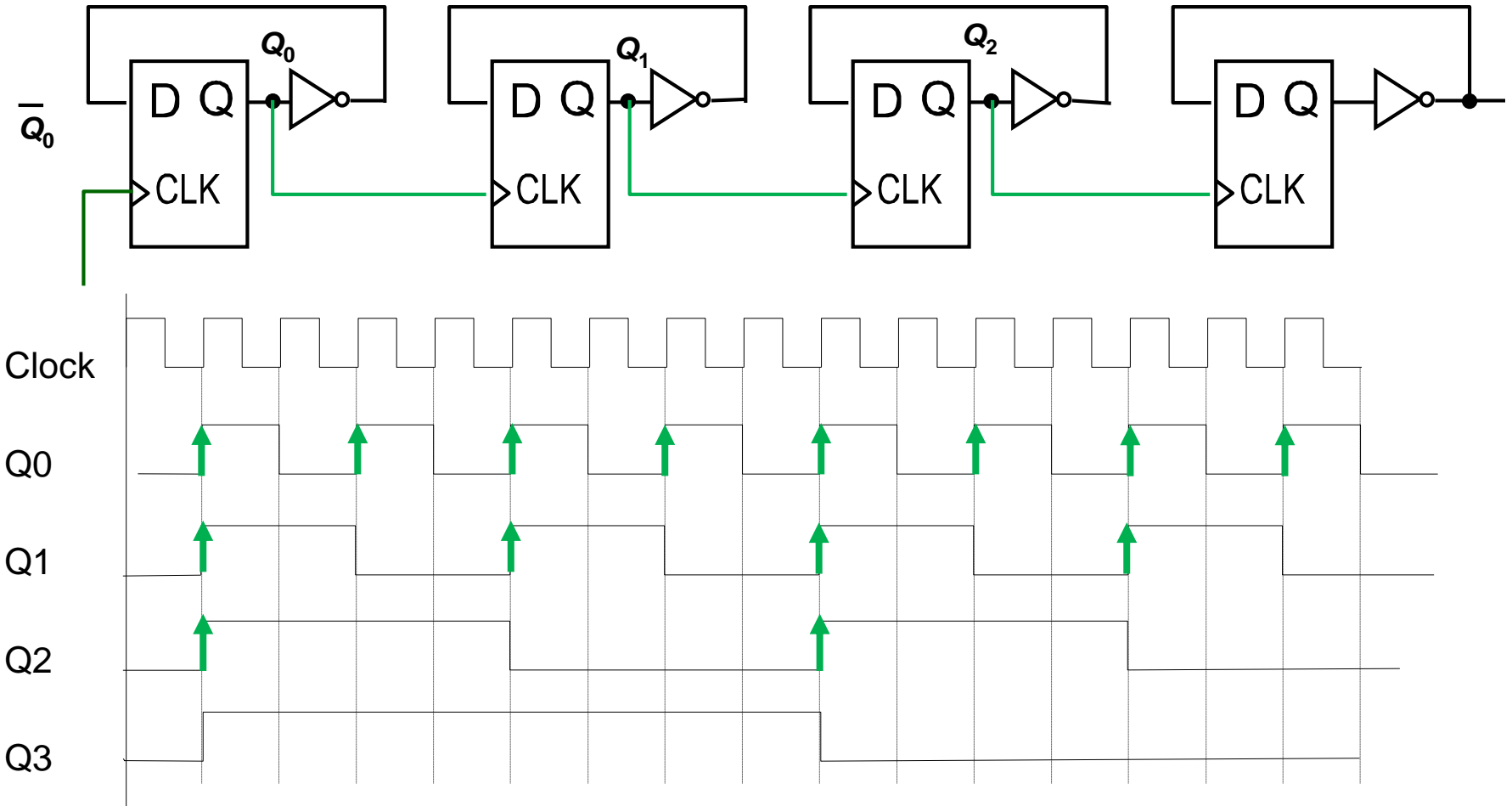

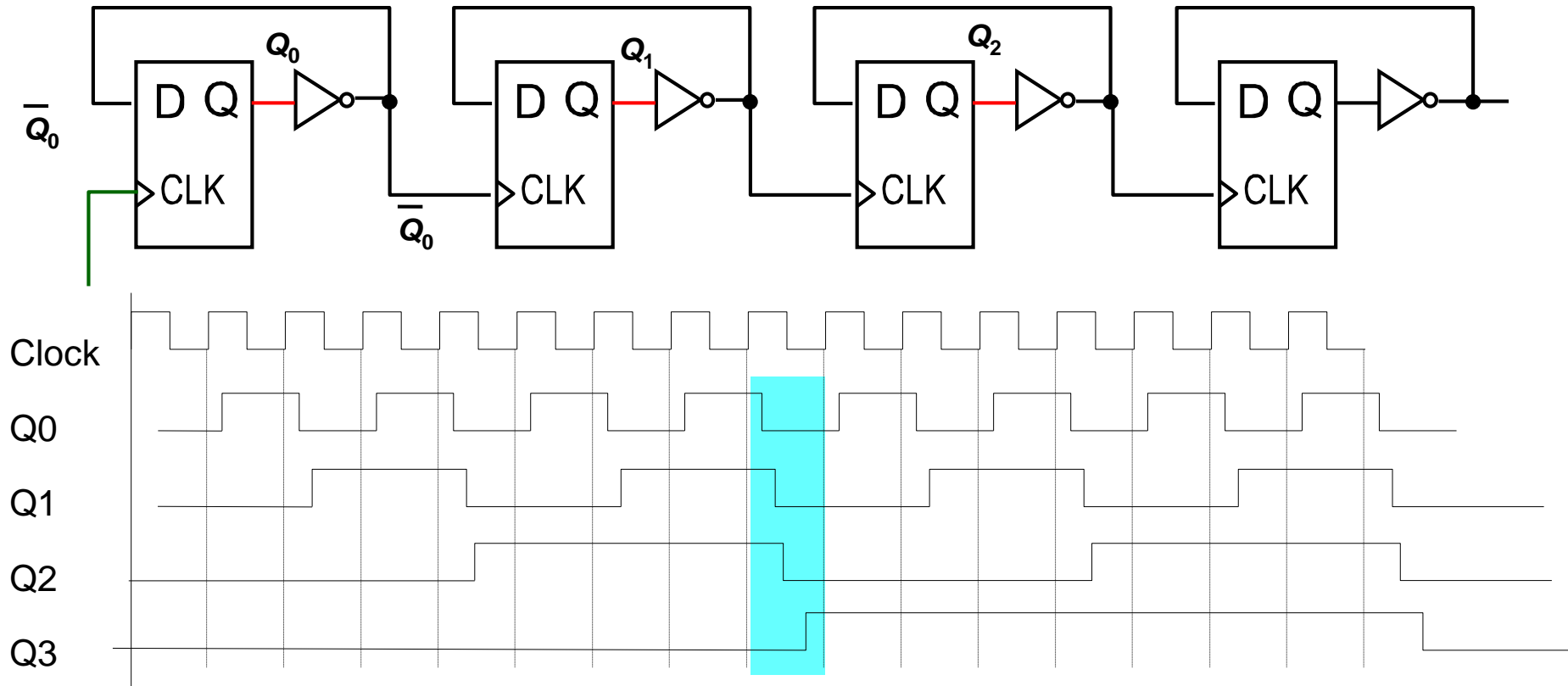
The disadvantage is the increasing delay of outputs



Intermediates - GRAY'S CODE 0111→0110→0100→0000→1000

0111 > 0110 > 0100 > 0000 < 1000

Synchronous versus asynchronous counter

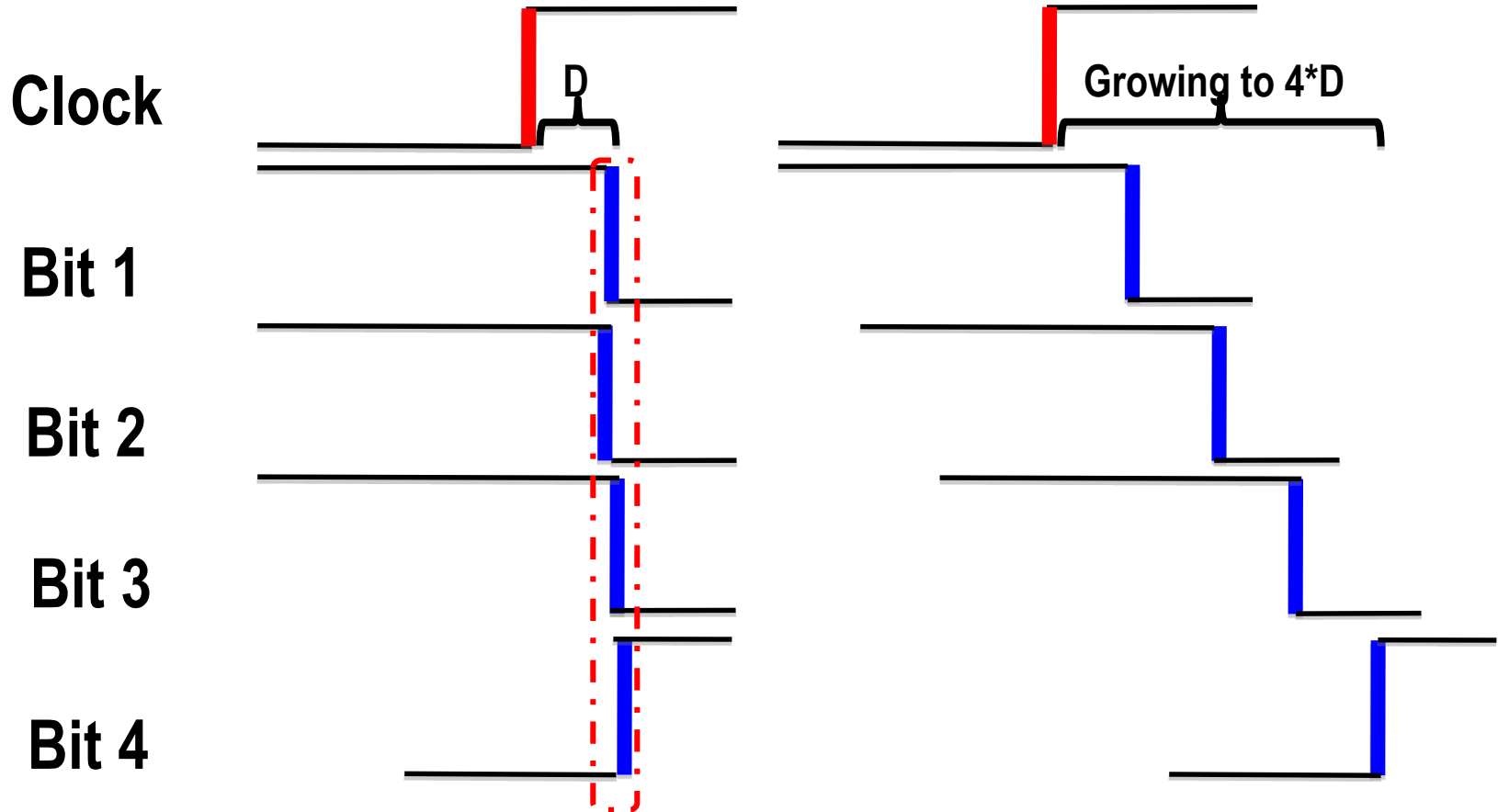

Slight phase shift


*The outputs of the synchronous counter are admittedly knocking in a short time interval, but **not all at once!!!***

Significant phase shift

They are slowed down by their load (fan-out).

Obsolete asynchronous dividers

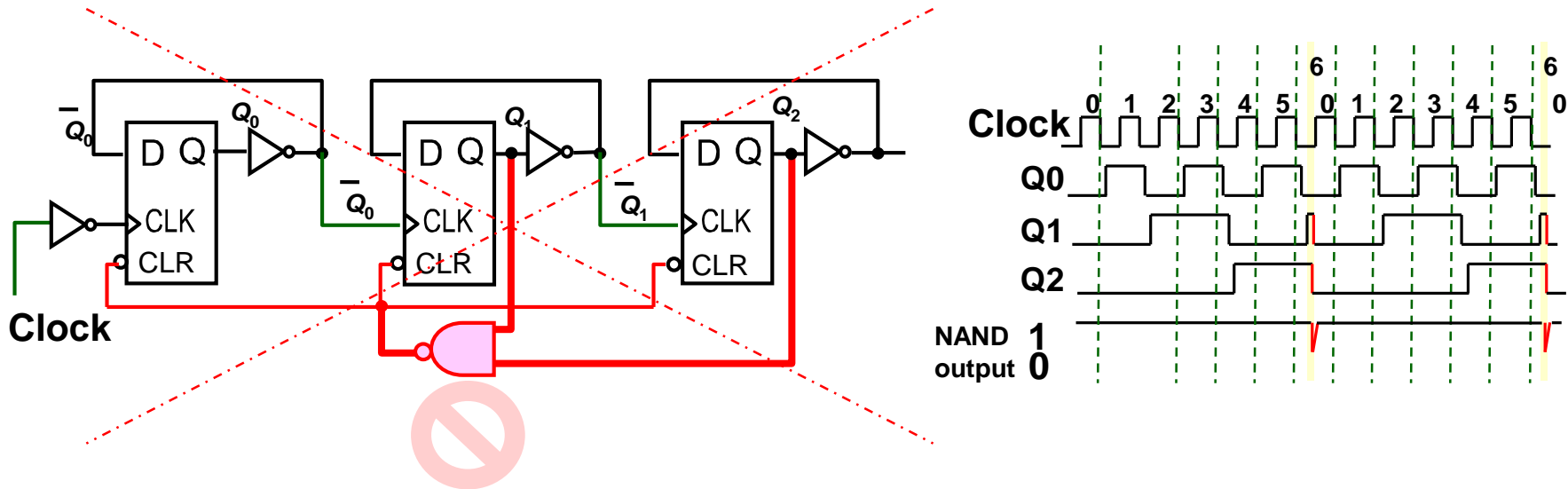
- Beware of schematics on sites where asynchronous inputs are used as working inputs. All such circuits refer to older TTL logic that was slower and did not respond to short gambling pulses.




Older design of TTL divider 6 - nowadays risky !

- On fast logic, i.e. all of today's, inputs with asynchronous behavior are used exclusively for initialization after power-up.
On VEEK-MT2 boards, they are connected to the **KEY[0]** signal.

Proper Propagation Logic for Counters

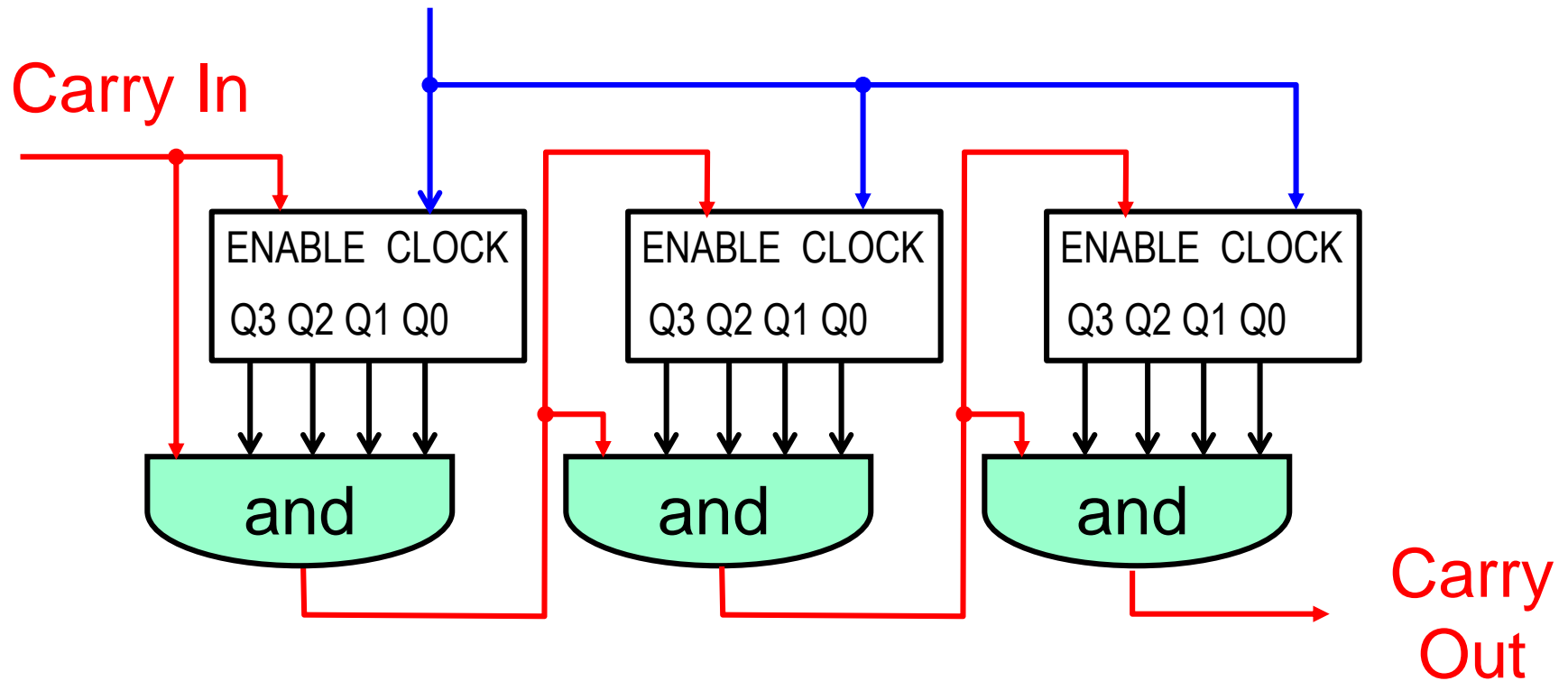

High-frequency divider by 10M (1/4)

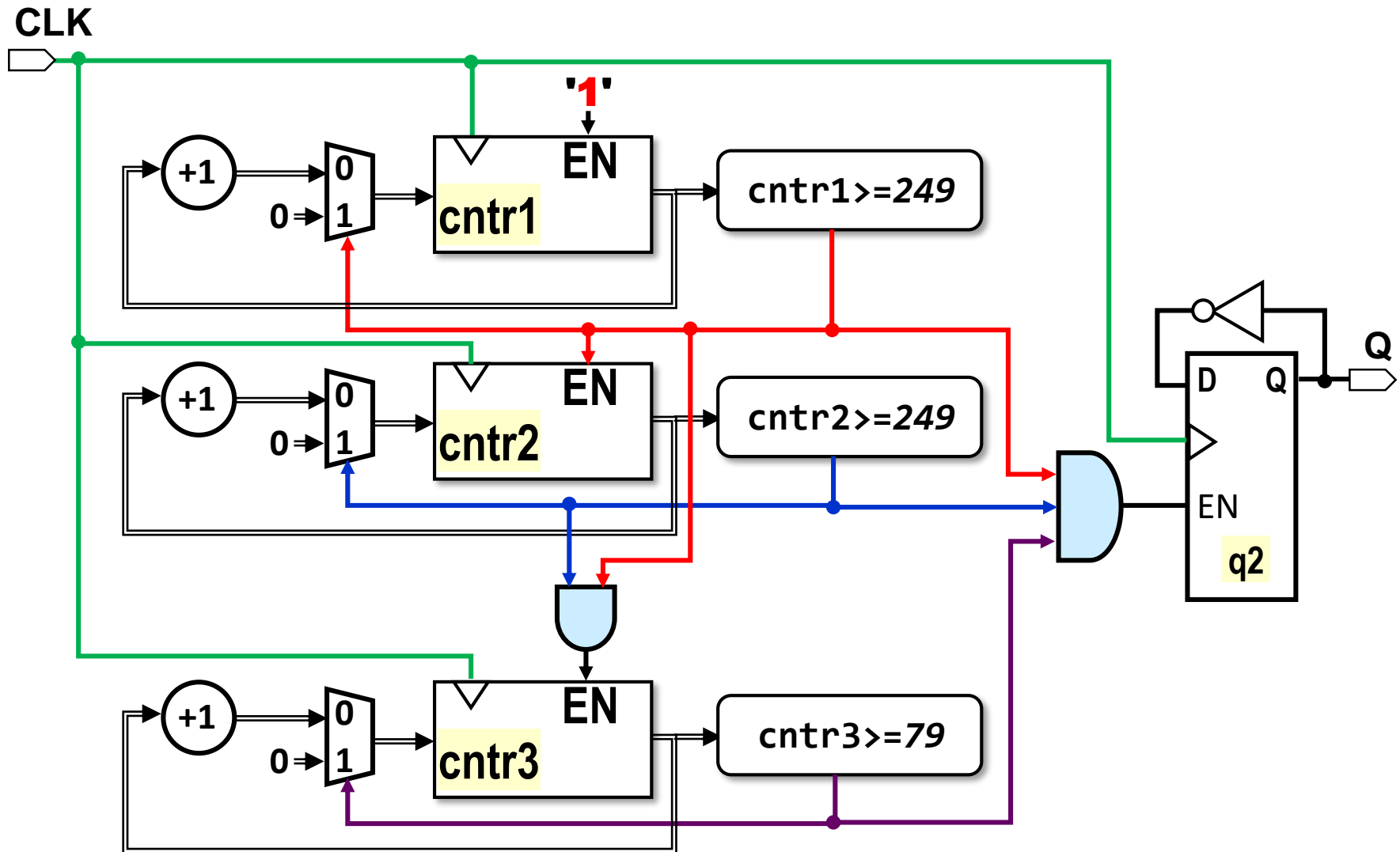

- The block structure uses the EN (enable) inputs of the DFF flip-flop circuits. All internal counters receive the clock signal permanently, they only determine whether to respond to it or not.
- The first counter cntr1 is enabled permanently in '1', so it always counts. When it reaches 249, its comparator switches the input multiplexer so that after the next clock edge it loads '0', starting from the beginning. The output of its comparator is also sent to the enable input of the next counter that adds +1. It counts the number of times cntr1 has been reset.
- The last counter, cntr3, is incremented only when both upper counters are zeroed. The output flip-flop circuit q2 flips when all three counters are zeroed at once, which occurs after $250 \times 250 \times 80 = 5$ million, so there will be a CLK divided by 10 million on Q.
- Note that all counters and comparators work in parallel and do not wait for their results. Their cascade has nearly the same complexity as one single divider. Much more important is the fact that the cascade handles almost 50 percent higher frequency on its CLK input.



High-frequency divider by 10M 2/4

```
library ieee; use ieee.std_logic_1164.all; use ieee.numeric_std.all;
entity DivBy10M is
    port ( CLK : in std_logic;
          Q : out std_logic);
end entity;
architecture rtlEdu of DivBy10M is
begin
    process(CLK)
        constant DivBy1: integer:=250; constant DivBy2: integer:=250;
        constant DivBy3: integer:=80;
        variable cntr1 : integer range 0 to DivBy1-1:=0;
        variable cntr2 : integer range 0 to DivBy2-1:=0;
        variable cntr3 : integer range 0 to DivBy3-1:=0;
        variable q2 : std_logic:='0';
        variable clear1, clear2, clear3 : boolean;
    begin --process
```



High-frequency divider by 10M 3/4

begin

if rising_edge(CLK) then

clear1:=cntr1>=DivBy1-1; clear2:=cntr2>=DivBy2-1; clear3:=cntr3>=DivBy3-1;

if TRUE then -- cntr1 is always enabled

if clear1 then cntr1:=0; else cntr1:=cntr1+1; end if;

end if;

if clear1 then --now, cntr2 is enabled

if clear2 then cntr2:=0; else cntr2:=cntr2+1; end if;

end if;

if clear1 and clear2 then -- now, cntr3 is enabled

if clear3 then cntr3:=0; else cntr3:=cntr3+1; end if;

end if;

if clear1 and clear2 and clear3 then -- div2 is enabled

q2:=not q2;

end if;

end if;

Q<=q2;

end process; end architecture;



High-frequency divider by 10M 4/4

architecture rtlShort of DivBy10M is
begin

process(CLK)

constant DivBy1_2: integer:=250;

constant DivBy3: integer:=80;

variable cntr1, cntr2 : integer range 0 to DivBy1_2-1:=0;

variable cntr3 : integer range 0 to DivBy3-1:=0;

variable q2 : std_logic:='0';

begin

if rising_edge(CLK) then

if cntr1<DivBy1_2-1 then cntr1:=cntr1+1;

else cntr1:=0;

if cntr2<DivBy1_2-1 then cntr2:=cntr2+1;

else cntr2:=0;

if cntr3<DivBy3-1 then cntr3:=cntr3+1;

else cntr3:=0; q2:=not q2;

end if;

end if;


end if;

end if;

Q<=q2;

end process; end architecture;

 Not giving priority to asynchronous input



Scenario 1 (priority violation)
2 (stop violation)

Violated asynchronous input priority


```
library ieee; use ieee.std_logic_1164.all;
entity Nonsense is
  port (clock, aclrn : in std_logic;
        D : in std_logic;
        q : out std_logic);
end;
architecture rtl of Nonsense is
begin process(clock, aclrn)
begin
  if rising_edge(clock) then
    q <= D;
  elsif aclrn = '0' then
    q <= '0';
  end if;
end if;
end process;
end rtl;
```

*Asynchronous clear (aclrn)
always has a higher priority,
so it must appear in the code before the clock
edge detection of the synchronous part -
otherwise it cannot be implemented!*

*Error (10818): Can't infer register for "q"
at Nonsense.vhd(14) because it does not
hold its value outside the clock edge
Error (10822): HDL error at Nonsense.vhd
(14): couldn't implement registers for
assignments on this clock edge*

Wrong Dependency on the Two Clocks

 - ❑ DET or DETFF - Dual Edge Triggered Flip-Flop
- ❑ Double Clock D type Flip-Flop



Faulty Dependence on 2 Clocks

```
library ieee; use ieee.std_logic_1164.all;
entity NotInOurFPGA is
  port (clock : in std_logic;
        D : in std_logic; q : out std_logic);
end;
architecture rtl of NotInOurFPGA is
begin
  process(clock)
  begin
    if rising_edge(clock) then
      q <= D;
    elsif falling_edge(clock) then
      q <= not D;
    end if;
  end process; end architecture;
```

*Our Cyclone does not include
flip-flop circuits sensitive to
multiple clock inputs.*

*- similar codes are not directly a
bug; we just don't have them
to implement.*

*Error: Netlist error at reg4.vhd(13):
can't infer register for q because it
changes value on both rising and
falling edges of the clock*

*Error: HDL error at
NotInOurFPGA.vhd(13): couldn't
implement registers for assignments
on this clock edge*

Violated value in the next function

Impossible operation

```
library ieee; use ieee.std_logic_1164.all;
entity DeltaWrong1 is
  port (clock : in std_logic;
        D, A : in std_logic; q : out std_logic);
end;
architecture rtl of DeltaWrong1 is
begin
  process(clock, A)
  begin
    q <= A;
    if rising_edge(clock) then
      q <= D;
    end if;
  end process; end architecture;
```

Error (10818): Can't infer register for "q" at reg_DeltaWrong1.vhd(11) because it does not hold its value outside the clock edge

Incorrect value change in the output function

```
library ieee; use ieee.std_logic_1164.all;
entity OmegaLatch is
  port (clock : in std_logic;
        D, A : in std_logic; q : out std_logic);
end;
architecture rtl of OmegaLatch is
begin
  process(clock, A)
  begin
    if rising_edge(clock) then
      q <= D;
    end if;
    if A='1' then q <= not D;
    end if;
  end process; end architecture;
```


*Warning (335093): TimeQuest
Timing Analyzer is analyzing 1
combinational loops as latches.*

Input A now belongs to the sensitivity list

*Here we have the combination circuit,
incomplete assignment creates Latch !*

Changing the value in the next value function - Technology Map
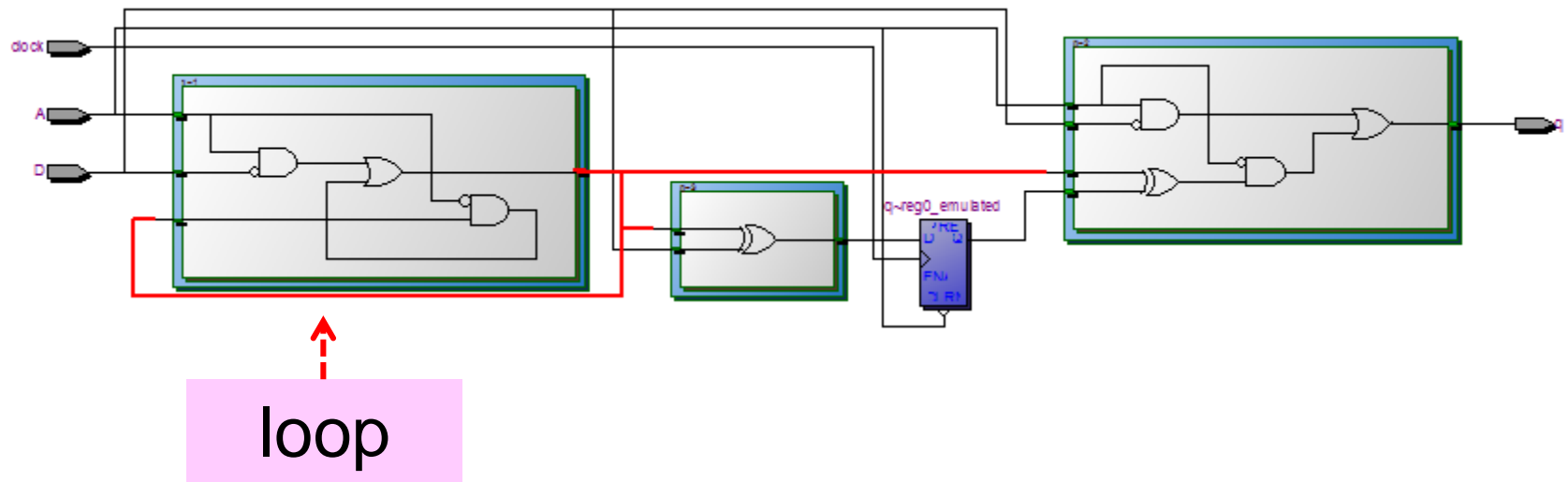
```
process(clock, A)  
begin if rising_edge(clock) then q <= D; end if;  
      if A='1' then q <= not D; end if;  
end process;
```



Incorrect value change

```
library ieee; use ieee.std_logic_1164.all;
entity OmegaLatch2 is
  port (clock : in std_logic;
        D, A : in std_logic; q : out std_logic);
end;
architecture rtl of OmegaLatch2 is
begin
  process(clock, A)
    variable x : std_logic;
  begin
    if rising_edge(clock) then x := D;
  end if;
    if A='1' then x := not D; end if;
    q<= x;
  end process; end architecture;
```

*Warning (335093): TimeQuest
Timing Analyzer is analyzing 1
combinational loops as latches.*

Entry A again belongs to the sensitivity list

*The variable won't help.
Latch again! We require
conditional storing x value!!!*

Incorrect value change in the output function

```
library ieee; use ieee.std_logic_1164.all;
entity OmegaLatch2 is
  port (clock : in std_logic;
        D, A : in std_logic; q : out std_logic);
end;
architecture rtl of OmegaLatch2 is
begin
  process(clock, A)
    variable x : std_logic;
  begin
    if rising_edge(clock) then x := D;
  end if;
    if A='1' then x := not D; else x := x; end if;
    q<= x;
  end process; end architecture;
```

*Warning (335093): TimeQuest
Timing Analyzer is analyzing 1
combinational loops as latches.*


Entry A again belongs now to the sensitivity list

*Latch again!
And why is that?*

Correct now - we no longer change x
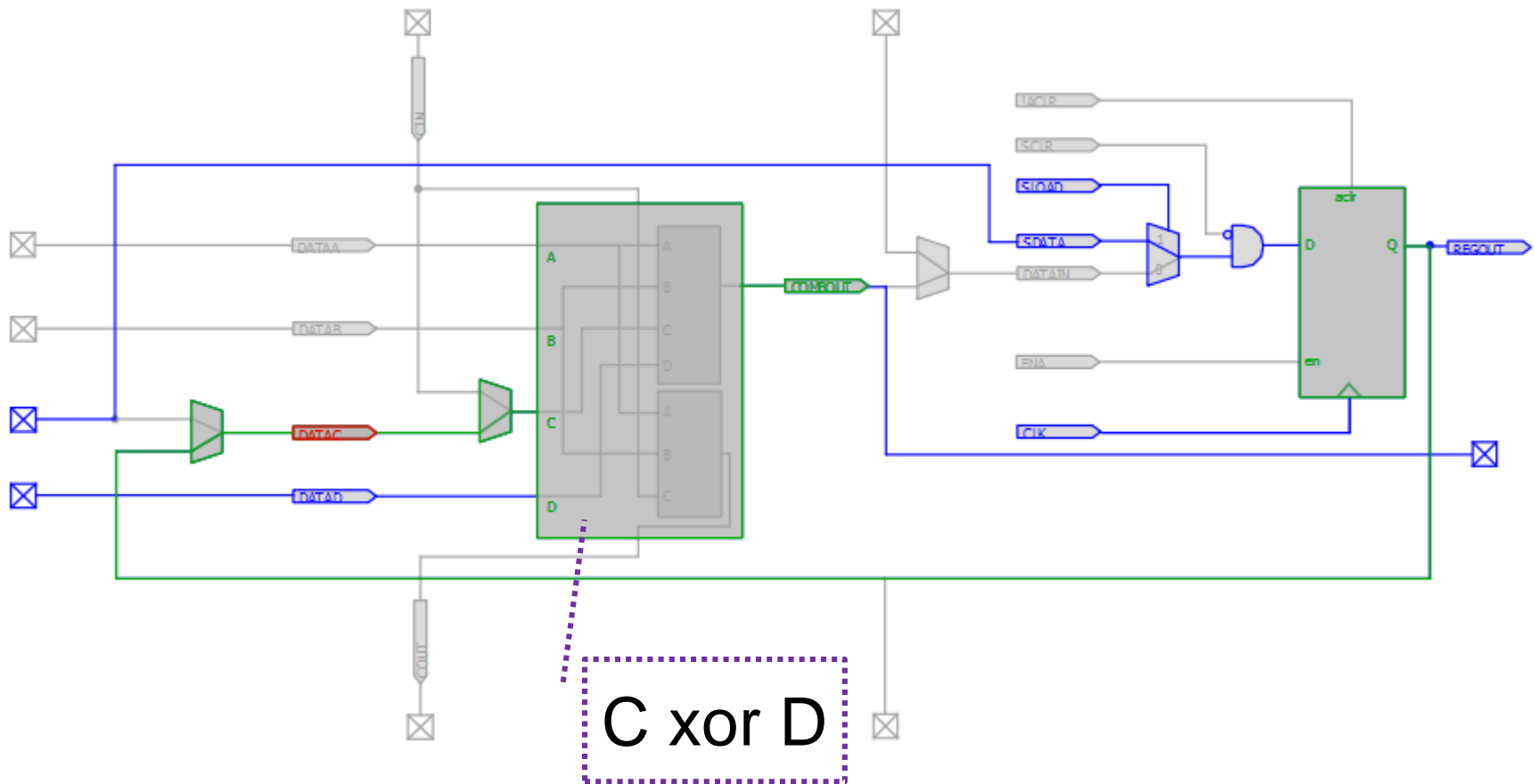
```
library ieee; use ieee.std_logic_1164.all;
entity OmegaNot is
  port (clock : in std_logic;
        D, A : in std_logic; q : out std_logic);
end;
architecture rtl of OmegaNot is
begin
  process(clock, A)
    variable x : std_logic;
  begin
    if rising_edge(clock) then x := D;
  end if;
    if A='1' then q<= x; else q<= not x; end if;
  end process;
end architecture;
```





Quartus has cleverly created an output function
the only logical element,
in which he used his fastest inputs C and D.

Suicide Structures




Jidai Geki, Harakiri (1962)

➤ **Non-constant asynchronous initialization**

Initialization to a Non-constant Value

```
port (clock, Init, D : in std_logic;  
      q: out std_logic); ...
```

```
begin process(clock, aclrn, Init)  
begin if aclrn = '0' then
```



```
    q <= Init;
```

```
    elsif rising_edge(clock) then  
        q <= D;  
    end if;
```

```
end process;
```

Never perform asynchronous initialization to non-constant values if you have only DFF circuits with one asynchronous input. Cyclone II and IV FPGAs have only flip-flop circuits with one asynchronous input, so it can only asynchronously initialize to one constant value.




2 asynchronous settings = constant initialization

```
port(clock, D, aclrn, apren : in std_logic;  
      q: out std_logic); ...
```

```
begin process(clock, aclrn, apren)
```

```
begin
```




```
  if apren = '0' then q <= '1';  
  elsif aclrn = '0' then q <= '0';
```

```
    elsif rising_edge(clock) then  
      q <= D;  
    end if;
```

```
end process;
```

 *Do not use two
independent
asynchronous
influences on a
synchronous variable.
DFF in our FPGA
has only one
asynchronous input.*






- Warning (13004): Presetable and clearable registers converted to equivalent circuits with **latches**. Registers power-up to an undefined state, and DEVCLRn places the registers in an undefined state.
 - Warning (13310): Register "q~reg0" is converted into an equivalent circuit using register "q~reg0_emulated" and **latch** "q~1"
- Warning (335093): TimeQuest Timing Analyzer is analyzing 1 combinational loops as **latches**.
- Warning (335093): TimeQuest Timing Analyzer is analyzing 1 combinational loops as **latches**.


The structure appears only in the Technology Map


RTL Map

 

Technology Map

 Quartus found here that our FPGA does not have a DFF with two asynchronous inputs



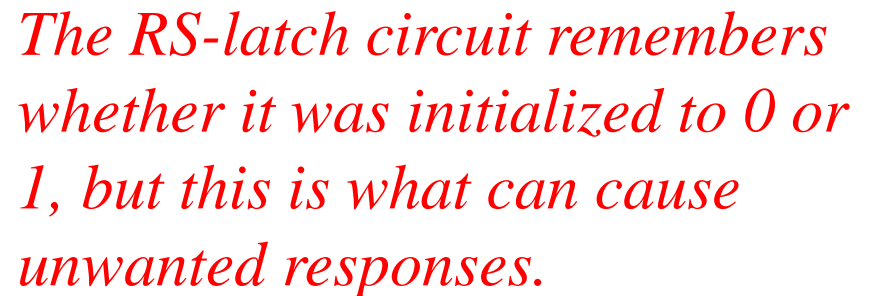

Quartus implements, but it must use unreliable wiring.


Incomplete Assignment in Combinational Parts

Quartus warning:
Combinational loops, latches

Incomplete assignment (1/2)

in the **combination** circuit
 
```
entity assignment1 is
port(a, b : in std_logic;
      q : out std_logic);
end;
architecture dataflow of assignment1 is
begin
    test : process(a, b)
    begin
        if b='1' then q<=a;
        end if;
    end process;
end architecture;
```



The VHDL specification specifies that a signal that has not been changed retains its previous value, which can only be solved by inserting a latch memory element.


*Thus, **the combination circuit** must always define the value of the signal, not be generated.*

However, incomplete assignments are commonly used in sequential circuits,

which already contain memory elements and do not need to be inserted

Incomplete Assignments(2/2)

 
- Warning (10631): VHDL Process Statement warning at assignment1.vhd(13): inferring **latch(es)** for signal or variable "q", which holds its previous value in one or more paths through the process
- Warning (335093): TimeQuest Timing Analyzer is analyzing 1 **combinational loops** as **latches**.
- Warning (335093): TimeQuest Timing Analyzer is analyzing 1 **combinational loops** as **latches**.



Always look for combinational "loop" and "latch" warnings in compiler messages.

```

 entity assignment1 is
port(a, b : in std_logic;
      q : out std_logic);
end;
architecture dataflow of assignment1 is
begin
    test : process(a, b)
    begin
        if b='1' then q<=a;
        else q<='0';
        end if;
    end process;
end architecture dataflow;
  
```



*The if-then-else statement **must** in the combinational circuit*

always specify a value on all possible branches

-> deterministic behavior.

Why points down, it works!!!

- I will always look for your suggestions
"loop" and "latch",
If your solution contains them,
then it cannot be accepted :-)*



[Image source wordpress.com]

- Latch copies faults from input to output for the entire active clock period.*
- In FPGAs it is not implemented by gates but by LUT tables, so it exhibits unexpected unwanted behavior similar to a hidden bomb - if it hasn't exploded yet, it doesn't mean it won't in the near future....*



Checker of VEEK-MT2 Project (Alpha version) - C:\SPS2024L\LSP_VeekMT2_TestWarningMessages_Q20\WeekMT2.qpf


File

To Do in Quartus Project | Log of Activities | Adjust VWF

Type	Code	Number of Descriptions
Disallowed	WARNING_DIVIDE	4
Disallowed	WARNING_LOOP	2
Disallowed	WARNING_LATCH	2
Disallowed	WARNING_SENSITIVITY	3

Occurrences in Items

The project creates a forbidden latch
Warning (10631): VHDL Process Statement warning at LCDlogic1.vhd(130): inferring latch(es) for signal or variable "RGB", which holds its previous value in one or more paths through the process File: C:/SPS/LSP_VeekMT2_TestWarningMessages_Q20/LCDlogic1.vhd Line: 130

 Your design created an forbidden LATCH.
If you need more information than you see here,
search for 'latch' in Quartus compiler messages.

ToDo

