 


# Logic Systems and Processors *cz:Logické systémy a procesory*

Lecturers: Martin Hlinovský+Richard Šusta


*Version V1.1*


 
# Warm-up Example




*The example focuses on the coding styles  
that are suitable for describing circuits.*




# Create Sext = Sign Extension Circuit

*It has the established abbreviation **sext***

# Unsigned / Signed Extensions


 

 
```
library ieee; use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
entity Sext is  
port( se : std_logic; -- sign extension is on  
      DataIn : in std_logic_vector(7 downto 0);  
      DataOut : out std_logic_vector(15 downto 0));  
end entity;
```


 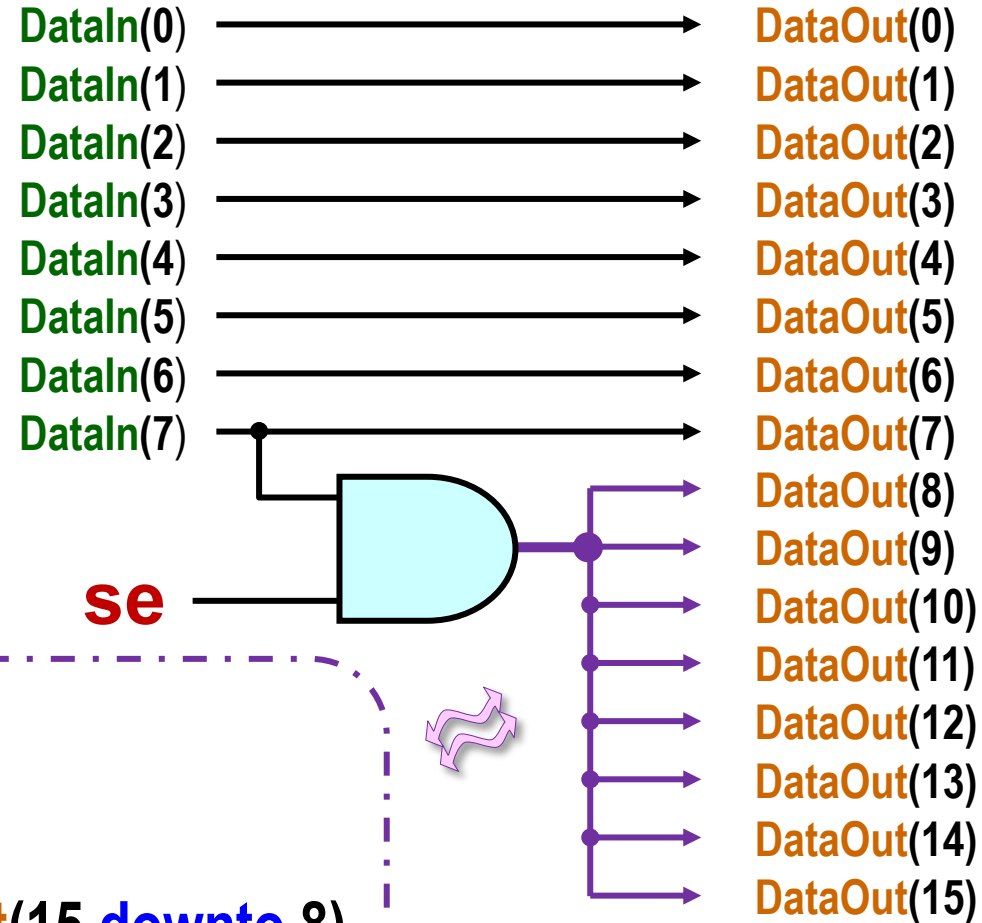
# VHDL Architecture - Step 2


The VHDL describes circuits, so we will start with the sext's schema:



It is certainly possible to assign 0 or 1 to DataOut from 8 to 15 according to the value of ( **DataIn(7)** **and** **se** ) condition, e.g., either


- using eight separate assignments, or  
one VHDL **for-generate loop** statement,

 However, the result would be the same as for the multiplexer below, which can be described with a shorter VHDL code.




```

 library ieee; use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity Sext is
port(  se : std_logic;
      DataIn : in std_logic_vector(7 downto 0);
      DataOut : out std_logic_vector(15 downto 0));
end entity;
  
```



```

 architecture dataflow of Sext is
begin
  
```



```

    DataOut(7 downto 0) <= DataIn;
  
```

```

    DataOut(15 downto 8) <= X"FF" when DataIn(7) and se else X"00";
  
```

```

-- all by 1 line: DataOut <= X"FF" & DataIn when DataIn(7) and se else X"00" & DataIn;
  
```

```

end architecture;
  
```

-- the code is for VHDL2008 (Quartus: Assignments->Settings->Compiler Settings->VHDL input)





# LCD - Liquid Crystal Display

*precisely TN LCD (Twist Nematic Liquid Crystal Display)*



*LSP course also describes the principles of modern digital systems,  
so we briefly look inside the topic of the LCD background task*

Image: [Terasic](#)

# Liquid Crystal Display principle

 


Image source:




Nowadays, 3 arrangements are used:

**TFT TN** – [*twisted LC* -> *vertical*] cheaper and with faster responses

**TFT VA** (Vertical Alignment) – [*vertical LC* -> *twisted*] the best colors and contrast, good viewing angle  
slow response

**TFT IPS** (*In-Plane-Switching electrodes*) – high price, better colors, wider viewing angle, usually slower.

 
Approximately 15% higher energy consumption compared to TFT TN





Source:




# Address Matrix



 


address  
6 = 0110

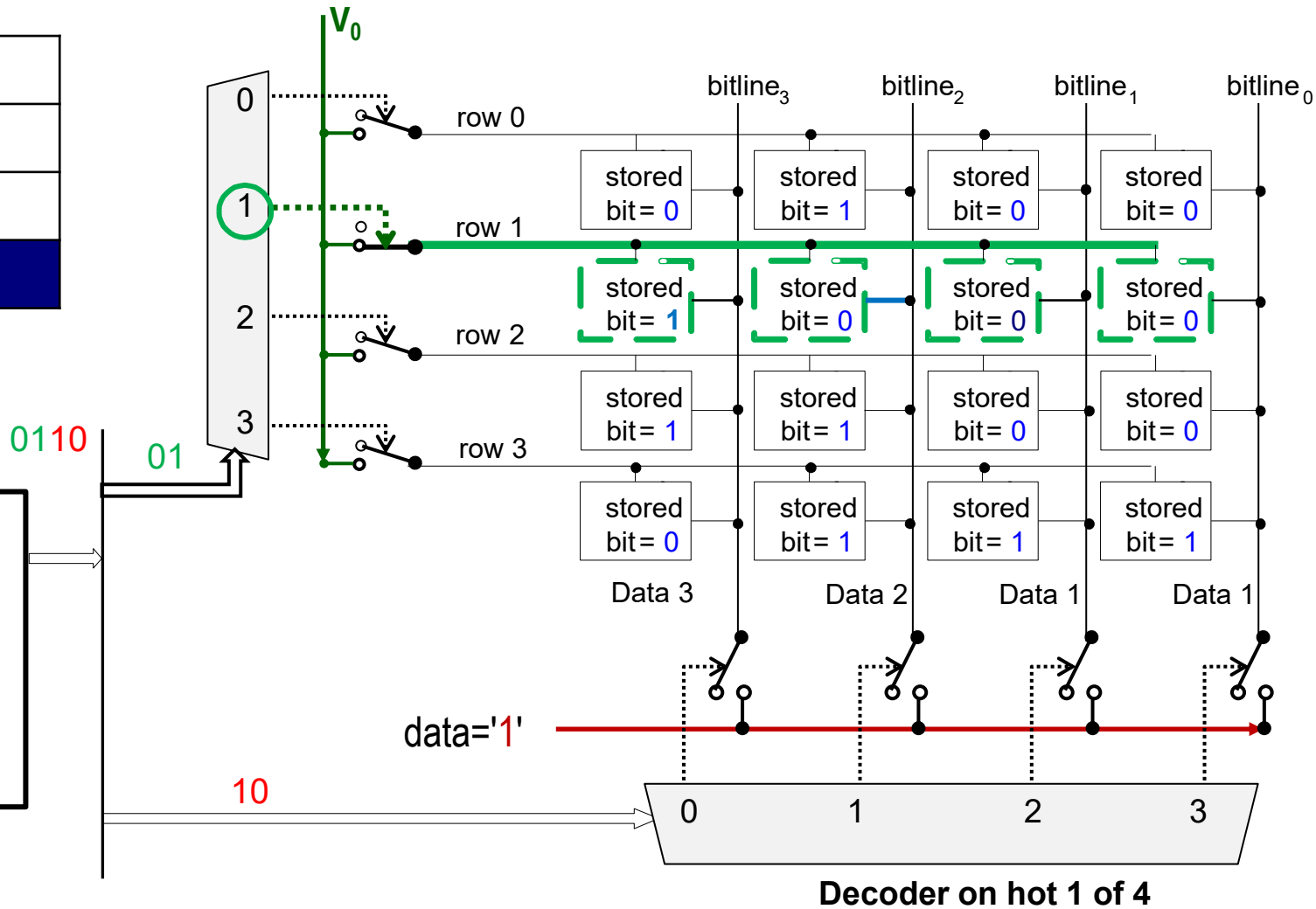 

 
 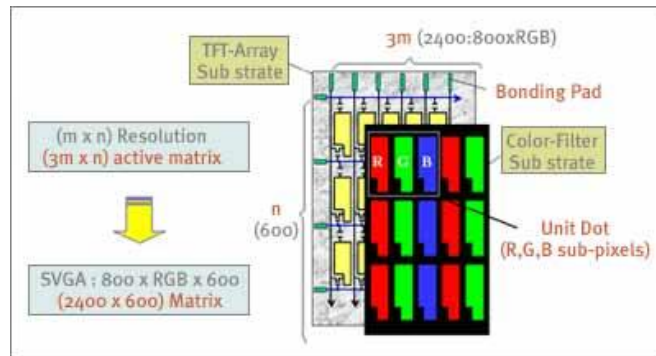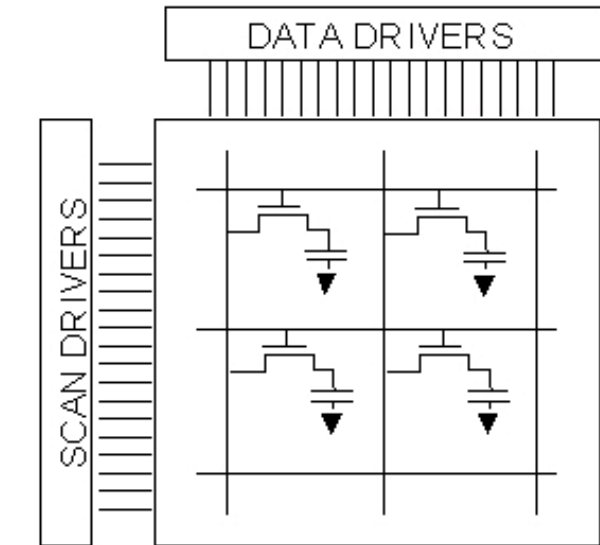
# TFT (Thin-Film Transistors) Active Matrix




Source of images:




# LCD capacitors store multiple levels!

TFT (switch) + LC cell (capacity)

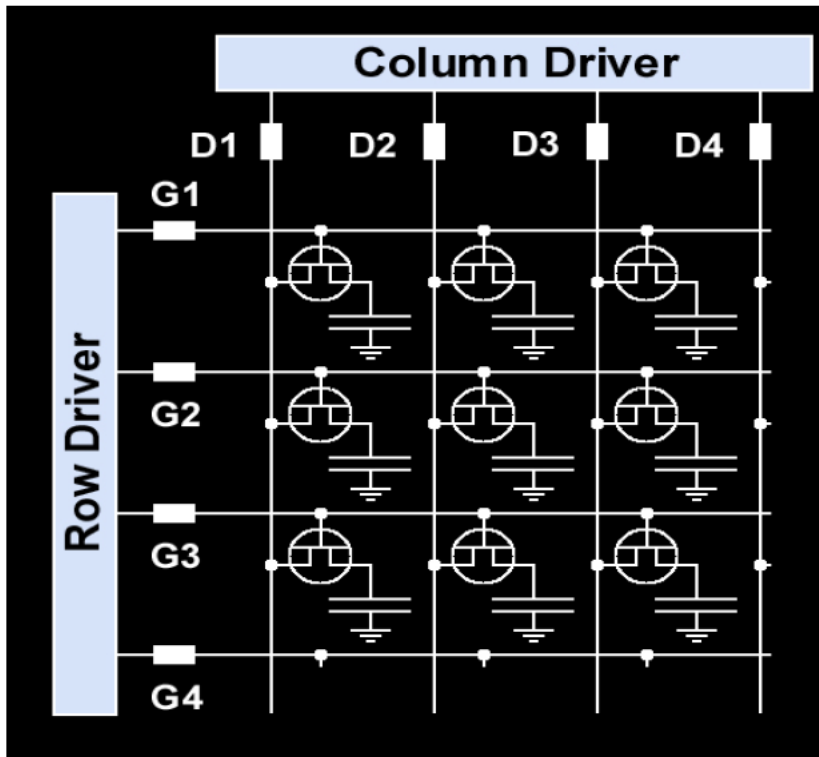

Hydrant (switch)+ Bucket (capacity)


 


Source: Dr. Zhibing Ge, College of Optics and Photonics




# LC LCD versus AMOLED - Refreshing

## LCD with Liquid Crystals

  

## AMOLED

 


The capacitors in LC LCDs have a typical value range from 100 fF (femtoFarads) to 2000 fF = from 0.1 pF to 2 pF, and need **regular refreshes** as DRAMs.

Nowadays, 2 OLED LCD types are used:

- **AMOLED** = Active Matrix OLED
- **OLED** with passive matrix – cheap LCD panels or very large LCDs, e.g, low-cost TVs. Slower responses than AMOLED.

# LCDs more often write in whole lines

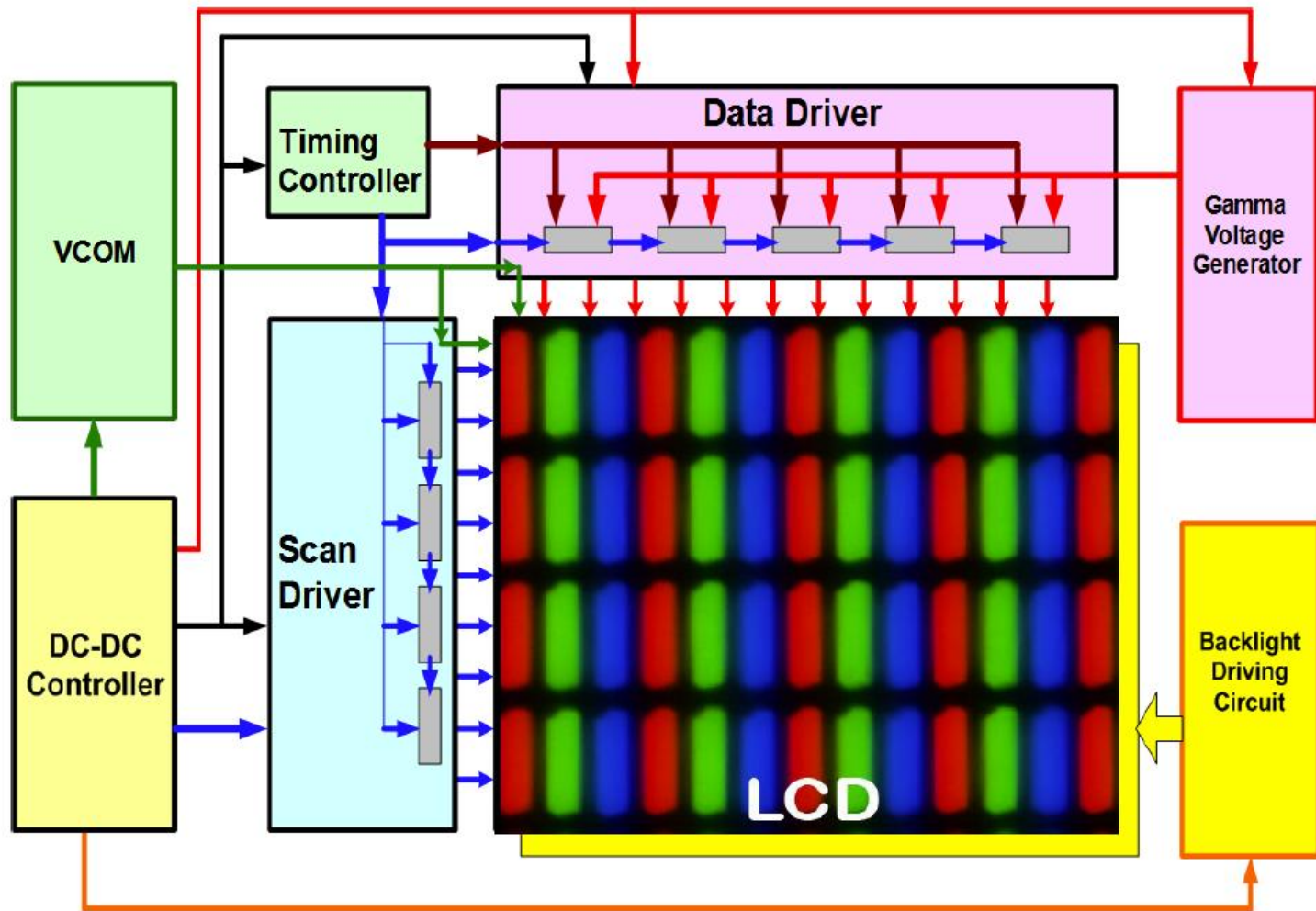

Source: Dr. Zhibing Ge, College of Optics and Photonics

# LCD Synchronization Generator

## LOGIC SYSTEMS AND PROCESSORS

### Public Site

Home

Install

**Guides**

Morse Code

VEEK-MT2 Board

### FELid Login Site

Overview of Results

Values to Tasks

Library

Logs of Changes

Descriptions of Quartus, GHDL and FPGA-LCD Utils installations are located on the [Install](#) page.


### TEXTBOOKS IN ENGLISH

0. [Binary Prerequisite V2.0](#) contains some basic concepts of binary numbers.

LSP lectures assume that students are familiar with them.

1.  [Logic Circuits on FPGAs](#) (160 pages) version 3.1 from Sept 17, 2025, added shift registers and

It explains the principles of basic logic circuits with a focus on their implementation in FPGAs.

2.  [LCD Backgrounds](#) contains templates how to create backgrounds and other images on LCD


Their VHDL codes assume the use of only FPGA logic elements and embedded memory blocks.

The selected example adapted to Veek-MT2 board [LCDbackgrounds VeekMT2.zip](#)

3. The document [Circuit Design with VHDL dataflow and structural V10.pdf](#) describes VHDL 1993.


+ Source codes: [CircuitDesignWithVHDL dataflow and structural codes.zip](#).

# Recommended Diagram of LCD Task

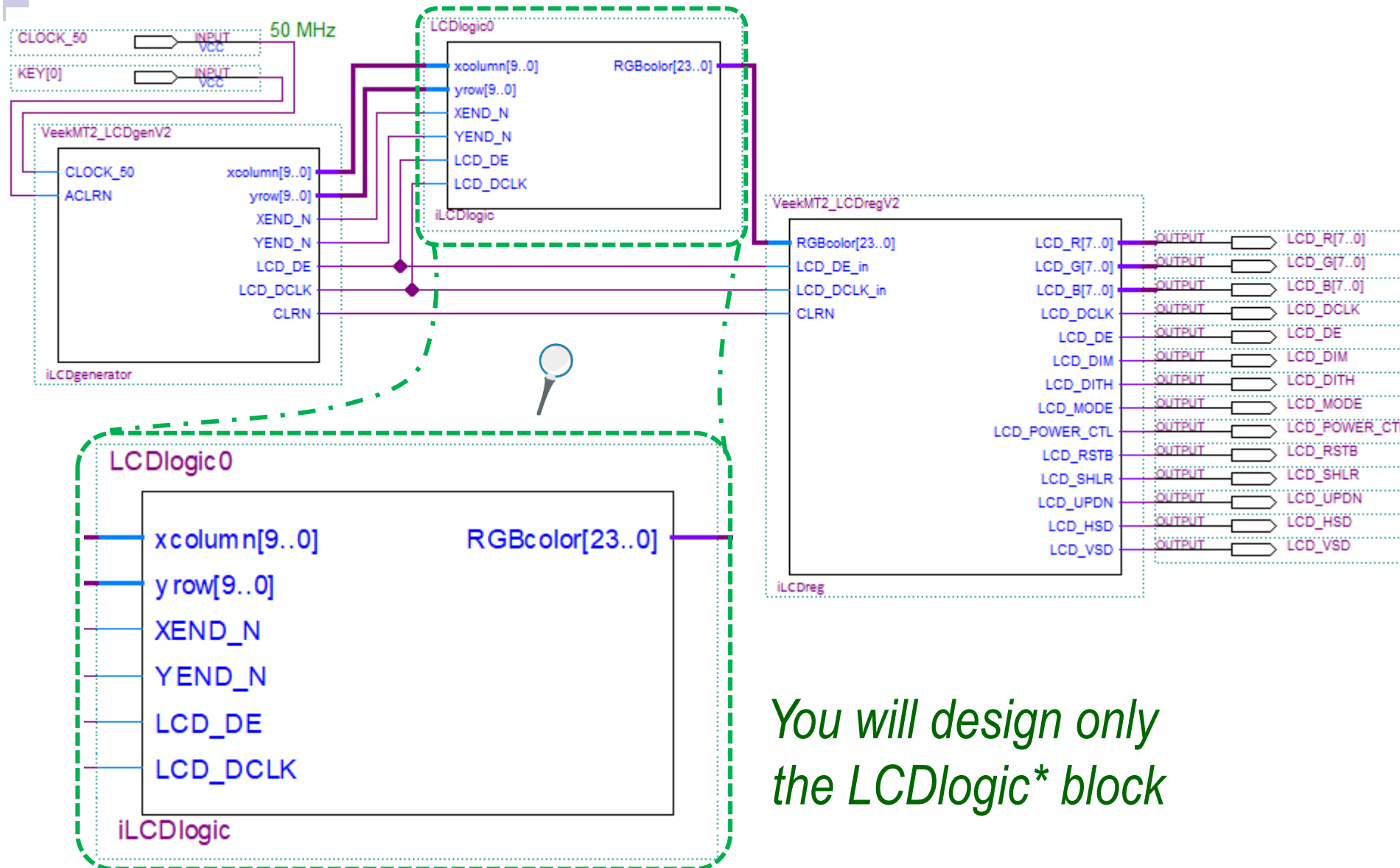

*You will design only the LCDlogic\* block*

# LCD Dimensions

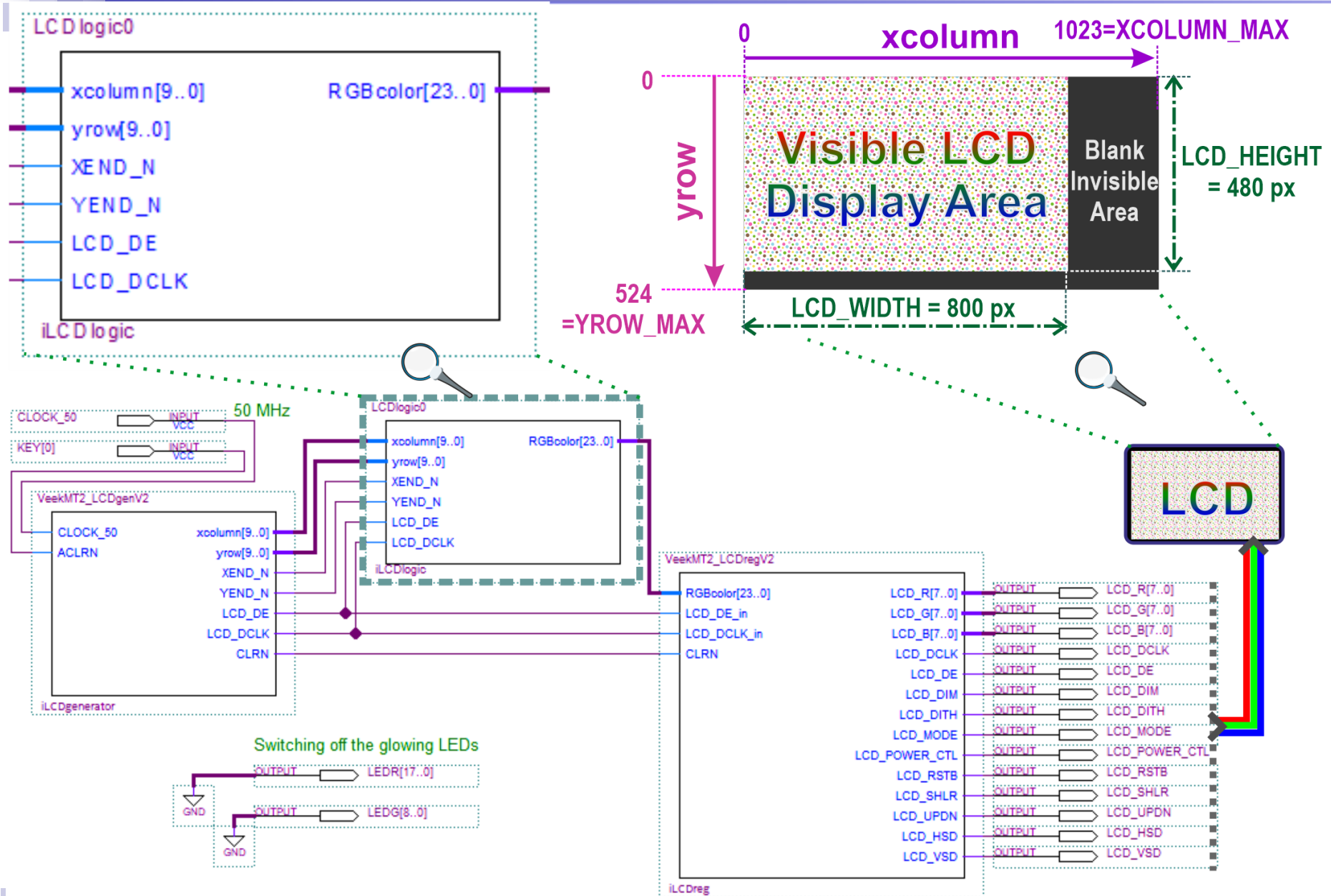

# WeekMT2\_LCDgenV2: Synchronization Generator

*// its code implements the following C code loop by counters*

unsigned short int **xcolumn**, **yrow**;

unsigned int **RGBcolor**;

bool **LCD\_DE**, **XEND\_N**, **YEND\_N**;

for (**yrow** = 0; **yrow** < 525; **yrow**++)

{ for (**xcolumn** = 0; **xcolumn** < 1024; **xcolumn**++)

{ **LCD\_DE** = **xcolumn** >= 800 || **yrow** >= 480 ? 0 : 1;

**XEND\_N** = **xcolumn** == 1023 ? 0 : 1;

**YEND\_N** = **yrow** == 524 ? 0 : 1;

**RGBcolor** = **LCDlogic**( **xcolumn**, **yrow** );



*// Your circuit of LCD background*

}

}




# Sample of Outputs

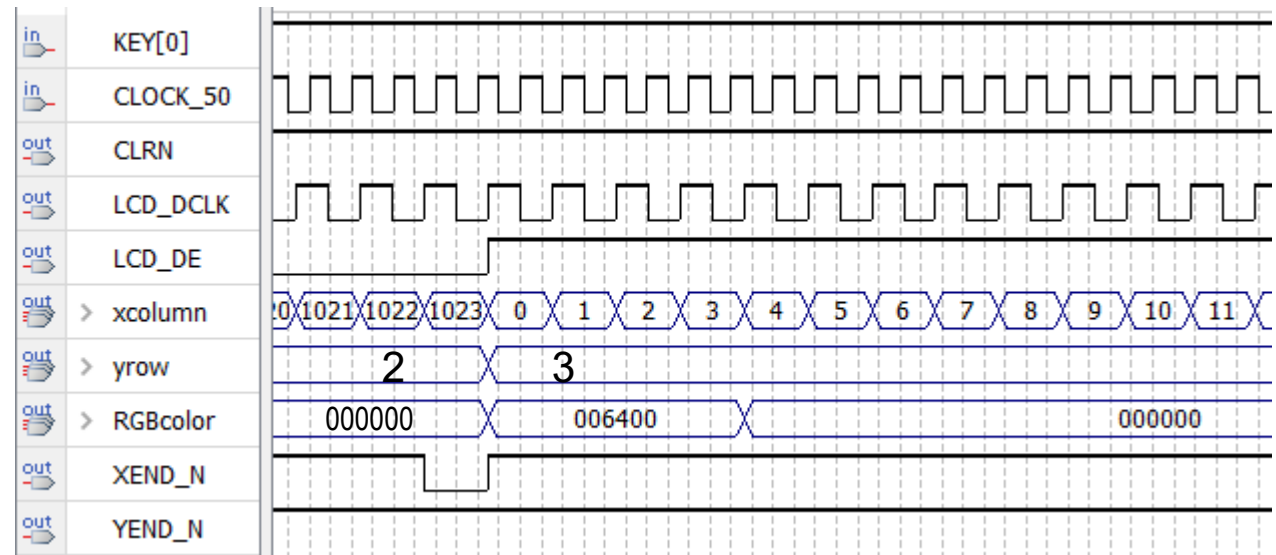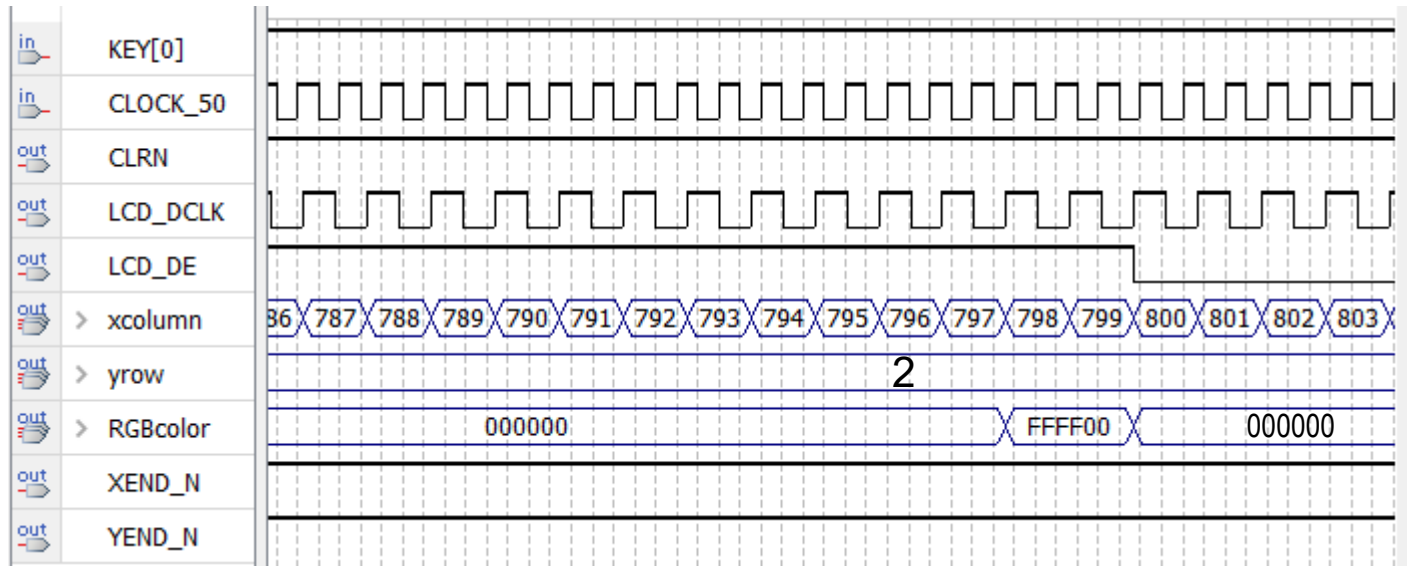


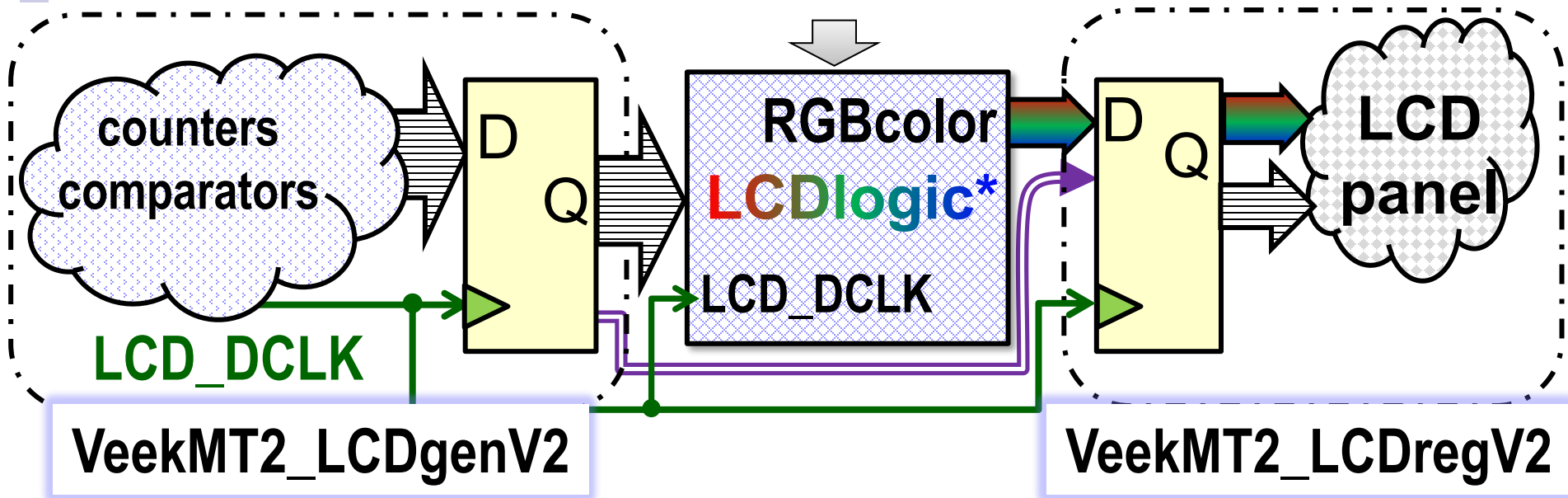
# RGBcolor is assigned by combinational logic!



## The **LCDlogic\*** module:

- It is inserted between a pair of registers.
- It **deliberately** does not include a register of its **RGBcolor** output.  
Such a register would disrupt the synchronization of the **RGBcolor** output with other LCD synchronization signals, introducing metastability, which we do not want.
- **RGBcolor must be created only with combinational logic!**
- Its combinational logic can certainly depend also on signals created by additional processes sensitive to a clock, but the **RGBcolor** process itself should not use clocks.




# LCD Pipeline

---

*data stream processing*

# LCD Pipeline and its Stages

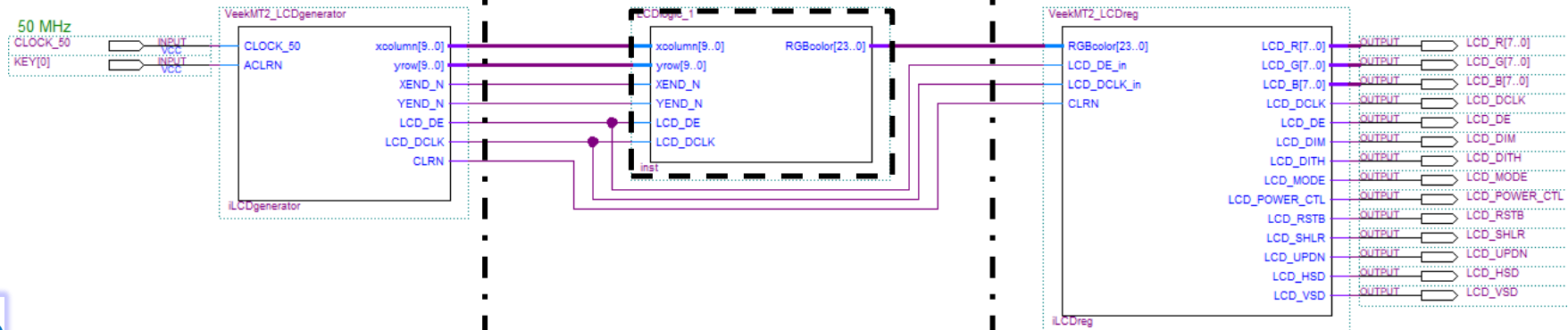

**Time**

**1. stage - GENERATE**

**2. stage -EXECUTE**


**3. stage - Write LCD**

	LCD_generator	LCDlogic	LCDreg
<b>t0</b>	—	—	—
<b>t1</b>	generates x0,y0	—	—
<b>t2</b>	generates x1,y0	calculates x0,y0 color	—
<b>t3</b>	generates x2,y0	calculates x1,y0 color	writes x0,y0 color
<b>t4</b>	generates x3,y0	calculates x2,y0 color	writes x1,y0 color




# *Priority task*

## *- visibility in a picture*

 

# Image by Cascade of Multiplexers

*conditions*

 


```
library ieee, work; use ieee.std_logic_1164.all;

use ieee.numeric_std.all; -- num

use work.LCDpackV2.all; -- V2.1 our definitions


entity LCDlecture is
```

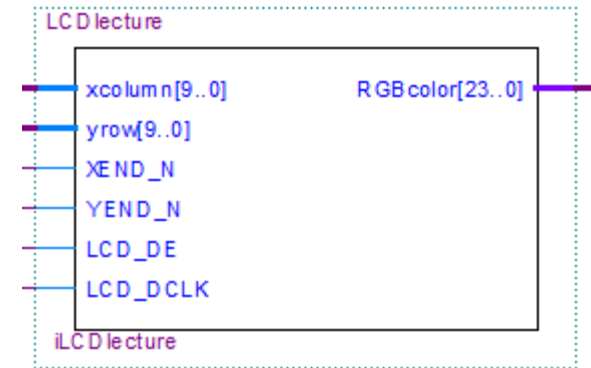

```
port( xcolumn, yrow : in xy_t := XY_ZERO; -- x,y-coordinates of pixel
      XEND_N, YEND_N : in std_logic := '0'; -- the last xcolumn/yrow
      LCD_DE        : in std_logic := '0'; -- DataEnable LCD
      LCD_DCLK       : in std_logic := '0'; -- LCD data clock, 33 MHz exactly
      RGBcolor       : out RGB_t := BLACK); -- colors assigned to pixels

end entity;
```



 

architecture beh1 of Lecture is

signal x : integer range 0 to 1023:=0; -- XCOLUMN\_MAX-1

signal y : integer range 0 to 524:=0; -- YROW\_MAX-1

begin -- architecture

x <= to\_integer(xcolumn); y <= to\_integer(yrow); -- unsigned -> integers

----- our image -----

--LCD\_WIDTH/2 LCD\_HEIGHT/2


RGBcolor <= GREEN when x<400 and y<240 else NAVY;

-- X"008000" X"000080"


end architecture;



RGBcolor

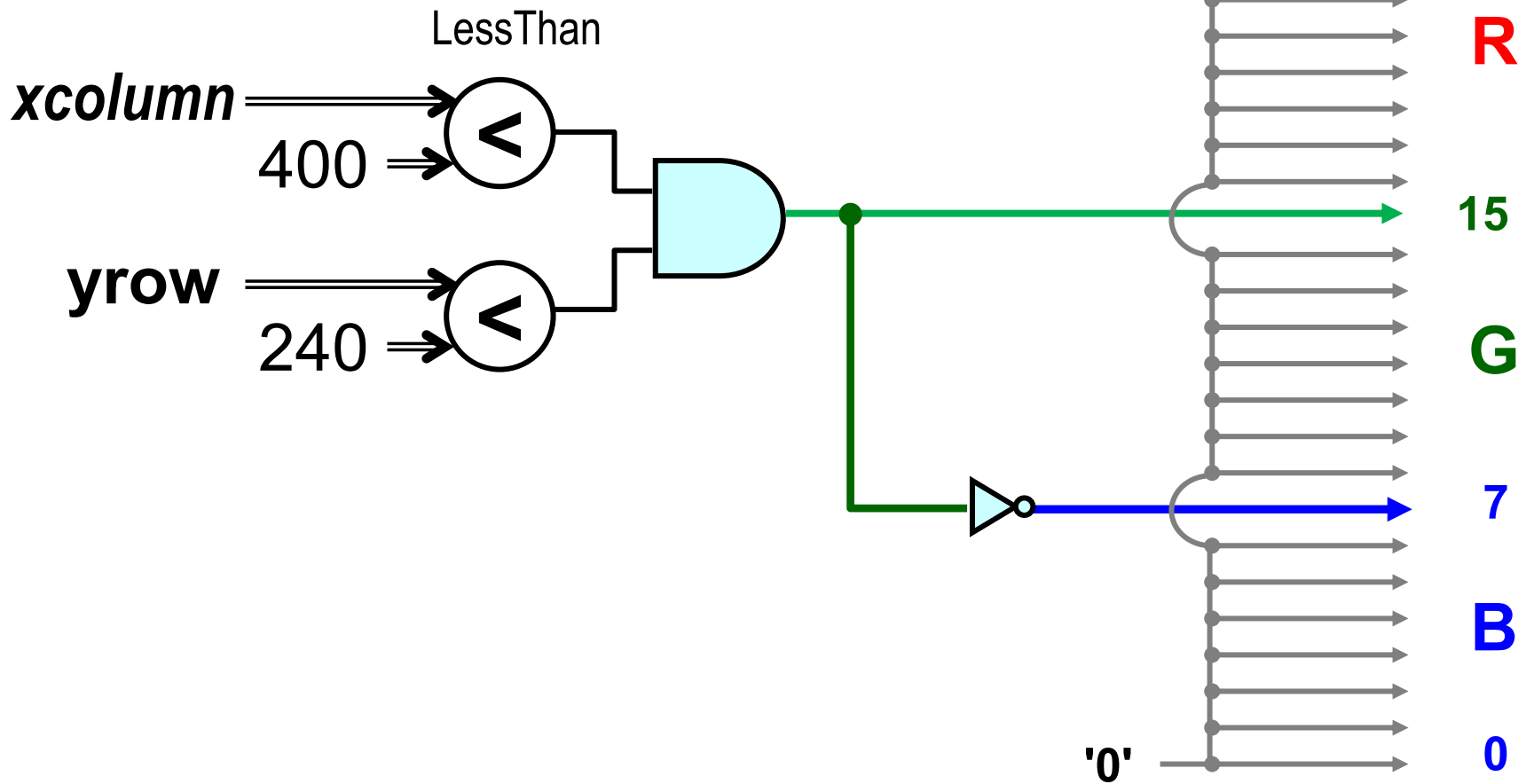



 

architecture beh1 of Lecture is

signal x : integer range 0 to 1023:=0; -- XCOLUMN\_MAX-1

signal y : integer range 0 to 524:=0; -- YROW\_MAX-1

begin -- architecture

x <= to\_integer(xcolumn); y <= to\_integer(yrow); -- unsigned -> integers

----- our image -----

-- X"800000"

RGBcolor <= MAROON when  $(x-400)^2 + (y-240)^2 < 128^2$  else

GREEN when  $x < 400$  and  $y < 240$  else NAVY;


-- X"008000"

X"000080"

-----

end architecture;



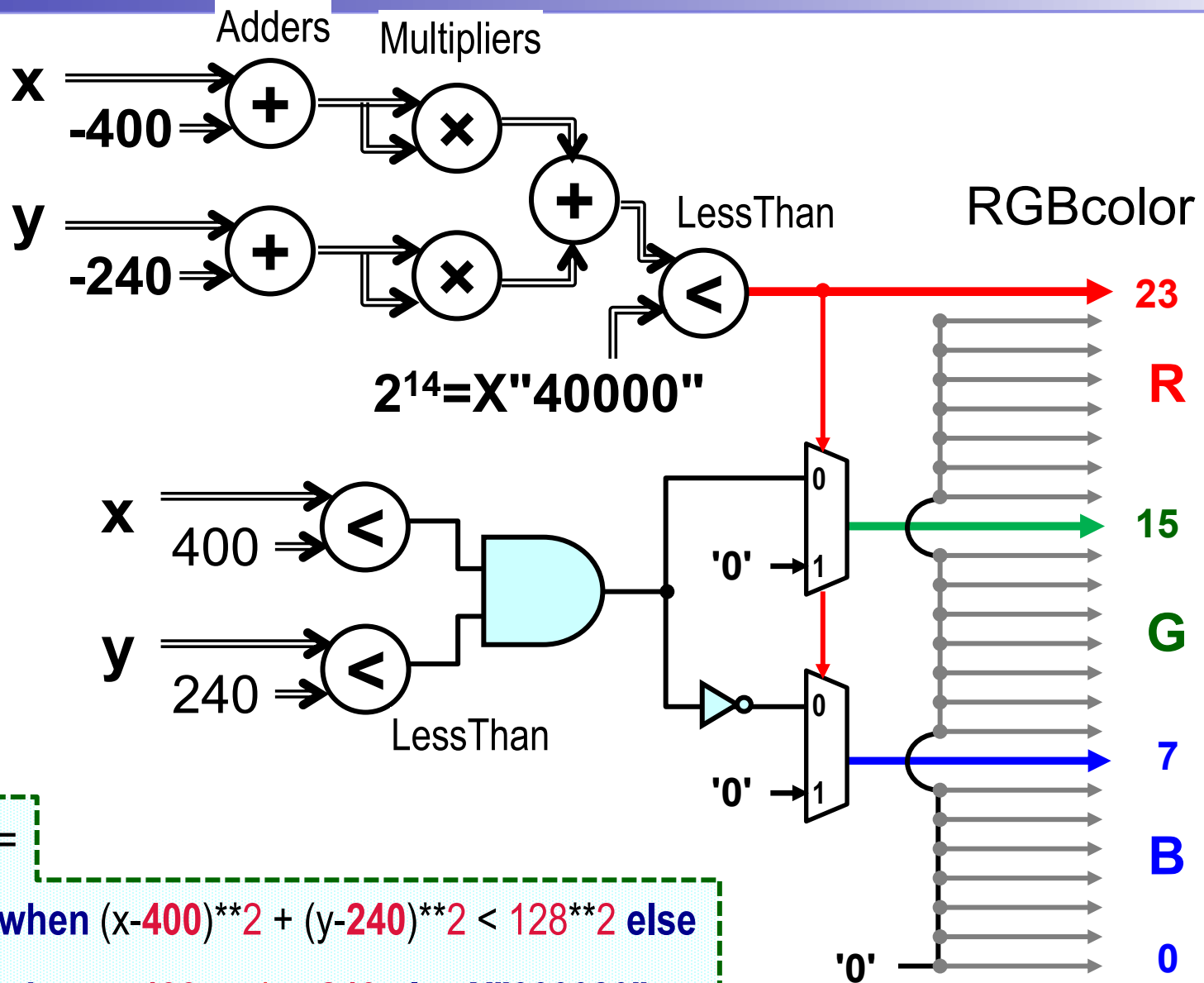

RGBcolor <=

$X"800000"$  when  $(x-400)**2 + (y-240)**2 < 128**2$  else


$X"008000"$  when  $x < 400$  and  $y < 240$  else  $X"000080"$ ;

RGBcolor <=

MAROON **when**  $(x-400)^2 + (y-240)^2 < 128^2$  **else**

GREEN **when**  $x < 400$  **and**  $y < 240$  **else**

NAVY;

 


RGBcolor <=

GREEN **when**  $x < 400$  **and**  $y < 240$  **else**

MAROON **when**  $(x-400)^2 + (y-240)^2 < 128^2$  **else**


NAVY;

 

RGBcolor <=

GREEN **when**  $x < 400$  **and**  $y < 240$  **and**  
 $(x-400)^2 + (y-240)^2 < 128^2$  **else**

NAVY;

 


RGBcolor <=

GREEN **when**  $x < 400$  **and**  $y < 240$  **and**  
 $(x-400)^2 + (y-240)^2 \geq 128^2$  **else**

NAVY;



# What about this picture?

 

# We cannot nest "when else"

architecture beh2 of Lecture is

signal x : integer range 0 to 1023:=0; -- XCOLUMN\_MAX-1

signal y : integer range 0 to 524:=0; -- YROW\_MAX-1

signal isR, isC : boolean:=FALSE;

begin x <= to\_integer(xcolumn); y <= to\_integer(yrow);

----- our image -----

isR <= x<400 and y<240;

isC <= (x-400)\*\*2 + (y-240)\*\*2 < 128\*\*2;


RGBcolor <= GREEN when isR and not isC else

YELLOW when isR and isC else

MAROON when isC else

NAVY;

end architecture;

 



# Dataflow Limits

- The conditions are growing for nested rules
  - the concurrent **select with** or **when else** statements **cannot contain inserted statements, only expressions.** So, we must first assign values to auxiliary signals.
- In the sequential domain, it is possible to nest statements and also overwrite previously assigned values.
- The compiler transforms sequential domain codes into concurrent statements by introducing auxiliary signals.



# VHDL Process

*and its applications*





# Three types of "concurrent" commands we are familiar with them from the concurrent domain.

**<=**

**with-select-when**

**when-else**

*Visit For*

Concurrent assignments

Selective assignments

Conditional assignments

*implemented using*

logic circuit


multiplexers

multiplexer cascades 2:1
 
## Sequential VHDL domain

is surrounded by keywords:

- **function ... end function;**
- **procedure ... end procedure;**
- **process ... end process;**
- It also includes the passive process that starts with the optional **begin** keyword inside an **entity** declaration to its **end**.



**Architecture**


**Concurrent Statements**

**Structural**

**Process**

**Sequential Statements**

port map  
generic map

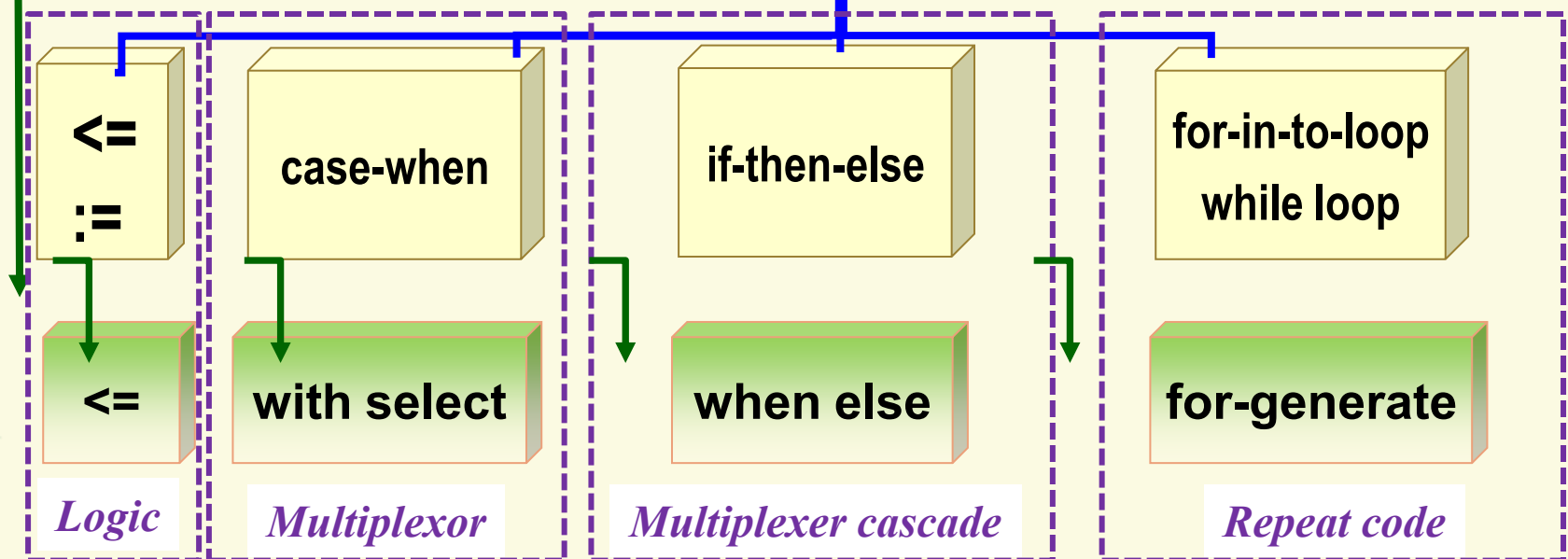

# Process Format

---

**[label:] process (sensitivity list)**

***declarations***

**begin**

***sequential statements***


**end process [label];**

-- *Label* is an optional parameter.

*However, we can see it in the simulation,  
in which it serves as a landmark.*

# Main Declarations in Sequential Domain

---

- **type**, **subtype**, **constant** and **variable** 
  - **function**, **procedure** - sequential codes of circuit parts for local use. They are not called in the circuit, but inserted by inline expansion technique.
  - **use** keyword allows adding additional libraries locally available only here, if they are needed.
- ❖ No **signal** or **component** declarations are allowed here.



- A *process* is a **VHDL construct that contains a set of actions to be executed sequentially**. These actions are known as *sequential statements*. **The process itself is a concurrent statement**. It can be interpreted as a circuit part enclosed inside a black box whose behavior is described by the sequential statements. We may or may not be able to construct physical hardware that exhibits the desired behavior.
- The **sensitivity-list is a list of signals to which the process responds (i.e., is “sensitive to”)**. The **declaration part consists of various declarations that are local to the process**.
- The list of sensitivities in the process is not a formal parameter, but hints s what inputs will cause the requirement for new evaluations.
- Whereas the appearance of a VHDL process is like a function or procedure of a traditional programming language, the behavior of the process is very different. A VHDL process is not invoked (or called) by another routine. It acts like a circuit part, which is either active (known as *activated*) or inactive (*known as suspended*).
- *In simulations, a VHDL process is activated when* a signal in the sensitivity list changes its value, like a circuit responding to an input signal. Once a process is activated, its statements will be executed sequentially until the process is complete. The process is then suspended until the next signal change.

[VHDL 1993 Reference, IEEE]

- A variable describes the abstract behavior of the system.
- We can declare variables in a process, function or procedure. We are not allowed to declare signals there, they belong only to the architecture.
- Variables are always local, i.e., they cannot be referenced from elsewhere than from the part that declared them.
- *Note: Shared variables were introduced in VHDL 93 for simulation purposes. Although they can be declared outside the process, they are difficult to implement in hardware. As a rule, they are circumvented by complex automatic conversions, which sometimes have unpredictable results.*
- **Shared variables are strictly prohibited in the circuit synthesis portions of LSP projects.** The rule is also applied by professional development companies.

# Assignments: Variables vs. Signals

- In the sequential domain, we cannot define signals, only variables, but by their declarations are similar to signals:

**variable** variable-name, variable-name , . . . . : **data-type**;

- New values are assigned to variables by **blocking** assignments:

variable-name := value-expression;

- Signals represent connections by wires and need **non-blocking** concurrent assignments:

signal-name <= signal-expression;

*The reasons for this will be the topic of some the following lecture.*

- In **VHDL 2008**, we can also use "**concurrent statements**" **when-else** and **with-select** in the sequential domain.

**But the Quartus Lite versions do not allow them here!**



**architecture** rtl2008 **of** Lecture **is**

**begin** -- *architecture*

LSPimage : **process**( xcolumn, yrow)

-- *In any process, we prefer variables. They must be initialized in the code!!!*

-- *The values after definitions are mainly for simulations.*

**variable** RGB : **RGB\_t** := BLACK; -- *the color of pixel*

**variable** x : **integer range 0 to 1023** := 0; -- *XCOLUMN\_MAX-1*

**variable** y : **integer range 0 to 524** := 0; -- *YROW\_MAX-1*

→ **begin** -- *process*

x := **to\_integer**(xcolumn); y := **to\_integer**(yrow); -- *unsigned to integers*

-- *our image* -----

RGB := MAROON **when** (x-400)\*\*2 + (y-240)\*\*2 < 128\*\*2 **else**

GREEN **when** x < 400 **and** y < 240 **else** -- *LCD\_WIDTH/2, LCD\_HEIGHT/2*

NAVY;

RGBcolor <= RGB; -- *assigning the output signal at the end*

→ **end process**;  
**end architecture**;

However, Quartus Lite does not allow  
**when else** in sequential parts

**architecture** rtl **of** Lecture **is**

**begin** *-- architecture*

LSPimage : **process**( xcolumn, yrow)

**variable** RGB : **RGB\_t** := BLACK; *-- the color of pixel*

**variable** x : **integer range 0 to 1023** := 0; *-- XCOLUMN\_MAX-1*

**variable** y : **integer range 0 to 524** := 0; *-- YROW\_MAX-1*

**begin** x := **to\_integer**(xcolumn); y := **to\_integer**(yrow); -

*----- our image -----*

**if**  $(x-400)^2 + (y-240)^2 < 128^2$  **then** RGB := MAROON;

**elsif** x < 400 **and** y < 240 **then** RGB := GREEN;



**else** RGB := NAVY;

**end if**;

RGBcolor <= RGB;

**end process; end architecture**;

# The result is the same

 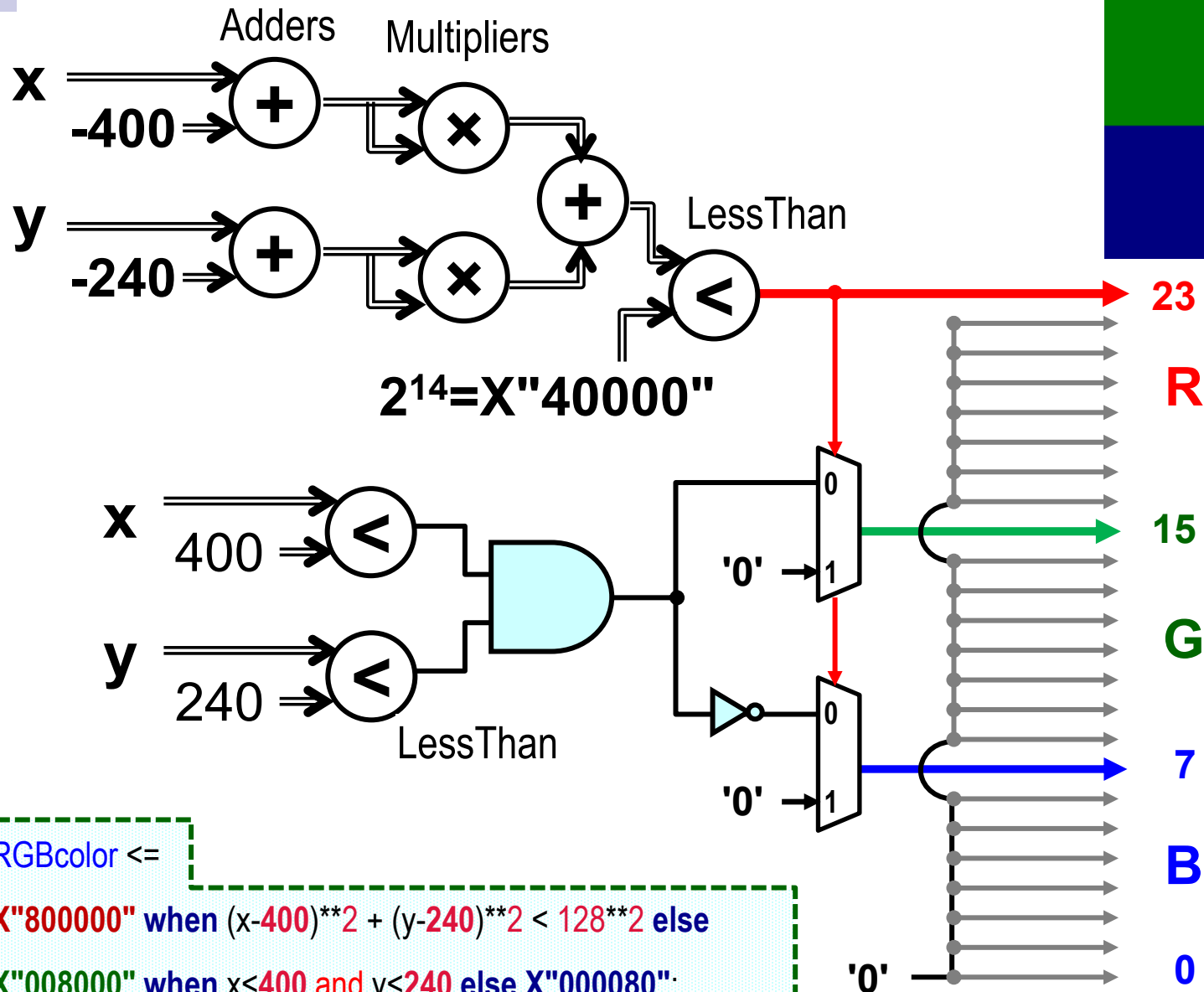

RGBcolor <=

$X''800000''$  when  $(x-400)^2 + (y-240)^2 < 128^2$  else

$X''008000''$  when  $x < 400$  and  $y < 240$  else  $X''000080''$ ;

# Two possible if-styles

more *if*-s

----- *our image* -----

RGB := NAVY;

**if**  $x < 400$  **and**  $y < 240$  **then** RGB := GREEN; **end if**;

**if**  $(x-400)^2 + (y-240)^2 < 128^2$  **then** RGB := MAROON; **end if**;

one long *if-elsif* command

----- *our image* -----

**if**  $(x-400)^2 + (y-240)^2 < 128^2$  **then** RGB := MAROON;

**elsif**  $x < 400$  **and**  $y < 240$  **then** RGB := GREEN;

**else** RGB := NAVY;

**end if**;

- ❑ Both methods lead to optimal circuits, and it depends only on the designers which code style they prefer.
- ❑ In the first step of the compilation, multiple **if-then** statements start with the **highest** priority condition which leads to a meta-scheme consisting of cascading two-input multiplexers.
- ❑ The multiple **if-then** statements describe the same cascade. They only begin from the **lowest**-priority condition.

# If statements can be nested

```
LSPimage : process( xcolumn, yrow, LCD_DE )  
  variable RGB :RGB_t :=BLACK; -- the color of pixel  
  variable x : integer range 0 to 1023:=0; -- XCOLUMN_MAX-1  
  variable y : integer range 0 to 524:=0; -- YROW_MAX-1  
  variable isR: boolean:=false; -- tis Rectangle  
  begin  x := to_integer(xcolumn); y := to_integer(yrow);  
    ----- our image -----  
    RGB := NAVY;  
    isR:=x<400 and y<240;  
    if isR then RGB := GREEN; end if;  
    if (x-400)**2 + (y-240)**2 < 128**2 then  
      if isR then RGB:=YELLOW; else RGB := MAROON; end if;  
    end if;  
    -----  
    RGBcolor <= RGB; -- assigning the output signal at the end  
  end process;
```

# Duplicate conditions? - Quartus will merge them

----- *our image* -----

```
RGB := NAVY;
```

```
if x<400 and y<240 then RGB := GREEN; end if;
```

```
if (x-400)**2 + (y-240)**2 < 128**2 then
```

```
if x<400 and y<240 then RGB:=YELLOW;
```

```
else RGB := MAROON; end if;
```

```
end if;
```

*But better coding styles define variables for shared conditions to emphasize their repetition...*

```
variable isR: boolean:=false;
```

```
--
```

```
isR:= x<400 and y<240; -- We must assign isR in our process code
```

```
if isR then RGB := GREEN; end if;
```

```
if isR then RGB:=YELLOW; else RGB := MAROON; end if;
```

# Syntax of Functions

---

[pure | impure ]

**function** **function\_name** (parameter\_list)

**return** type\_name **is**

[**sequential\_declarations**] *-- identical to processes*

**begin**

sequential statements...

**end** [**function**] [**function\_name**];

[ ] *indicates the possibility of omitting the element,*

| *denotes a selection of one option*

**pure**, *the default option, specifies that the function has no side effects.*



```
function assignIf(cond:boolean;  
                  colorTrue, colorFalse:RGB_t)  
return RGB_t is  
begin  
    if cond then return colorTrue;  
            else return colorFalse;  
    end if;  
end function;
```

```
RGB := assignIf(x<400 and y<240,  
                YELLOW, MAROON);
```

LCDpackV2 version V2.1 and higher includes assignIf also overloaded for integer results

```
LSPimage : process( xcolumn, yrow)
variable RGB :RGB_t :=BLACK; -- the color of pixel
variable x : integer range 0 to 1023:=0; -- XCOLUMN_MAX-1
variable y : integer range 0 to 524:=0; -- YROW_MAX-1
variable isR: boolean:=false;
begin  x := to_integer(xcolumn); y := to_integer(yrow);
----- our image -----
RGB := NAVY; isR:=x<400 and y<240;
if isR then RGB := GREEN; end if;
if (x-400)**2 + (y-240)**2 < 128**2 then
    RGB:=assignlf(isR,YELLOW, MAROON);
end if;
-----
RGBcolor <= RGB; -- assigning the output signal at the end
end process;
```



# *PROCESS*

and its "sensitivity list"


- **wait on** *signal list*;
  - wait until the signal changes;  
e.g.: **wait on** a;
- **wait until** *condition*;
  - wait until the condition is met;  
e.g.: **wait until** c='1';
- **wait for** *duration*;
  - wait for a specified duration;  
e.g.: **wait for** 10 ns;
- **wait**;
  - wait indefinitely → end of the process in which the command was used.

# "Sensitivity list" $\equiv$ "wait on!"

```
process(a,b)  
begin
```

```
-- some statements, e.g.  
y<=a and b;
```


```
end process;
```

 

```
process  
begin
```

```
-- some statements, e.g.  
y<=a and b;
```

```
wait on a, b;  
end process;
```

 

If **a** or **b** input values do not change,  
the value of **y** remains unchanged  
← the property of a combinational circuit

- To speed up simulations, VHDL requires specifying sensitivity lists, i.e., the lists of all signals whose change requires a new simulation run of the process. Quartus discovers incomplete lists and shows warnings. Please correct it.
- The sensitivity lists control the simulation. The incomplete lists create incorrect simulations.
- **A sensitivity list is not analogous to function parameters!** It is the alternative syntax forms of the process with the "wait on" command. Instead of writing "wait on" signals at the end of a process, we see them at the beginning.

```
process(a,b)
begin

-- some statements, e.g.
y<=a and b;

end process;
```

```
process
begin

-- some statements, e.g.
y<=a and b;

wait on a, b;
end process;
```

- Assembling a circuit from code is not an easy task, so a subset of VHDL commands is only synthesizable. We must also adhere to many strict rules. In part intended only for simulations, we can use anything because they are not compiled as circuits, but executed as programs.

# Arithmetic in Circuits


---

How is it done?


Logic Circuits textbook, chapter 6.

# Multiplication by a Power of 2

$$x * 2^1$$

 


$$x * 2^3$$

 





# Division by Powers of 2 - Wires

 


$\text{unsigned}(x) / 2^1$

 


$\text{signed}(x) / 2^1$

 


$x \bmod 2^1$

 

$\text{unsigned}(x) / 2^3$

 


$\text{signed}(x) / 2^3$

 


$x \bmod 2^3$


 
# Multiplication by the Sum of Powers of 2




a binary complement of  $x$

 




*Quartus multiplies by  $2^N - 1$  sometimes*

 - *by using an adder...*
- *by a multiplier*


   
# Combinational Arithmetic Circuits





*By minimizing the SoP or PoS, it is appropriate to design:*



*and other types*  $<=$   $=$   $/=$   $>=$

$\neq$  is  $!=$  in C,  $\sim=$  in Matlab,  $<>$  in Basic or Pascal,  
but  $/=$  in VHDL

    
If a constant  $K \mid 2^N$ , i.e.,  $K$  is divisible by a  $N$  power of 2, where integer  $N > 0$ , then  $K$  has  **$N$  lower bits = '0'**.  
In that case,  $x < K$  and  $x \geq K$  comparators are smaller because they can test only the upper non-zero bits.



# Operation with two general numbers x,y

*SoP and PoS minimization give too complex results for the following circuits. Their decompositions are necessary:*



➤ Comparators

 


*and comparisons*

$>=$   $>$   $<=$


➤ Adders and subtractors

  

➤ Multipliers

 

 
Divisions by the constants  $K \neq 2^N$  can be approximated




*Note: In LCD, xcolumn and yrow coordinates can be divided by any number with the aid of counters, see [LCD Backgrounds](#) page 21.*

**Do not use**  
the direct divisions by  
a general number or by constant  $\neq 2^N$   
because they have extremely  
complex circuit implementations

!!!

 

# Use LSP tools Checker of Projects

 

Checker of VEEK-MT2 Project (Alpha version) - C:\SPS2024L\LSP\_WeekMT2\_TestWarningMessages\_Q20\Week...

File

ToDo in Quartus Project | Log of Activities | Adjust VWF

Type	Code	Number of Descriptions	Occurrences in Items
Disallowed	WARNING_DIVIDE	4	The project creates disallowed divider
Disallowed	WARNING_LOOP	2	Info (278004): Inferred divider/modulo megafunction ("lpm_divide") from the following logic: "LCDlogic1.inst Mod0" File: C:/SPS/LSP_WeekMT2
Disallowed	WARNING_LATCH	2	_TestWamingMessages_Q20/LCDlogic1.vhd Line: 148
Disallowed	WARNING_SENSITIVITY	3	Info (12130): Elaborated megafunction instantiation "LCDlogic1.inst lpm_divide:Mod0"
			File: C:/SPS/LSP_WeekMT2_TestWamingMessages_Q20/LCDlogic1.vhd Line: 148
			Info (12133): Instantiated megafunction "LCDlogic1.inst lpm_divide:Mod0" with the following parameter: File: C:/SPS/LSP_WeekMT2
			_TestWamingMessages_Q20/LCDlogic1.vhd Line: 148

< >

The code created an disallowed division circuit.  
If you need more information than you see here,  
search for 'lpm\_divide' in Quartus compiler messages.

ToDo