 


Logic Systems and Processors *cz:Logické systémy a procesory*

Lecturer: Richard Šusta

richard@susta.cz, susta@fel.cvut.cz,
+420 2 2435 7359

Version V1.0



Stable Combinational Loops in **SRAM MEMORIES**

- Types: RWM (RAM), ROM, FLASH, SSD
- **RAM** = **R**andom **A**ccess **M**emory or **RWM** = **R**ead **W**rite **M**emory
- RAM memories:
SRAM (Static), **DRAM** (Dynamic).

Type	CMOS	Area per cell	Access	First Reads/Writes Latency
SRAM	cca 6 to 8	$\sim 140 F^2$	always	$< 1\text{ns} - 5\text{ns}$
DRAM	1	$6 \text{ to } 10 F^2$	requires refresh	$25 \text{ ns} - 40 \text{ ns}$


F^2 - 2D Feature - the smallest dimension realizable by a used technology





- 1) **SSDs or Flashes**, even the fastest ones, have their first read latencies in tens of microseconds and write times in the hundreds of microseconds.
In FPGA, they are used to configure static interconnects between elements but are too slow as working memories.
- 2) **DRAM** productions need unique technology processes
⇒ It is difficult to integrating with technologies of logic circuits
- 3) **DDRx** memories accelerate only sequential readings/writings.
Their first read/write latencies are slower.

*We will deal with DRAMs and DDRx
in the lecture about processor memories.*


Combinational Loops

 





Unstable: Oscillators

  


Stable: SRAMs

 

SRAM Stable Combinational Loop

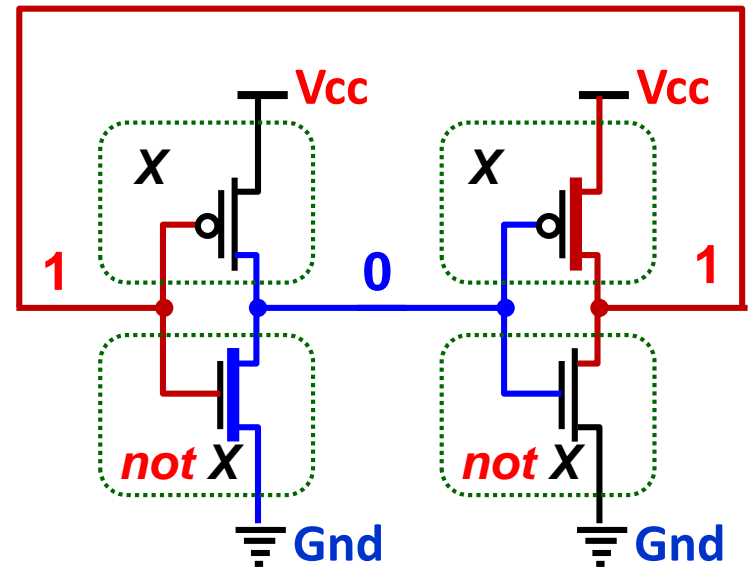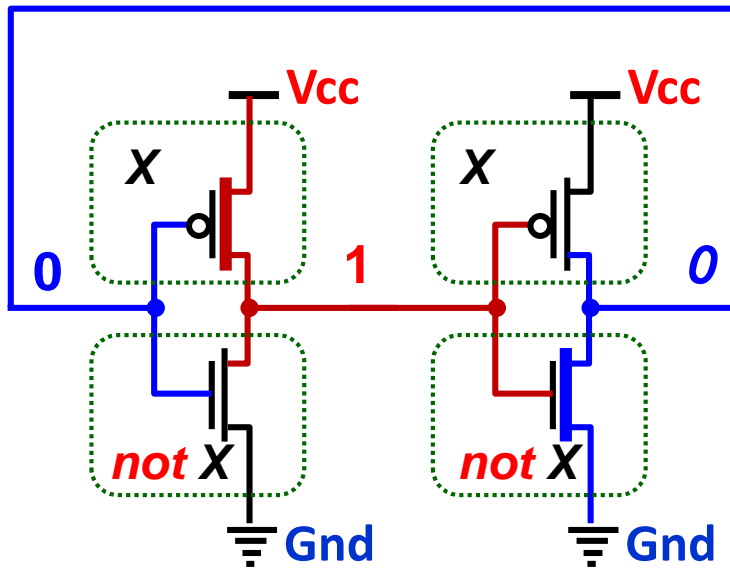  


One SRAM Memory Cell





 


read | write 0 | write 1

 Two bit lines, positive and negated, ensure that at least one CMOS has good voltage conditions in each state of the inverter memory loop.




Simplified Memory Cell

     


MATRIX OF MEMORY CELLS

Memory Matrix

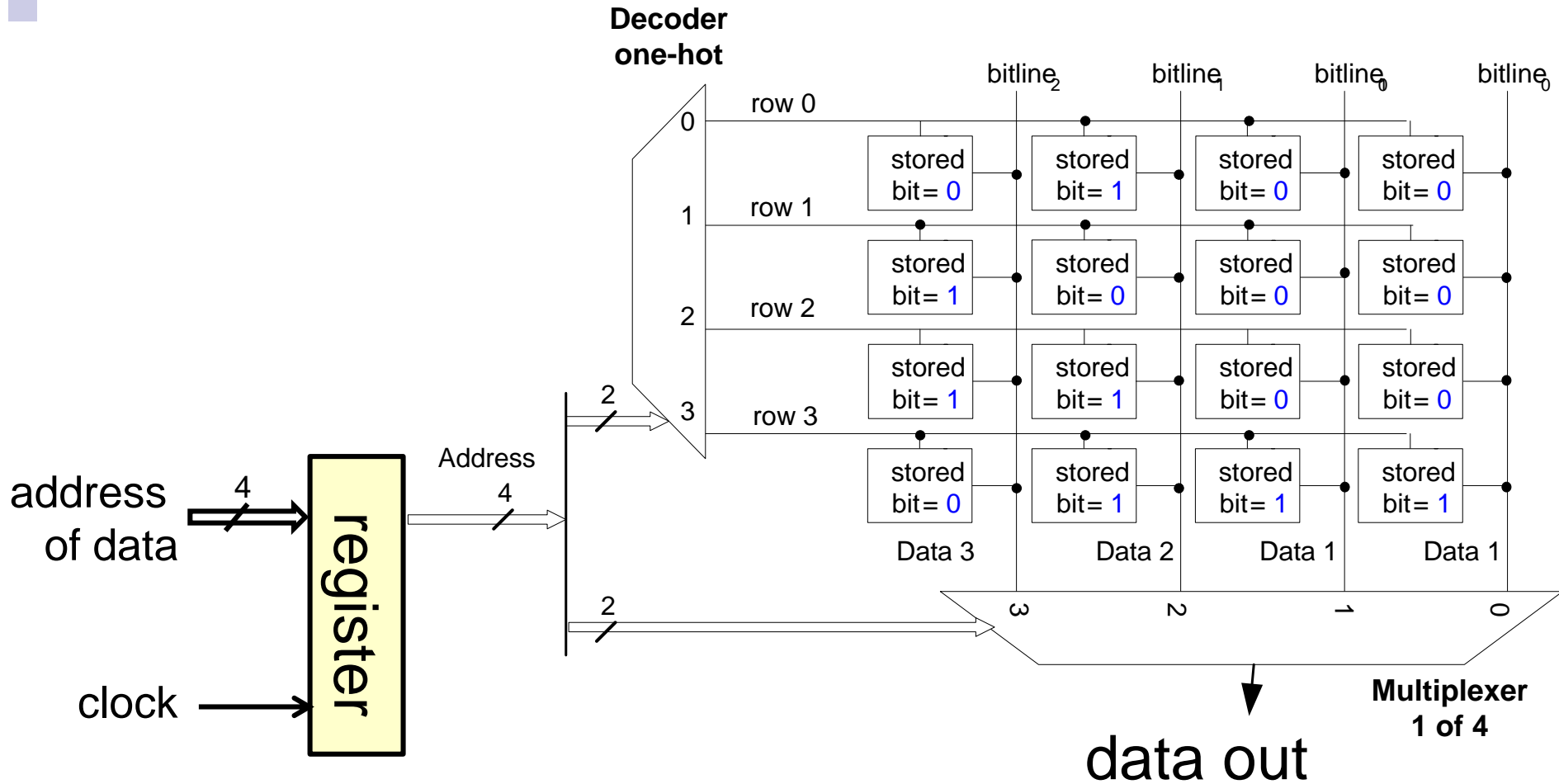


Register of address is a necessary condition for the implementation and to reduce power consumption

Memory Matrix - Example 1/4

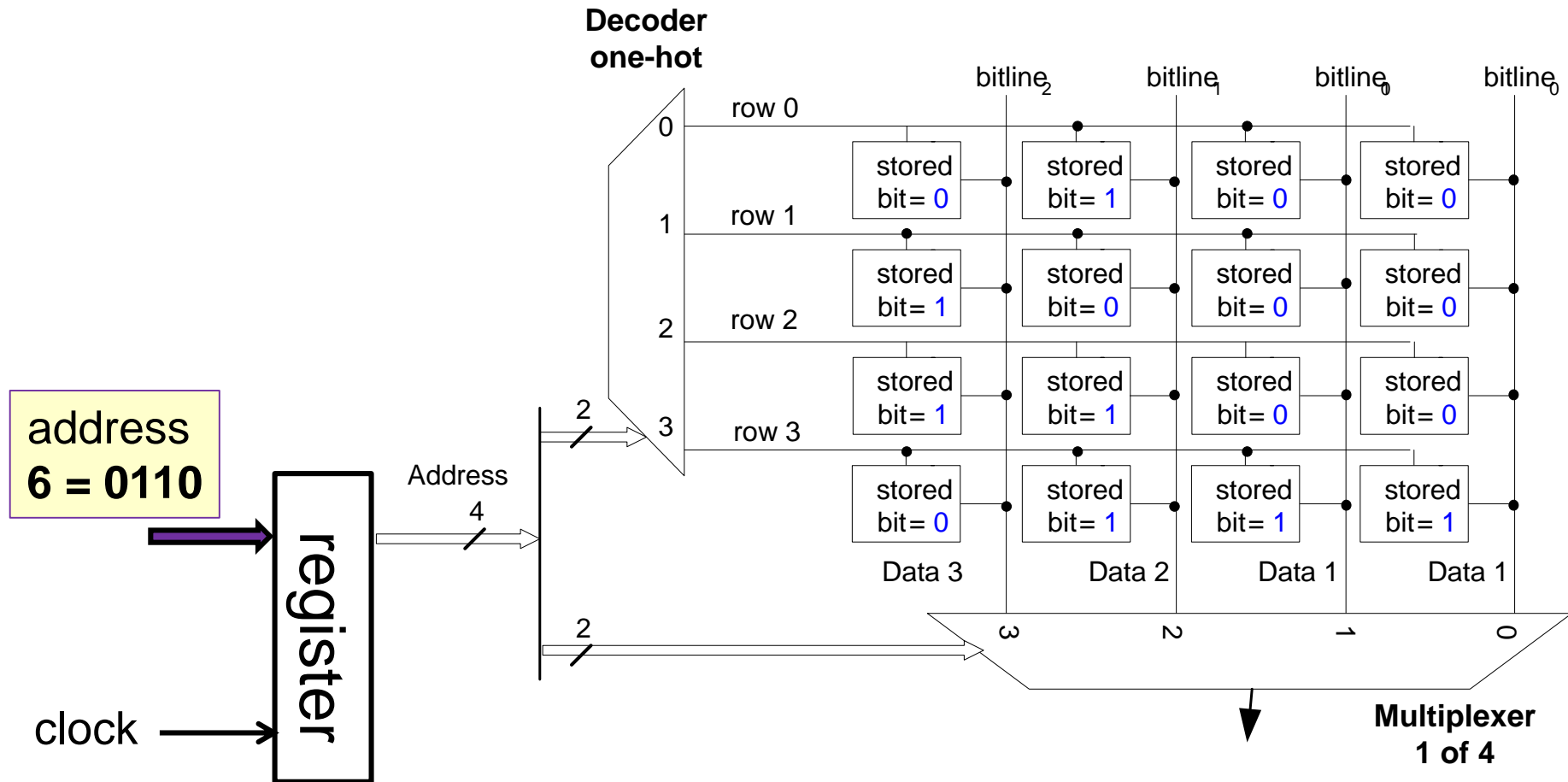


Address value is waiting for the rising edge of clocks

Memory Matrix - Example 2/4

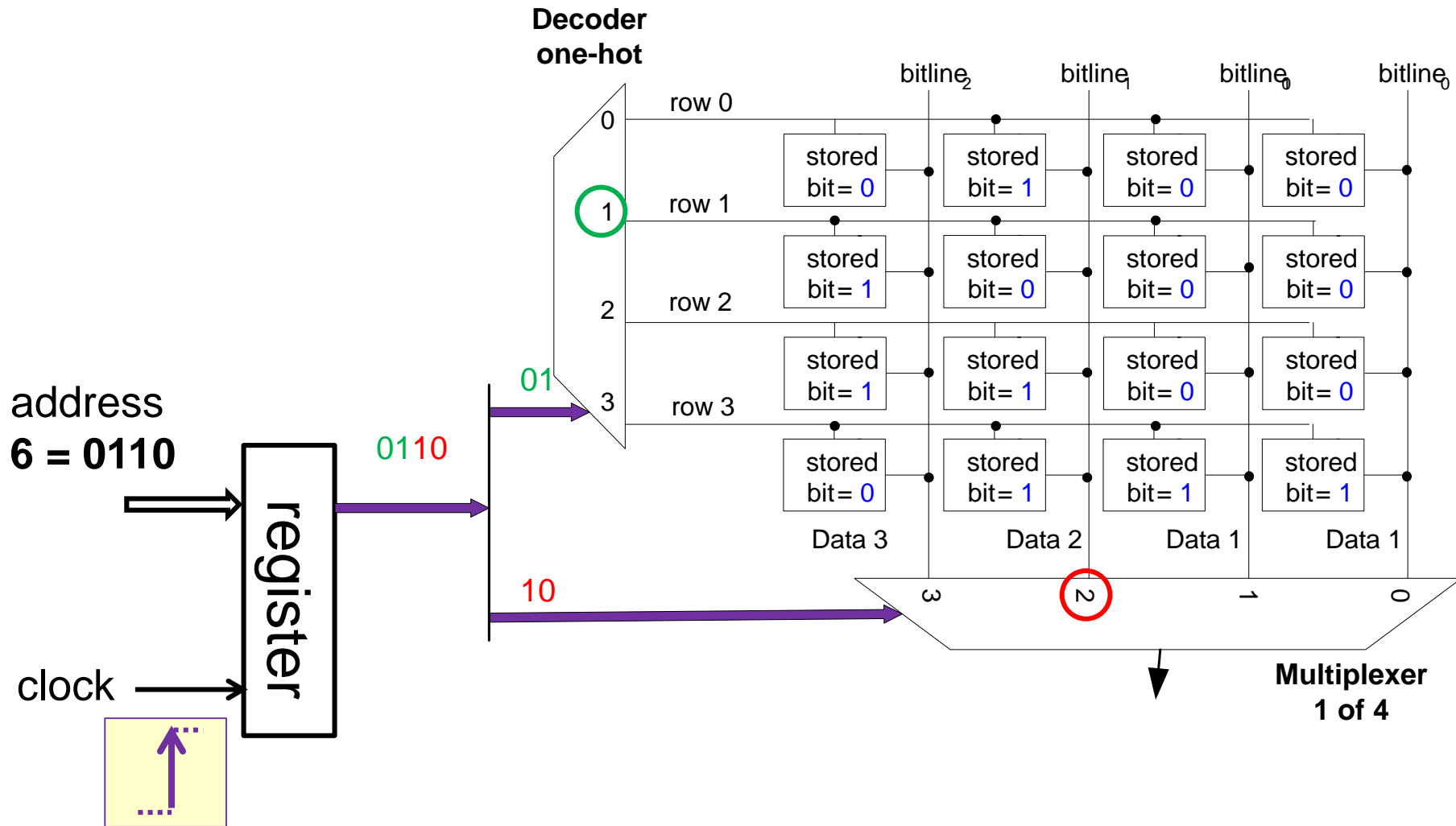


Address was loaded on the rising edge of clocks and divided to two parts, higher and lower bits

Memory Matrix - Example 3/4

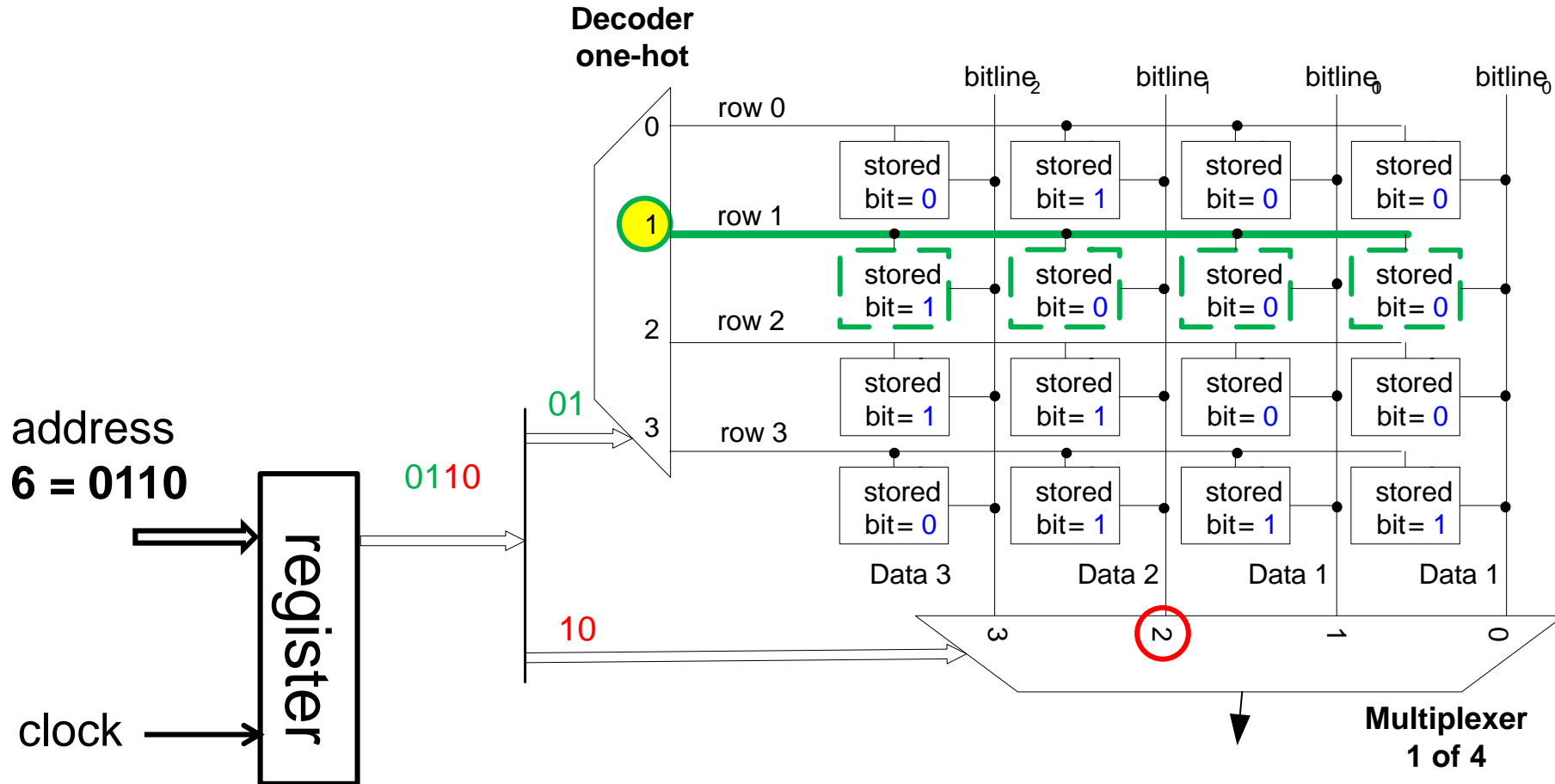

*Output of one-hot decoder 1 from N activate row
and of cell in it.*

Memory Matrix - Example 4/4

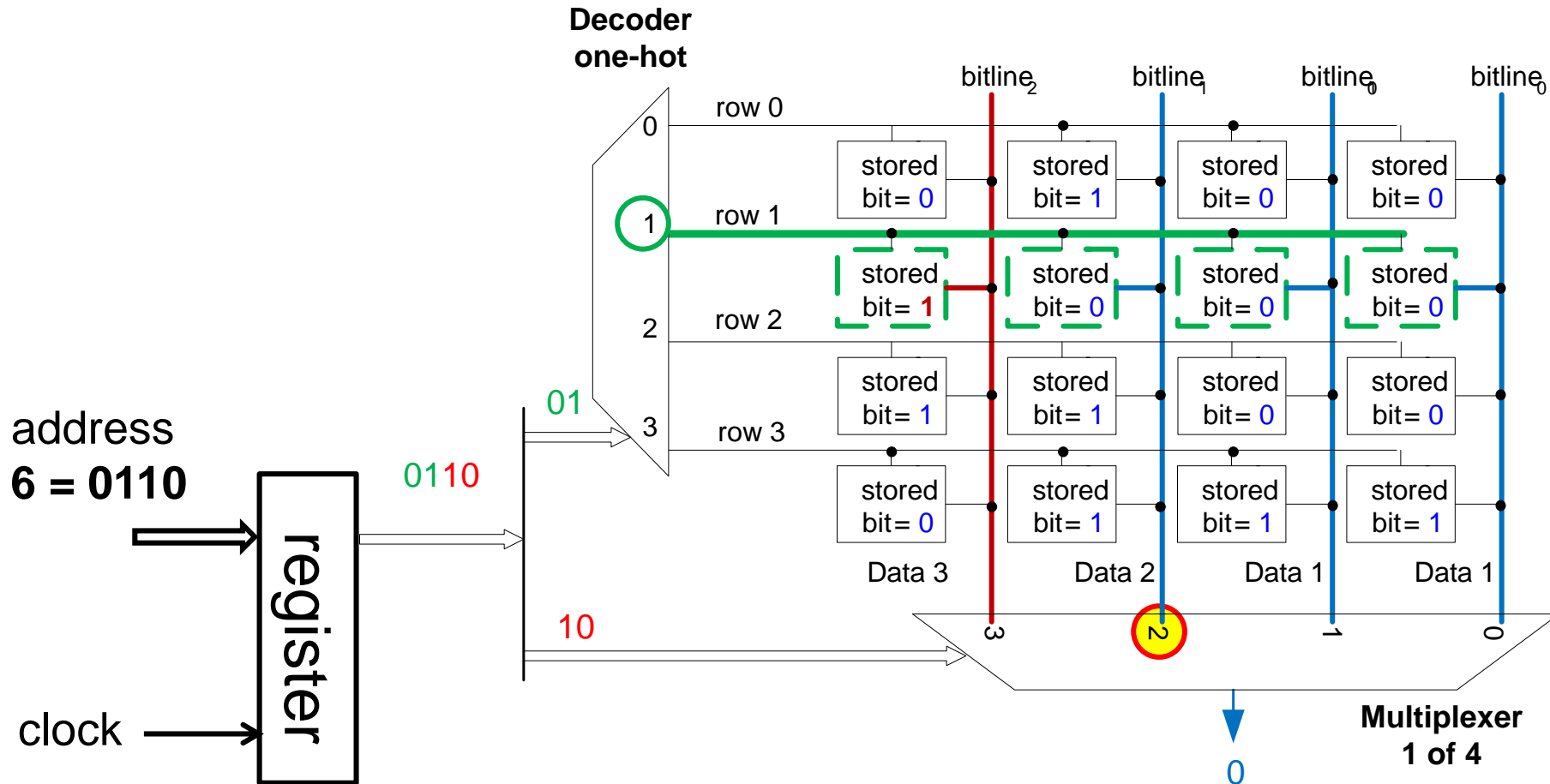

The cells are connected to bitlines, but the output multiplexer selects only one value - Data 2 = 0



ROM (read-only) memory by logic cells

On Cyclone II, it is mostly implemented by multiplexers
1 from 16, then 1bit memory type $N \times 1$ requires>

- 16×1 : 1 row, 1 multiplexer
- 256×1 : 2 rows, $16+1=17$ mux (multiplexers).
- 4 kbit $= 2^{12} \times 1$: 3 rows, $256+16+1= 273$ mux.
- 64 kbit $= 2^{16} \times 1$: 4 rows, $4096+256+16+1 = 4369$ mux.
- 1 Mbit $= 2^{20} \times 1$: 5 rows, $65536+4096+256+16+1 = 69905$ mux.

cca 1/15 memory capacity must be added for selection logic.

For larger storage, it is too ineffective to use multiplexers that always select data even if they are not in use.




A memory matrix with 16 input multiplexers and decoders 1 from 16 requires for 1 bit memory $N \times 1$


- 256 x 1 - 2 rows, 1 multiplexer + 1 decoder $1 \times N = 2$ LE
- 64 kbit = $2^{16} \times 1$ - 4 rows, 17 mux + 17 dec. = 34 LE.
- 16 Mbit = $2^{24} \times 1$ - 6 rows, 273 mux + 273 dec. = 546 LE.

Selection logic was significantly reduced and requires less power, because we activate only one 16x16 matrix.

1 port SRAM

 

 2 port SRAM - it doubles read/write logic



Memories always require address register



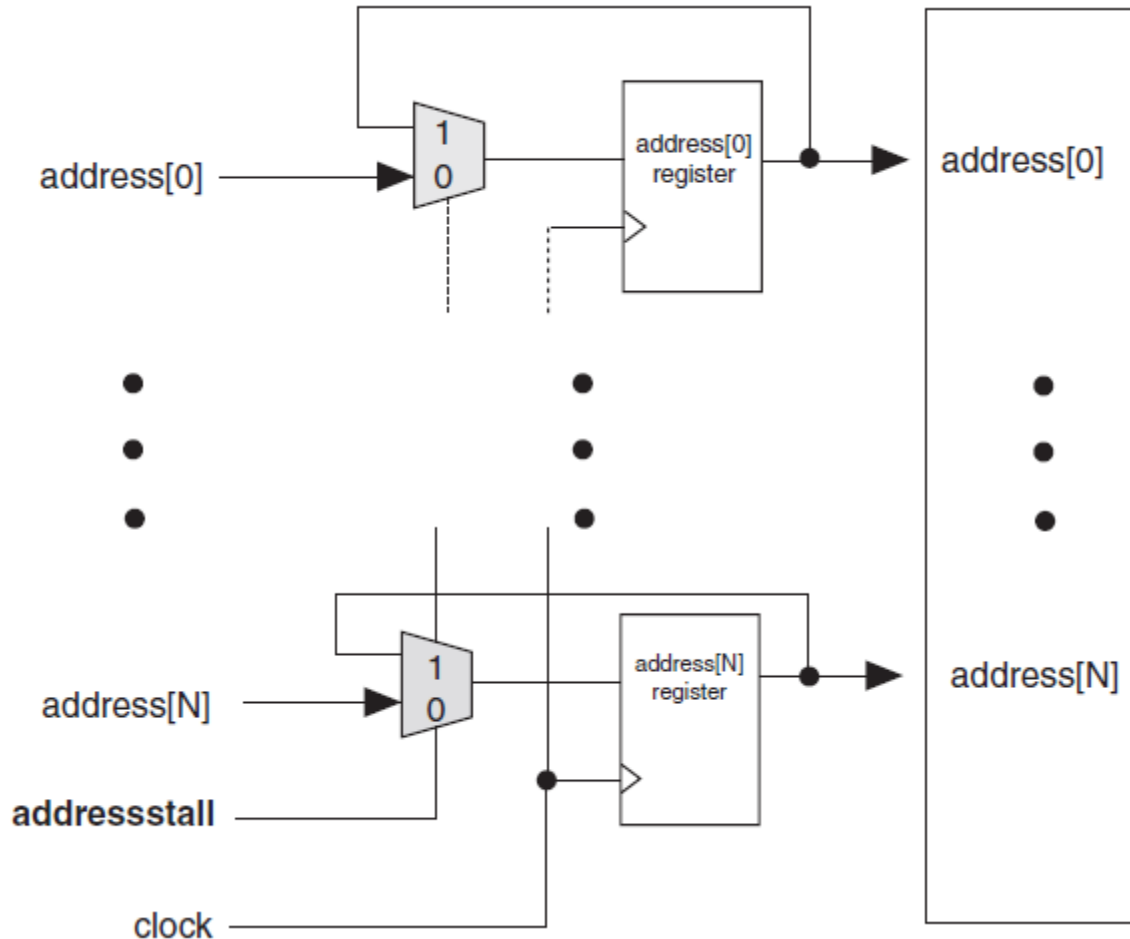


Image source: Intel

OK

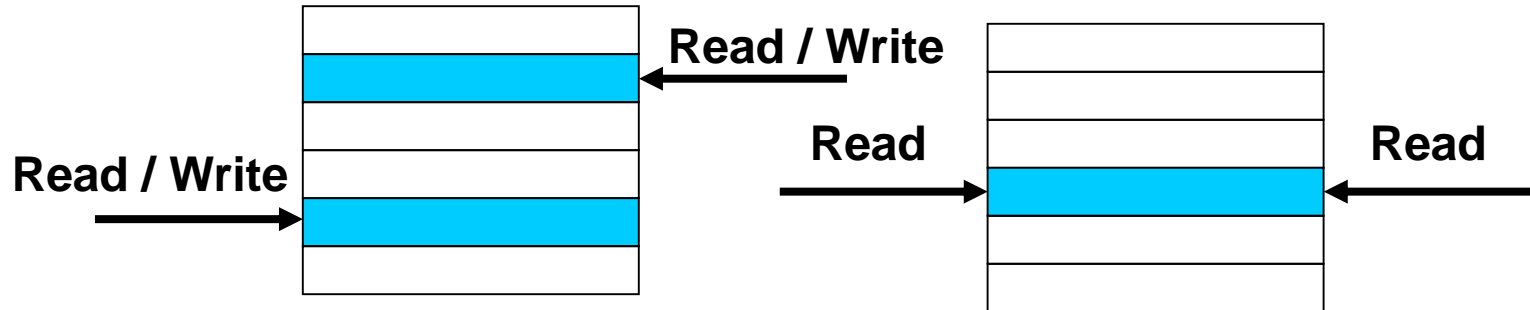


Problem

 


Cyclone family SRAM

Read & Write to the same address returns old data, but only if clocks are the same, otherwise the result is unknown

Reading Hex Keyboard by Matrix

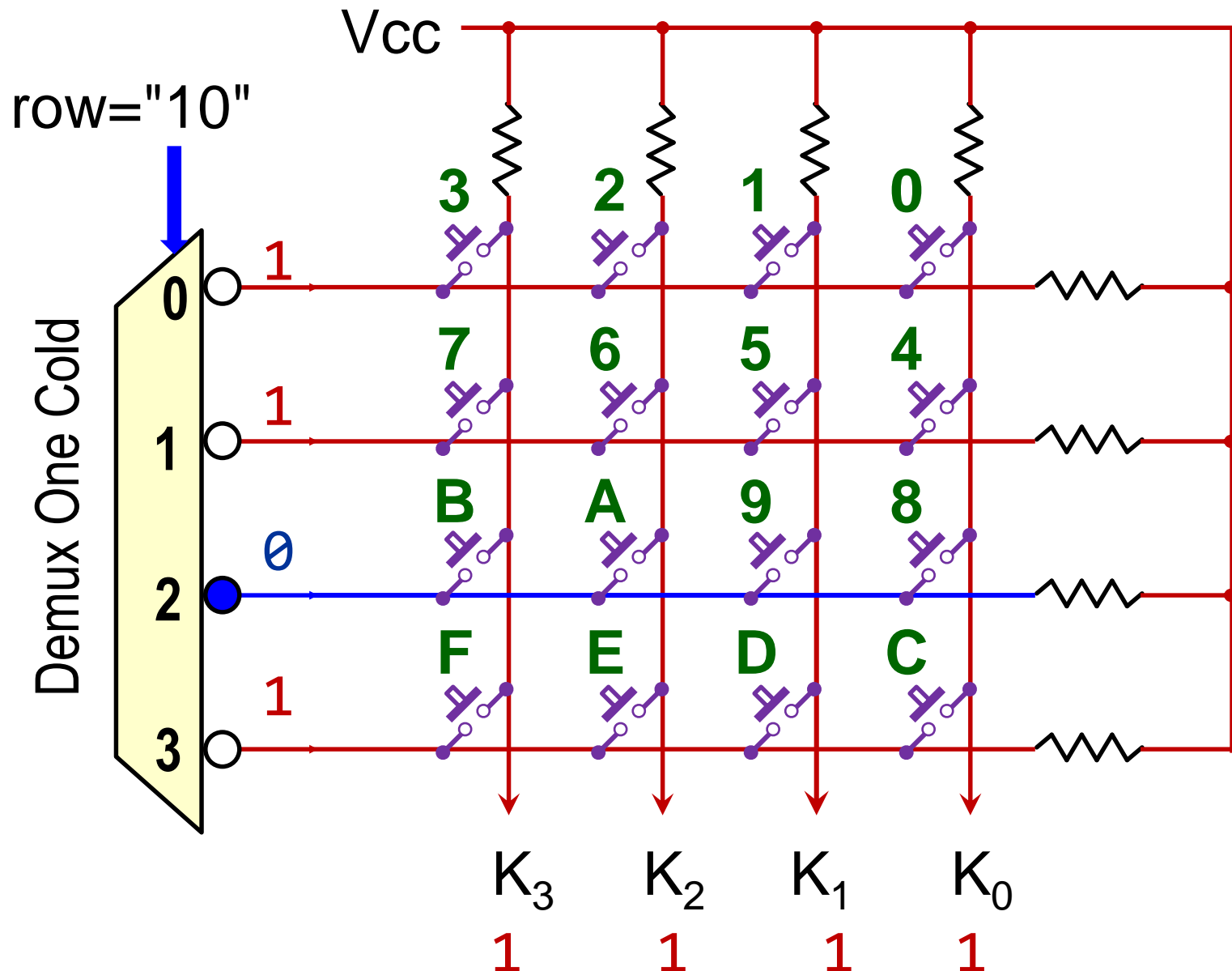

Reading Hex Keyboard by Matrix

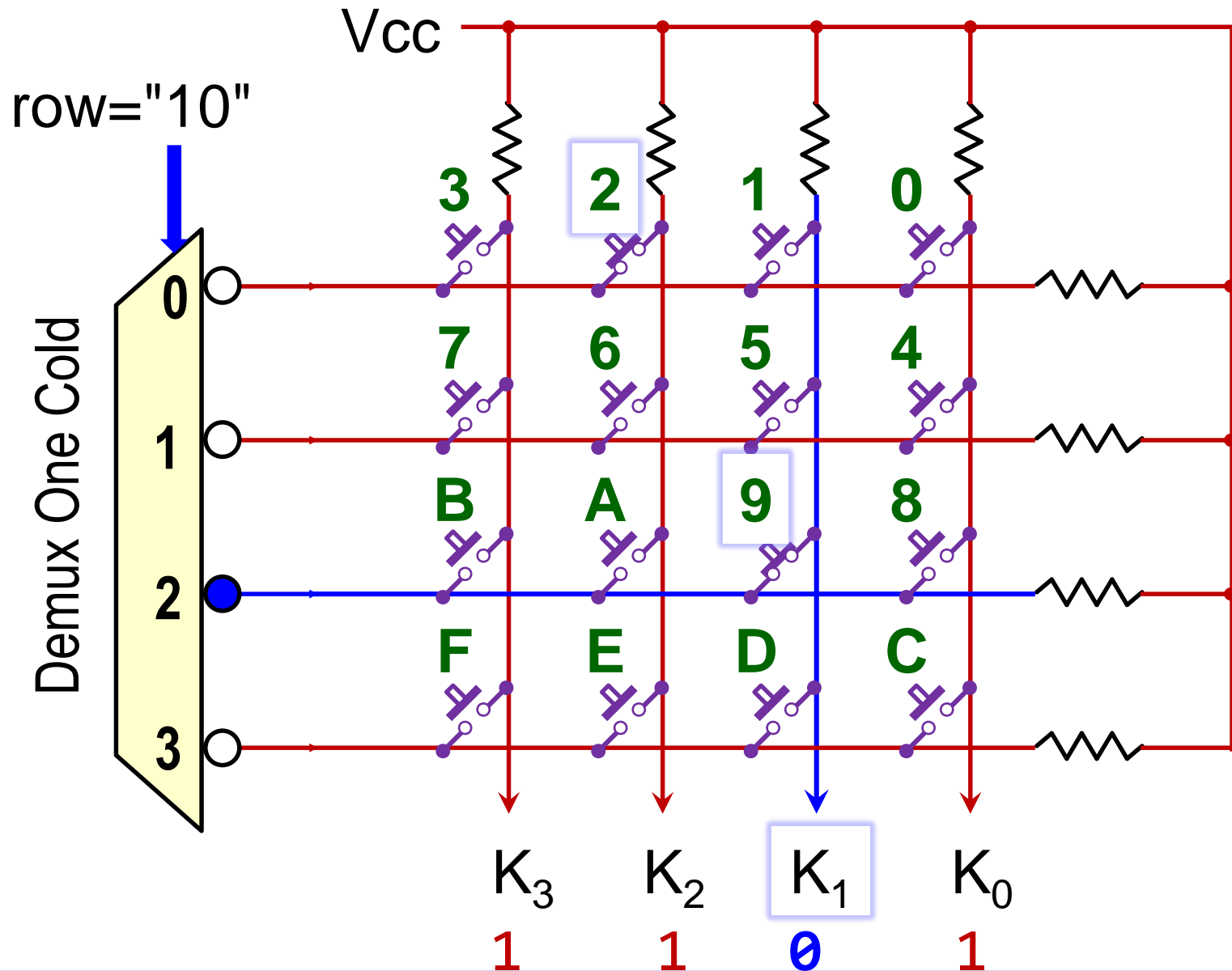

LCD - Liquid Crystal Display



*precisely TN LCD (Twist Nematic Liquid Crystal Display)
also uses a memory matrix*



*LSP course is also about the principles of modern digital systems,
so we briefly look inside the topic of the third training task*

Image: [Terasic](https://www.terasic.com/)

 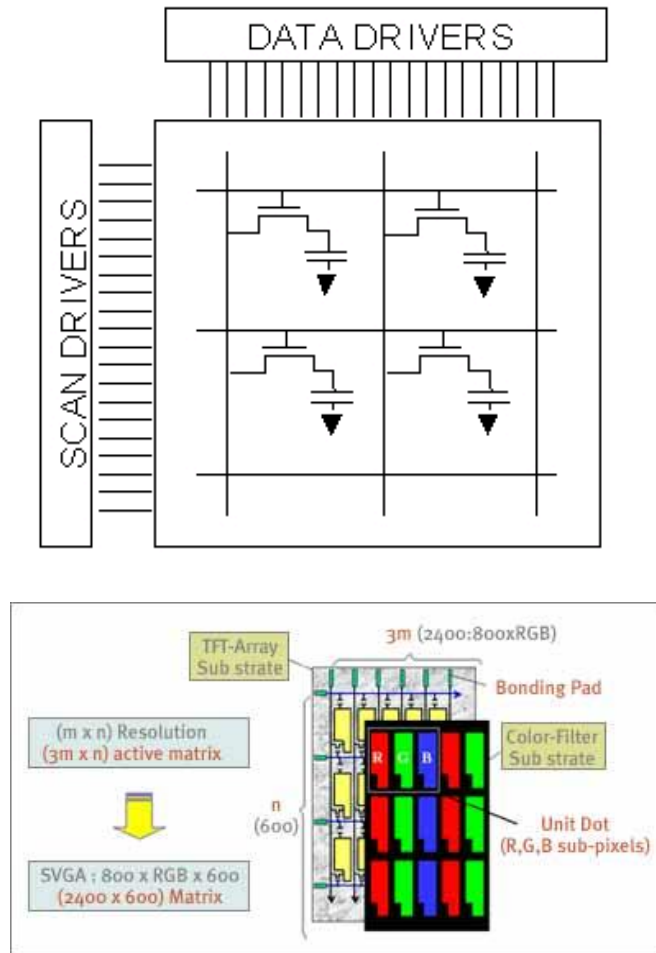
TFT (Thin-Film Transistors) with active matrix




Source: 

LCD capacitors distinguish multiple levels!

TFT (switch) + LC cell (capacity)

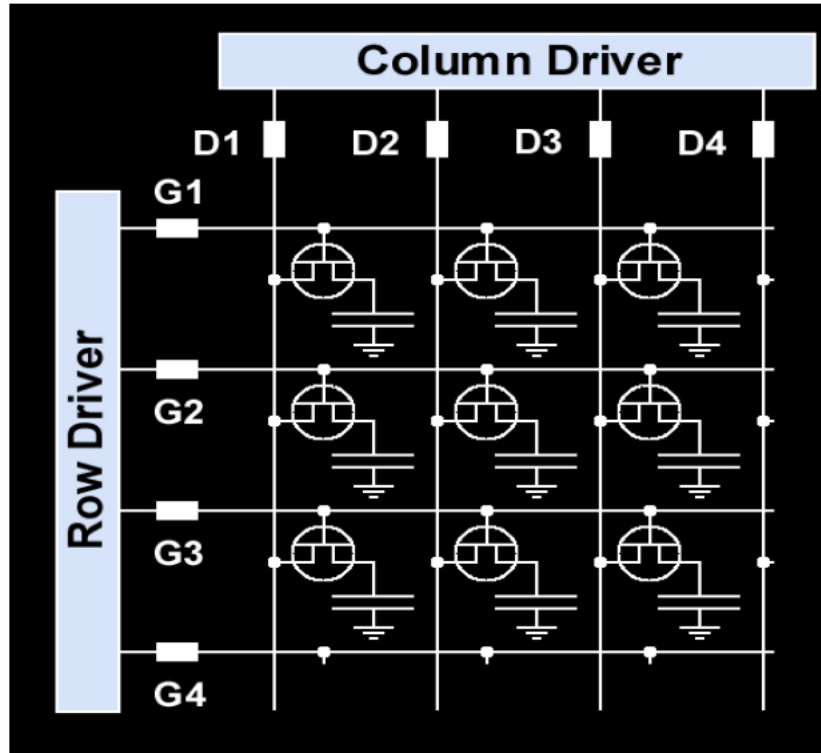


Hydrant (switch)+ Bucket (capacity)

 

Source: Dr. Zhibing Ge, College of Optics and Photonics



LCDs write whole lines

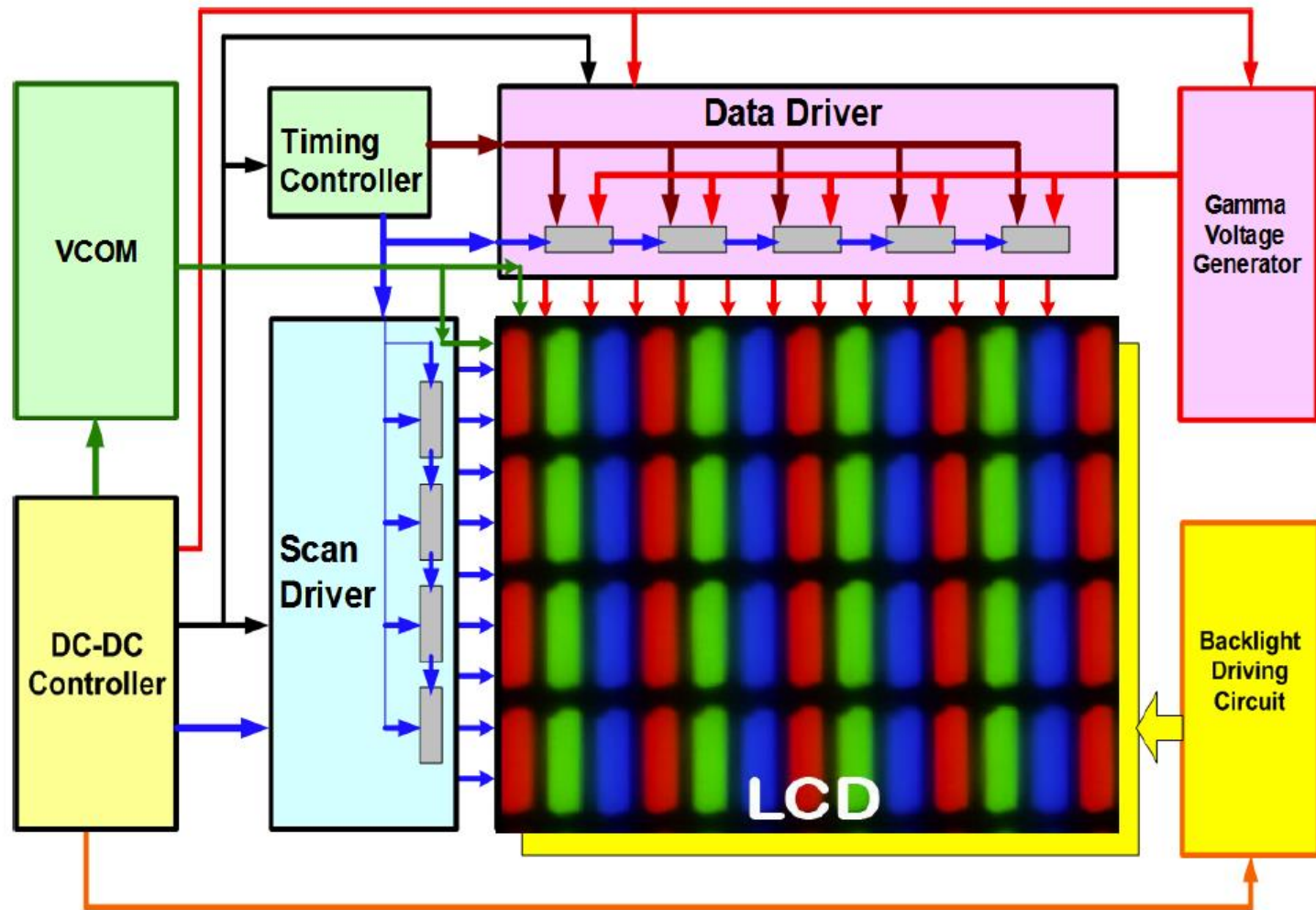

Source: Dr. Zhibing Ge, College of Optics and Photonics



LCD versus OLED types

TN, IPS <-technologies-> AMOLED, PMOLED

  

Source: <https://www.androidauthority.com/>

LCD versus OLED


 
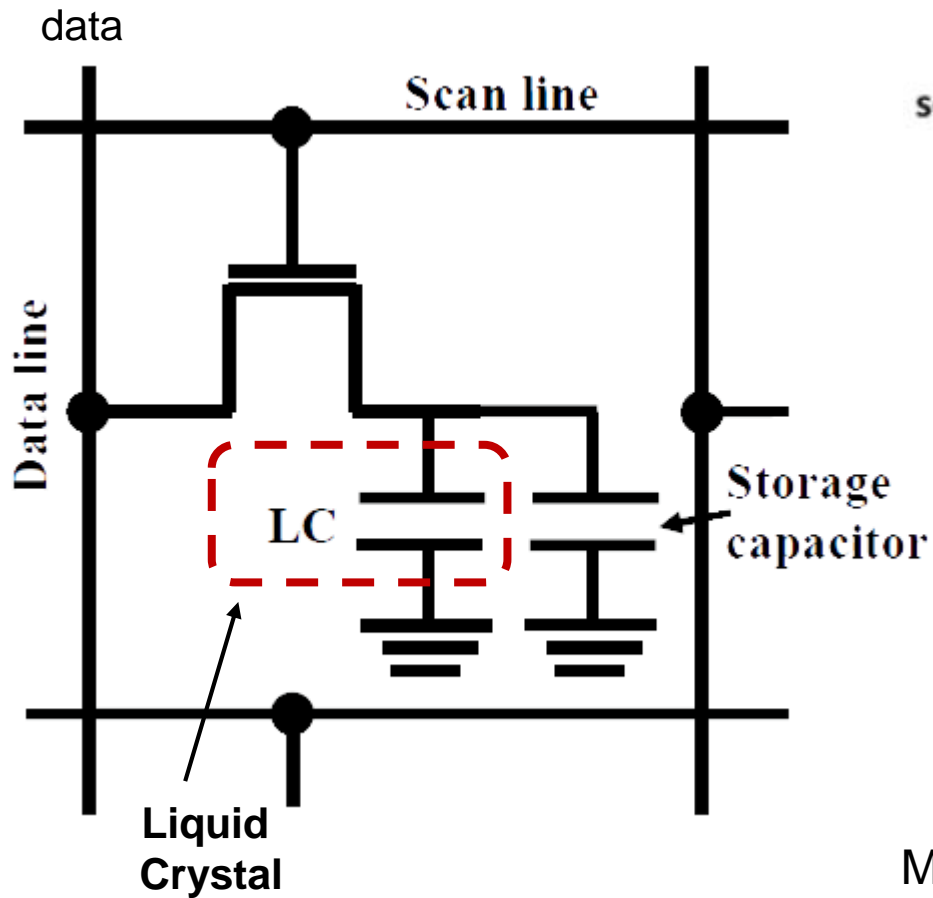


M1 NMOS powers the OLED according to the voltage of capacitor C1.

Source: Digital PWM-driven AMOLED display..., 2014 IEEE International Solid- State Circuits Conference (ISSCC)



LCD versus OLED - Refreshing

LCD TFT

   

The capacitors need **regular refreshes**.
Their typical values range
from 100 fF (=0.1pF) to 2000 fF
(=2pF).

Linear Polarization

  

Source: https://tikz.net/optics_polarization/


 


Image source:

 

<https://www.orientdisplay.com/>



Source:

